

## Lecture 12

# CMOS Delay & Transient Response





Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology


Hoboken, NJ 07030

    Adapted from Lecture Notes, David Mahoney Harris CMOS VLSI Design



 
# Transient Response

- **DC analysis** tells us  $V_{out}$  if  $V_{in}$  is **constant**
- **Transient analysis** tells us  $V_{out}(t)$  in response to a **change** in  $V_{in}$
- Requires solving differential equations
- Input is usually considered to be a step or ramp
  - From GND to  $V_{DD}$  or vice versa



 
# Delay Definitions

- $t_{pdr}$ : *rising propagation delay*
  - maximum time from input crossing  $V_{DD}/2$  to rising output crossing  $V_{DD}/2$
- $t_{pdf}$ : *falling propagation delay*
  - maximum time from input crossing  $V_{DD}/2$  to falling output crossing  $V_{DD}/2$
- $t_{pd}$ : *average propagation delay*
  - $t_{pd} = (t_{pdr} + t_{pdf})/2$
- $t_r$ : *rise time*
  - from output crossing  $0.2 V_{DD}$  to  $0.8 V_{DD}$
- $t_f$ : *fall time*
  - from output crossing  $0.8 V_{DD}$  to  $0.2 V_{DD}$


 
# Delay Definitions (cont.)

- $t_{cdf}$ : *falling contamination delay*
  - minimum time from input crossing  $V_{DD}/2$  to falling output crossing  $V_{DD}/2$
- $t_{cdr}$ : *rising contamination delay*
  - minimum time from input crossing  $V_{DD}/2$  to rising output crossing  $V_{DD}/2$
- $t_{cd}$ : *avg. contamination delay*
  - $t_{pd} = (t_{cdr} + t_{cdf})/2$




# Delay in CMOS Circuits

- A switching CMOS gate generates output current in response to changing input voltages
- All nodes have some finite capacitance (to ground)
  - gate capacitance
  - parasitic source/drain (diode) capacitance
  - parasitic wiring capacitance
- Transient waveforms found by solving:

$$C_{node} \cdot (dV_{node}/dt) = \sum_k I_{k,node}$$

for each node in circuit

 

# Inverter Step Response



- Find step response of inverter driving  $C_{load}$

$$V_{in}(t) = u(t - t_0) \cdot V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$


$$dV_{out}(t)/dt = -I_{dsn}(t)/C_{load}$$
 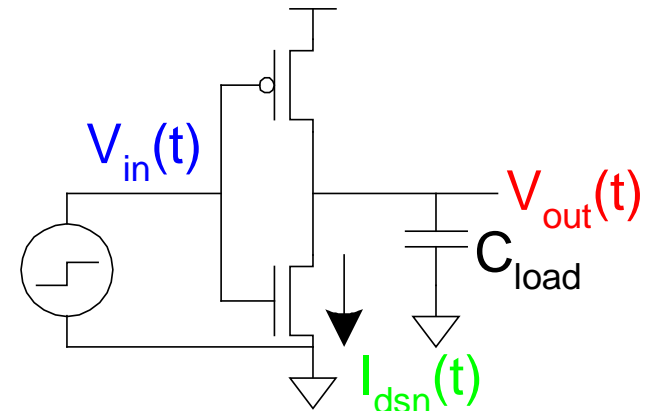
$$I_{dsn}(t) = \begin{cases} 0 & \text{for } t < t_0 \\ (\beta/2m) \cdot (V_{DD} - V_t)^2 & \text{for } V_{out} > V_{DD} - V_t \\ \beta \cdot (V_{DD} - V_t - V_{out}(t)/2m) \cdot V_{out}(t) & \text{for } V_{out} < V_{DD} - V_t \end{cases}$$



 
# Simulated Inverter Delay

- Solving differential equations by hand is too hard
- SPICE simulator solves the equations numerically
- Uses more accurate I-V models too!
- But simulations take time to write!


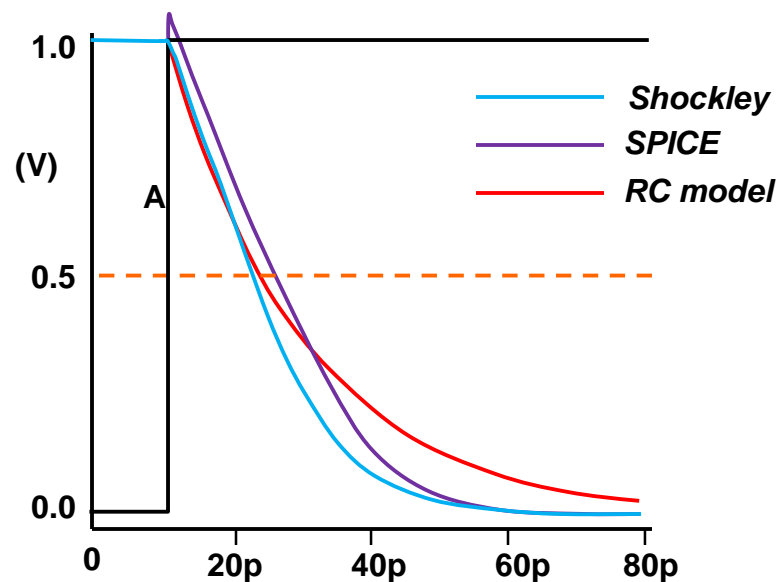
# Delay Estimation


- We would like to be able to easily estimate delay
  - For exploration of design space, don't need to be as accurate as simulation
  - Want a technique where its easier to ask “What if?”
- The step response usually looks like a 1<sup>st</sup> order RC response with a decaying exponential.
- Can we model conducting transistor as effective resistance?




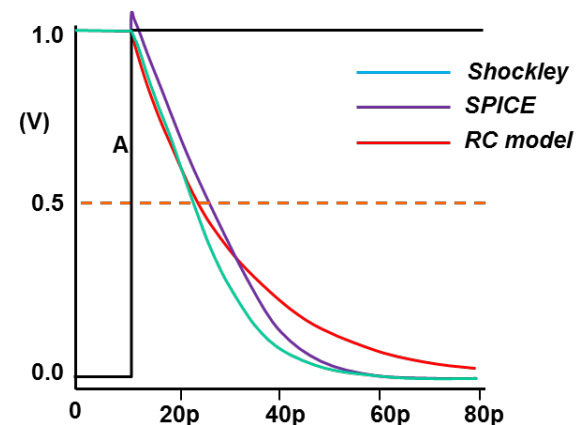
# Effective Resistance

- Simplification: treat transistor as resistor
  - Replace  $I_{ds}(V_{ds}, V_{gs})$  with effective resistance  $R$
  - $I_{ds} = V_{ds}/R$  or 0 depending on gate voltage
- Pick  $R$  to best model dynamic response of gate
  - Too inaccurate to predict current at any given time
  - But good enough to predict gate delay




# Capacitance

- Input to CMOS gate presents effectively infinite input resistance
- The dominant load in CMOS circuits is capacitance
- Capacitance exists wherever there are two conductors separated by a thin insulator
- Gate to channel capacitor is very important
  - Creates channel charge necessary for operation
- Source and drain have capacitance to body
  - Parasitic capacitance across reverse-biased diode depletion region
  - Called diffusion capacitance because it is associated with source/drain diffusion
- Long interconnect wires also have parasitic capacitance to the substrate
 
# Gate Capacitance


- Gate is top plate of capacitor
- Assume bottom plate is source
  - In cut-off, bottom plate is actually the body
  - In linear mode, bottom plate is channel which is connected to source and drain
  - In saturation, bottom plate is channel connected to source
- $C_g \approx \epsilon_{ox} \cdot W \cdot L / t_{oxe} = C_{oxe} \cdot W \cdot L = C_{permicron} \cdot W$  (for  $L = L_{min}$ )
- $C_{permicron}$  is typically about 1-2 fF/ $\mu\text{m}$  of width



 
# Diffusion Capacitance

- $C_{sb}$ ,  $C_{db}$
- Diffusion (source/drain) region is resistive and capacitive (to body)
- Capacitance depends on area and perimeter
- Use small as possible diffusion nodes
- Comparable to  $C_g$  for min. contacted diffusion
- Use  $C_g/2$  for merged
- Varies with process


Isolated  
Diffusion  
 $\approx C_g$   
 $C_{node} = 2 \cdot C_g$



 Shared  
Diffusion  
 $\approx C_g$   
 $C_{node} = C_g$




 Merged  
Diffusion  
 $\approx C_g/2$   
 $C_{node} = C_g/2$


 
# RC Delay Model

- Use equivalent circuits for MOS transistors
  - Ideal switch + capacitance and ON resistance
  - Unit nMOS has resistance  $R$ , capacitance  $C$
  - Unit pMOS has resistance  $2R$ , capacitance  $C$
- Capacitance (gate & diffusion) proportional to width
- Resistance inversely proportional to width




# RC Values

- Capacitance
  - $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$  of gate width in  $0.6 \mu\text{m}$
  - Gradually decline to  $1 \text{ fF}/\mu\text{m}$  in nanometer techs.
- Resistance
  - $R \approx 5\text{-}10 \text{ K}\Omega \cdot \mu\text{m}$  in  $0.6 \mu\text{m}$  process
  - Improves with shorter channel lengths
- Unit transistors
  - May refer to minimum contacted device ( $4 \lambda / 2 \lambda$ )
  - Or maybe  $W=1 \mu\text{m}$  device (doesn't matter as long as you are consistent)

	<b>AMI 0.6<math>\mu\text{m}</math></b>	<b>TSMC 250nm</b>	<b>TSMC 180nm</b>	<b>IBM 130nm</b>	<b>IBM 65nm</b>
$R_n$ ( $\text{k}\Omega \cdot \mu\text{m}$ )	9.2	4.0	2.7	2.5	1.3
$R_n$ ( $\text{k}\Omega \cdot 4\lambda$ )	7.7	8.0	7.5	9.6	10
$R_p$ ( $\text{k}\Omega \cdot \mu\text{m}$ )	19.9	8.9	6.5	6.4	2.9
$R_p$ ( $\text{k}\Omega \cdot 4\lambda$ )	16.6	17.8	18.1	24.7	22.3

 
# RC Values

- Estimate the delay of a fanout-of-1 inverter
- Set size (width) of PMOS to 2 x unit size to have equal pull-up (rising) and pull-down (falling) drive resistance


 
# Example: 3-input NAND


- Sketch a 3-input NAND with transistor widths chosen to achieve effective (worst case) rise and fall resistances equal to a unit inverter (R).





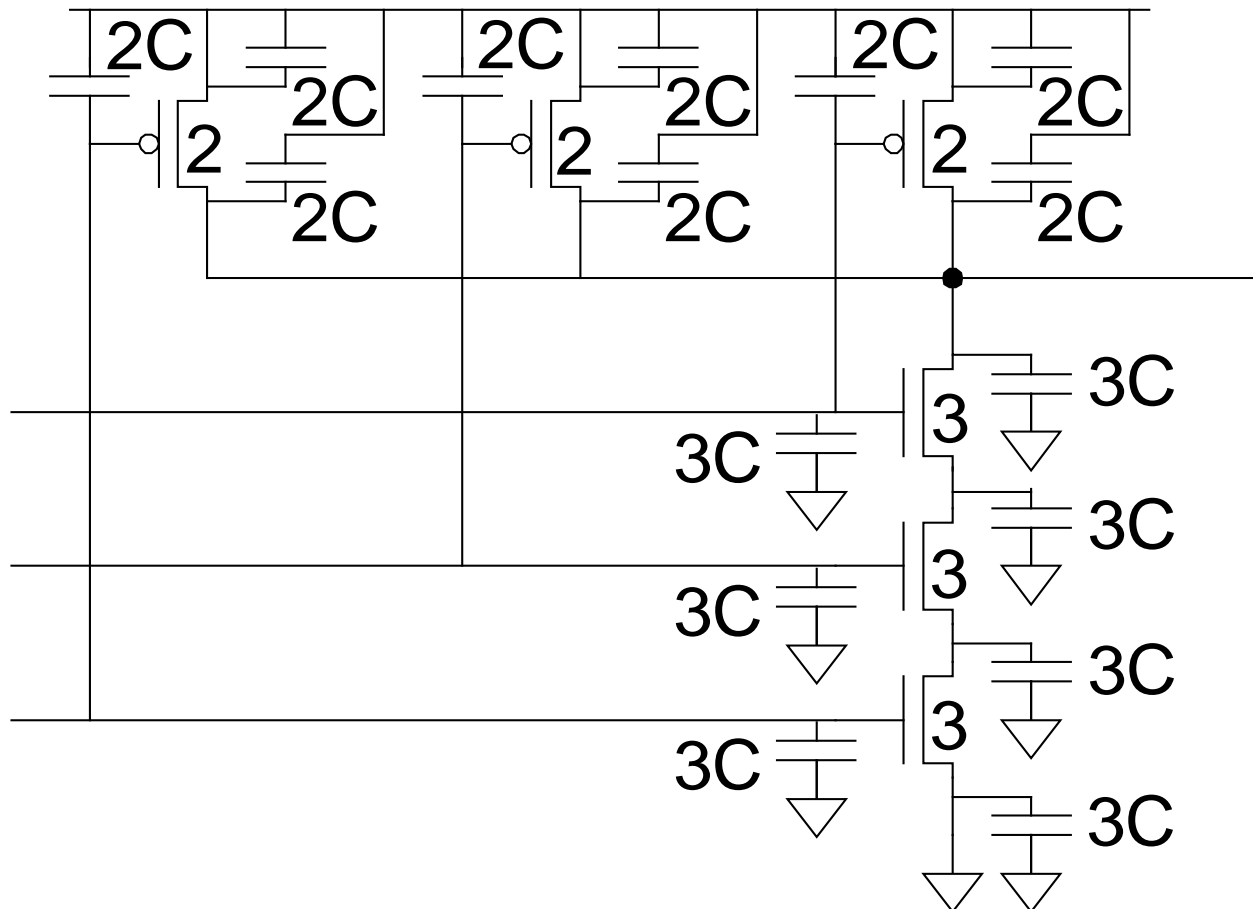
# 3-input NAND Capacitors

- Annotate the 3-input NAND gate with gate and diffusion capacitance.





 
# 3-input NAND Capacitors

- Annotate the 3-input NAND gate with gate and diffusion capacitance.



  
 
# Rise & Fall Delay

- What are worst-case rise and fall delays?




- How can we estimate delay of these networks?

# $\tau$ with multiple RC components

  

$$\tau = RC$$

 

$$H(s) = \frac{1}{1 + s[R_1C_1 + (R_1 + R_2) \cdot C_2] + s^2R_1C_1R_2C_2}$$

$$\tau = ?$$

- Second order response is too complicated
  - defeats whole purpose of simplifying to an RC network
- Can approximate to:

$$\tau \approx \tau_1 + \tau_2 = R_1C_1 + (R_1 + R_2) \cdot C_2$$

# Elmore Delay


- ON transistors modeled as resistors
- Pullup or pulldown network represented as an RC tree
  - root of tree is driving voltage source (often VDD or GND)
  - resistors are branches
  - leaves are capacitors at ends of branches
- Elmore delay to any target (node  $j$ ) in the branch:

$$t_{pdj} = \sum_i R_{sij} \cdot C_i$$

where:

- $i$  represents all the nodes in the branch
  - $C_i$  is the capacitance at node  $i$
  - $R_{sij}$  is the resistance of the shared path from the source to  $node_i$  and from the source to the target  $node_j$
- Elmore delay is conservative
    - over-estimates the delay

# Shared Path

 

- delay to node N is:


$$R_1 C_1 + (R_1 + R_2) \cdot C_2 + \dots + (R_1 + R_2 + \dots + R_N) \cdot C_N$$

- delay to node 2 is:

$$R_1 C_1 + (R_1 + R_2) \cdot C_2 + (R_1 + R_2) \cdot (C_3 + C_4 + \dots + C_N)$$



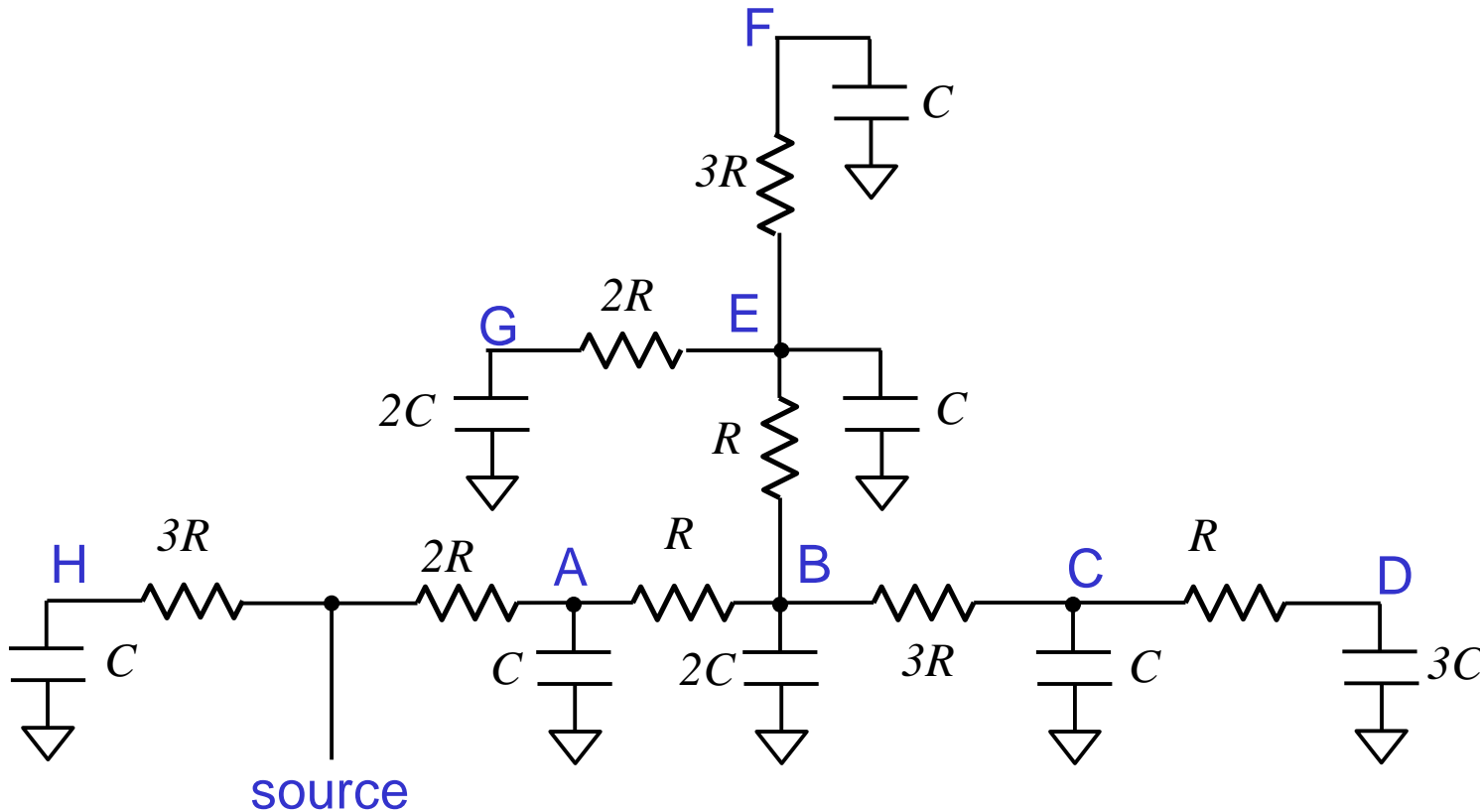
# Example: Elmore Delay

- Calculate delay from source to all nodes in circuit:


 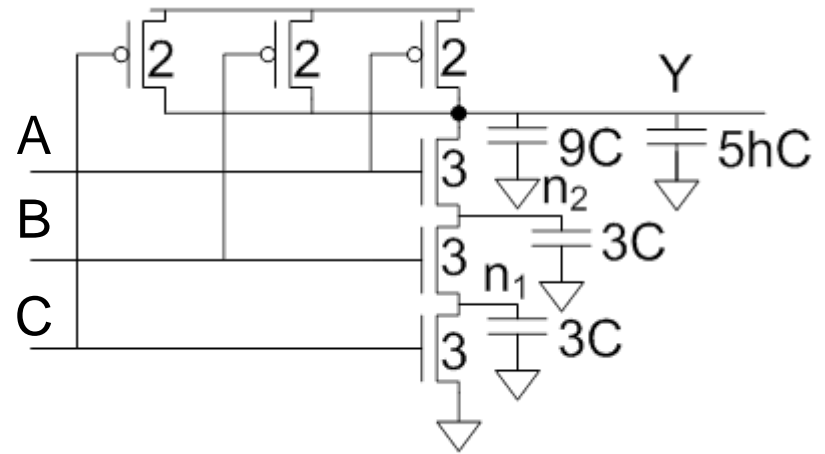 
# 3-input NAND: pull-down delay

- Estimate worst-case rising and falling delay of 3-input NAND driving  $h$  identical gates.



Worst case pull-down delay occurs when ABC goes from (110) to (111)




$$t_{pdf} = (3C)\left(\frac{R}{3}\right) + (3C)\left(\frac{R}{3} + \frac{R}{3}\right) + [(9 + 5h)C]\left(\frac{R}{3} + \frac{R}{3} + \frac{R}{3}\right)$$

$$t_{pdf} = (12 + 5h)RC$$


   
# 3-input NAND: pull-up delay

- Estimate worst-case rising and falling delay of 3-input NAND driving  $h$  identical gates.



Worst case pull-up delay occurs when ABC goes from (111) to (110)

$$t_{pdr} = [(9 + 5h)C](R) + (3C)(R) + (3C)(R)$$

$$t_{pdr} = (15 + 5h)RC$$

# Delay Components

$$t_{pdf} = (12 + 5h)RC$$

$$t_{pdr} = (15 + 5h)RC$$


- Delay has two parts
  - *Parasitic delay*
    - 15 or 12 RC
    - Independent of load
  - *Effort delay*
    - 5h RC
    - Proportional to load capacitance

# Falling Contamination Delay


- Best-case (contamination) delay can be substantially less than propagation delay:

*if top nMOS is last to turn on:*

*i.e. ABC goes from (011) to (111)*

 

$$t_{cdf} = (9 + 5h)RC$$


 


*compare to:  $t_{pdf} = (12 + 5h)RC$*

# Rising Contamination Delay

Fastest response if all pMOS turn on simultaneously:

i.e. ABC goes from (111) to (000)

  


$$t_{cdr} = \left(3 + \frac{5}{3}h\right)RC$$

compare to:  $t_{pdr} = (15 + 5h)RC$


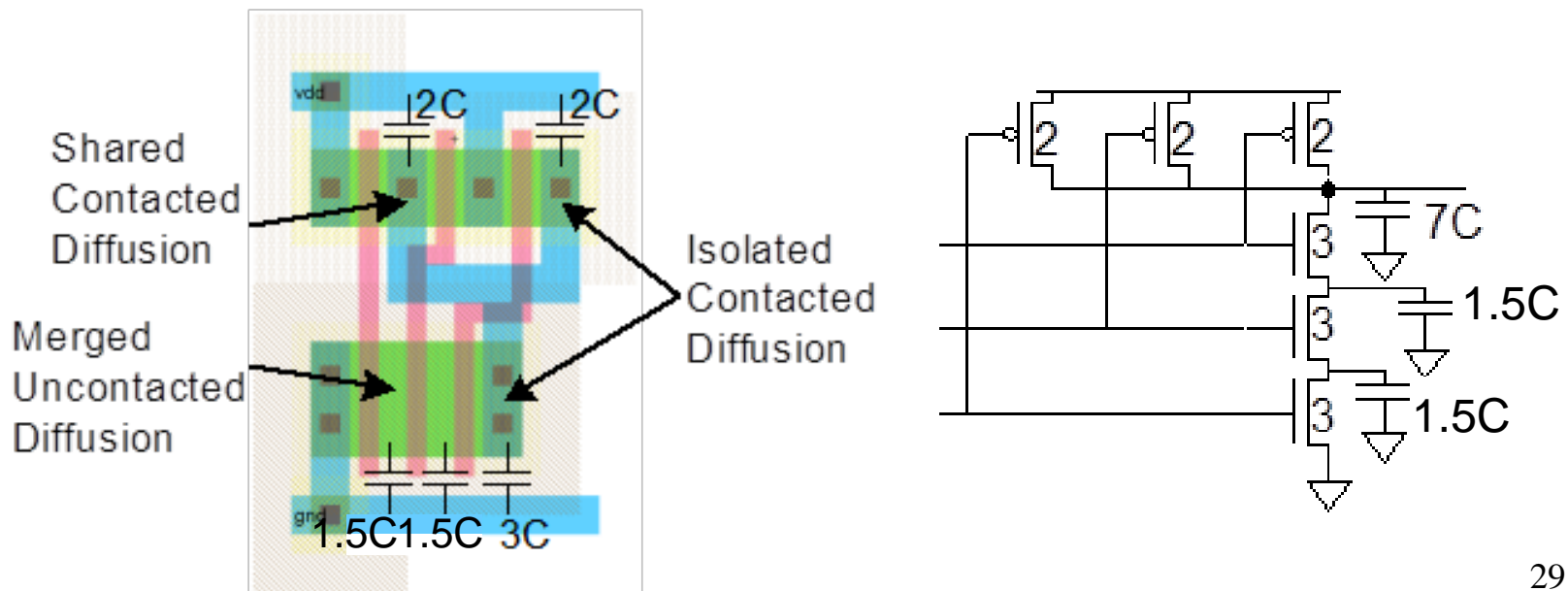
# Diffusion Capacitance

- We assumed contacted diffusion on every s / d.
  - but shared on series nMOS chain
- Good layout minimizes diffusion area
- Good NAND3 layout shares one diffusion contact
  - Reduces output capacitance by  $2C$
- Merged un-contacted diffusion also helps



# Layout Comparison

- Which layout is better?

  

# Example: Gate delays

For the gate  $Y = \overline{A.B + C.D}$

- a) Draw the schematic
- b) Size the transistors to give pullup and pulldown strength equal to unit size inverter
- c) Annotate with effective R of each transistor and C of each node
- d) Calculate worst case rising & falling propagation delay while driving  $h$  similar gates
- e) Calculate best case rising & falling contamination delay while driving  $h$  similar gates