

Lecture 13

CMOS Power Dissipation





Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology

Hoboken, NJ 07030

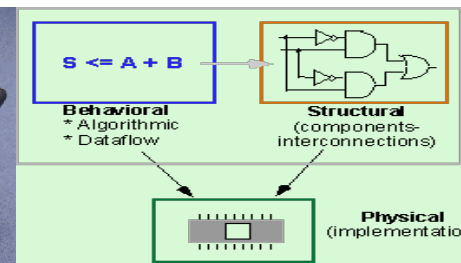   Adapted from Digital Integrated Circuits: A Design Perspective, Rabaey *et. al.*, 2003
and Lecture Notes, David Mahoney Harris CMOS VLSI Design




CMOS – a Low Power Technology

- CMOS developed in 1970's as a low power technology
 - (almost) no DC current when gate is not switching
 - no static power dissipation
- CMOS replaces NMOS in 1980's as dominant digital technology
 - NMOS designs dissipated about $200\mu\text{W}/\text{gate}$
 - Power dissipation no longer an issue!
- CMOS process technology evolves to provide:
 - more transistors per chip (Moore's Law)
 - faster switching speed (few MHz \Rightarrow hundreds of MHz)
- 1992 DEC announces Alpha 64-bit microprocessor
 - triumph of high speed CMOS digital design
 - first 200MHz processor, 1.7M transistors
 - 30W power dissipation
 - Power dissipation is once again an issue!

Why Power Matters: Package & System Cooling

 
- Need to remove heat from high performance chips
 - max. operating temperature silicon transistors: 150 – 200 °C
- Chip on PC board can dissipate 2-3 watts
- With suitable heatsink, maybe 10 watts
- With forced-air cooling (fans), up to 150W



- With sophisticated liquid cooling, maybe 1000W

Why Power Matters: Battery Size & Weight

 - Today, we see more hand-held battery operated devices
- Unlike CMOS technology, battery technology has seen only modest improvements over last few decades



“Mobile Computing Environment”,
Paradiso et. al. Pervasive
Computing, IEEE 2005

- Expected battery lifetime increase over the next 5 years:
30 to 40%

Why Power Matters: Power Distribution

- Power Supply and Ground design
 - If $V_{DD}=1.0V$, a 100W chip draws 100 amps!
 - Many package pins required
 - Virtex-6 1924-pin package:
 - 220 power and 484 GND pins
 - On-chip wiring distribute this current
 - Electro-migration issues
- On-chip noise and system reliability
 - Large currents switched through package and PCB inductance
- Environmental Concerns
 - Computers and consumer electronics account for 15% of residential energy consumption



Back to Basics: Power & Energy

- Power is drawn from a voltage source attached to the V_{DD} and GND pins of a chip.
- Instantaneous Power: $P(t) = I(t)V(t)$ (watts)
- Energy: $E = \int_0^T P(t)dt$ (joules)
- Average Power: $P_{\text{avg}} = \frac{E}{T} = \frac{1}{T} \int_0^T P(t)dt$


Back to Basics: Power in Circuit Elements

- Power Supply:



$$P_{VDD}(t) = I_{DD}(t)V_{DD}$$

- Resistor

 


$$P_R(t) = \frac{V_R^2(t)}{R} = I_R^2(t)R$$

- Capacitor



Capacitors don't
dissipate power!

– but they do store energy:

 

$$E_C = \int_0^{\infty} I(t)V(t) dt = \int_0^{\infty} C \frac{dV}{dt} V(t) dt$$

$$= C \int_0^{V_C} V(t) dV = \frac{1}{2} CV_C^2$$

Power Dissipation in CMOS

- $P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}}$
- Dynamic power: $P_{\text{dynamic}} = P_{\text{switching}} + P_{\text{shortcircuit}}$
 - Switching load capacitances
 - Short-circuit current
- Static power: $P_{\text{static}} = (I_{\text{sub}} + I_{\text{gate}} + I_{\text{junct}} + I_{\text{contention}})V_{\text{DD}}$
 - Subthreshold leakage
 - Gate leakage
 - Junction leakage
 - Contention current

Dynamic Power: Charging a Capacitor

- When the gate output rises from GND to V_{DD} :

- Energy stored in capacitor is

$$E_C = \frac{1}{2} C_L V_{DD}^2$$

- But energy drawn from the supply is


$$E_{V_{DD}} = \int_0^{\infty} I(t) V_{DD} dt = \int_0^{\infty} C_L \frac{dV}{dt} V_{DD} dt$$

$$= C_L V_{DD} \int_0^{V_{DD}} dV = C_L V_{DD}^2 \quad \textit{independent of size of transistors!}$$

- Half the energy from V_{DD} is dissipated in the pMOS transistor as heat, other half stored in capacitor


- When the gate output falls from V_{DD} to GND

 - Stored energy in capacitor is dumped to GND
- Dissipated as heat in the nMOS transistor



Switching Waveforms

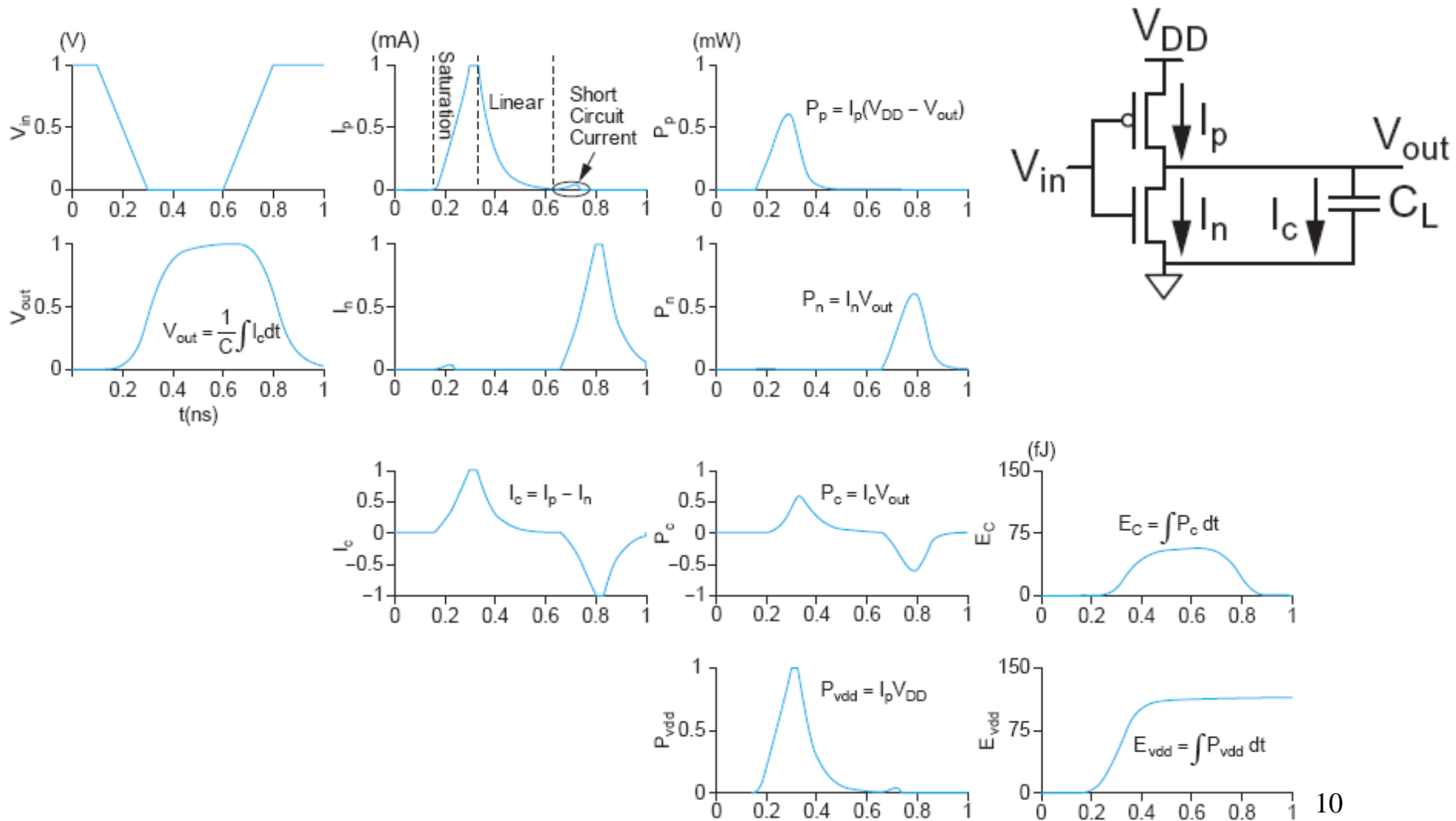- Example: $V_{DD} = 1.0 \text{ V}$, $C_L = 150 \text{ fF}$, $f = 1 \text{ GHz}$



Switching Waveforms

$$P_{switching} = \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt$$


$$= \frac{V_{DD}}{T} \int_0^T i_{DD}(t) dt$$

$$= \frac{V_{DD}}{T} \times \left[\begin{array}{l} \text{total charge drawn} \\ \text{from power supply} \\ \text{in time } T \end{array} \right]$$

$$= \frac{V_{DD}}{T} \times [T f_{sw} C V_{DD}]$$

$$P_{switching} = C \cdot V_{DD}^2 \cdot f_{sw}$$

 Note: $P_{switching}$ is independent of drive strength of the nMOS and pMOS transistors



Activity Factor

- Suppose the system clock frequency = f
- Most gates do not switch every clock cycle
- Let $f_{sw} = \alpha f$, where α = activity factor
 - $\alpha = P_{0 \rightarrow 1}$: probability that a signal switches from 0 to 1 in any clock cycle
 - If the signal is the system clock, $\alpha = 1$
 - If the signal switches once per cycle, $\alpha = 0.5$
 - If the signal is random (clocked) data, $\alpha = 0.25$
 - Static CMOS logic has (empirically) $\alpha \approx 0.1$
- Dynamic power of a circuit: (summing over all the nodes in the circuit)

$$P_{switching} = V_{DD}^2 \cdot f \cdot \sum_i \alpha_i \cdot C_i$$

Dynamic Power Example

- 1 billion transistor chip
 - 50M logic transistors
 - Average width: 12λ
 - Activity factor = 0.1
 - 950M memory transistors
 - Average width: 4λ
 - Activity factor = 0.02
 - 65 nm, 1.0V process ($\lambda = 25\text{nm}$)
 - $C = 1 \text{ fF}/\mu\text{m}$ (gate) + $0.8 \text{ fF}/\mu\text{m}$ (diffusion)
- Estimate dynamic power consumption @ 1 GHz.
Neglect wire capacitance and short-circuit current.


Reducing Switching Power

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$

- So try to minimize:
 - Activity factor
 - Capacitance
 - Supply voltage
 - Frequency


Activity Factor Estimation

 - Let $P_i =$ probability (node $i = 1$)
and $\bar{P}_i = (1 - P_i) =$ probability (node $i = 0$)
- $\alpha_i =$ prob. that node i makes a transition from 0 to 1, so
- $\alpha_i = \bar{P}_i \cdot P_i = (1 - P_i) \cdot P_i$




Activity Factor Estimation

 - For random data, $\alpha = 0.5 \cdot 0.5 = 0.25$



- Data is often not completely random
 - e.g. upper 9 bits of 16-bit word representing somebody's age
- Data propagating through ANDs and ORs has lower activity factor

Example: Switching Probability of NOR2

 

- For NOR2, $P_Y = \bar{P}_A \cdot \bar{P}_B$
- $\bar{P}_Y = (1 - P_Y) = (1 - \bar{P}_A \cdot \bar{P}_B)$
- $\alpha_Y = P_Y \cdot \bar{P}_Y$
 $= (\bar{P}_A \cdot \bar{P}_B) \cdot (1 - \bar{P}_A \cdot \bar{P}_B)$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

- If $P_A = P_B = 0.5$, $P_Y = 0.25$, $\alpha_Y = 3/16 \approx 0.19$




Switching Probabilities (Static Gates)

Gate	P_Y
AND2	$P_A P_B$
AND3	$P_A P_B P_C$
OR2	$1 - \bar{P}_A \bar{P}_B$
NAND2	$1 - P_A P_B$
NOR2	$\bar{P}_A \bar{P}_B$
XOR2	$P_A \bar{P}_B + \bar{P}_A P_B$

- Remember $\alpha_Y = \bar{P}_Y \cdot P_Y$

Example: 4-input AND gate

- Assume all inputs have $P=0.5$

   



- Which has the lowest power?

Number of Stages vs. Power

- Power depends on activity and capacitance at each node
- Generally fewer stages usually mean less power
- Compare this to delay
 - frequently add stages to improve delay
- Tradeoff between speed and power

Beware of Glitches!

  - Extra transitions caused by finite propagation delay




*Suppose input changes
from ABCD = "1101" to "0111" ?*

*Glitching occurs whenever a node
makes more transitions than
necessary to reach its final value*

*Glitching can raise the activity
factor of a gate to greater than 1!*


Clock Gating

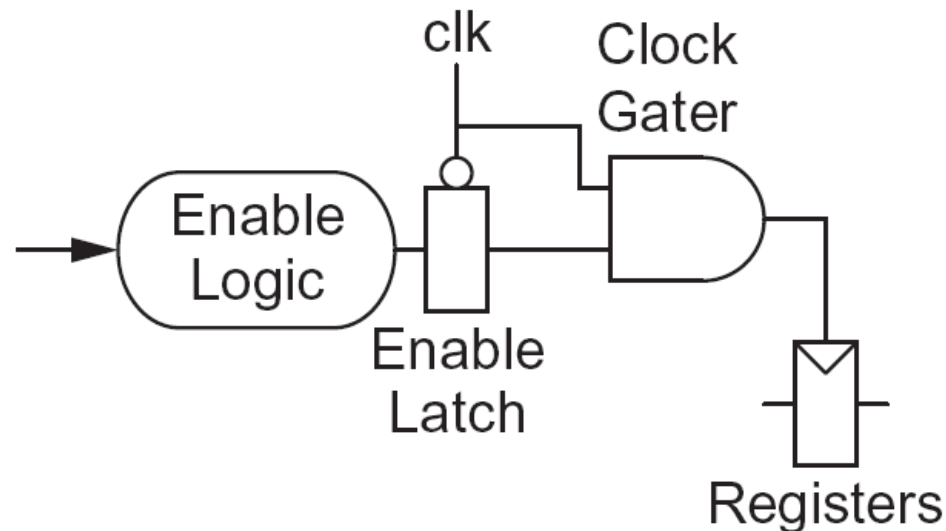- Another way to reduce the activity is to turn off the clock to registers in unused blocks
 - Saves clock activity ($\alpha = 1$)
 - Eliminates all switching activity in the block
 - Requires determining if block will be used



Capacitance

- Extra capacitance slows response and increases power
 - Always try to reduce parasitic and wiring capacitance
 - Good floorplanning to keep high activity communicating gates close to each other
 - Drive long wires with inverters or buffers rather than complex gates
- Gate sizing and number of stages
 - Designing network for minimum delay will usually result in a high-power network.
 - Small increase in delay (e.g. by reducing the # of stages) can give large reduction in power
 - There are no closed form solutions to determine gate sizes that minimize power under a delay constraint.
 - Can be solved numerically

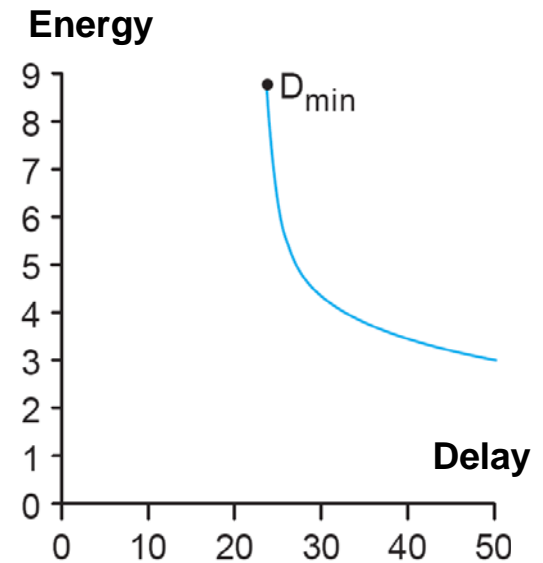

Voltage


- Power dissipated in gate is $P_{av} = \alpha \cdot f \cdot C_L \cdot V_{DD}^2$
- Energy per switching event* is $E_s = P_{av} / (2 \cdot \alpha \cdot f) = (C_L \cdot V_{DD}^2) / 2$
 - Power & Energy can be significantly reduced by decreasing V_{DD}
- *But* delay of gate is $D = (C_L \cdot \Delta V) / I$
$$\approx (C_L \cdot V_{DD}) / [(\beta/2) \cdot (V_{DD} - V_t)^2]$$
 - Decreasing V_{DD} increases delay
- Circuit can be made (almost) arbitrarily low power at the expense of performance – not very useful

* switching event is defined as a transition from $0 \rightarrow 1$ or $1 \rightarrow 0$

Energy-Delay Product

- Introduce metric **energy-delay product (EDP)**
= (energy per switching event) X (gate delay)
 
$$EDP = E_S \cdot D = \frac{k \cdot C_L^2 \cdot V_{DD}^3}{(V_{DD} - V_t)^2}$$



- Minimum EDP at $V_{DD} = 3 \cdot V_t$ (for long channel process)


Frequency

- Suppose we can do a task in T sec. on one processor
- Can we do it in $T/2$ sec. on two processors?
 - if application has sufficient intrinsic parallelism
- How about doing it in T sec. on two processors running at half clock frequency?

$$\begin{array}{|c|} \hline \text{Proc. at} \\ V \text{ volts, } f \text{ Hz} \\ = P \text{ watts} \\ \hline \end{array} \quad \equiv \quad \begin{array}{|c|} \hline \text{Proc. at} \\ V \text{ volts, } f/2 \text{ Hz} \\ = P/2 \text{ watts} \\ \hline \end{array} \quad + \quad \begin{array}{|c|} \hline \text{Proc. at} \\ V \text{ volts, } f/2 \text{ Hz} \\ = P/2 \text{ watts} \\ \hline \end{array}$$

- This gives no net power savings.
- But $speed \propto (V_{DD} - V_T)^2 / V_{DD}$, so if we reduce clock frequency, we can also reduce V_{DD} :

Reduced Frequency & Voltage

 

In this example, reducing speed by factor of 50% allows voltage reduction of ~35%

Proc. at
 V volts, f Hz
 $= P$ watts

\equiv


Proc. at $0.65V$
volts, $f/2$ Hz
 $\approx 0.2 P$ watts

$+$

Proc. at $0.65V$
volts, $f/2$ Hz
 $\approx 0.2 P$ watts

- Parallelism with reduced f and V_{DD} leads to lower power
 - diminishing returns as V_{DD} approaches V_T


Dynamic Power Dissipation Example

 

- A NAND2 gate of size (input capacitance) $12C$ is driving an inverter of size $36C$ which in turn drives a load of $120C$ units of capacitance. Assume the inputs A, B are independent and uniformly distributed. What is the dynamic switching power dissipation of this gate if the gate capacitance C of a unit sized transistor is 0.1fF , V_{DD} is 1.0V and the operating frequency is 1GHz ?

Short-Circuit Power

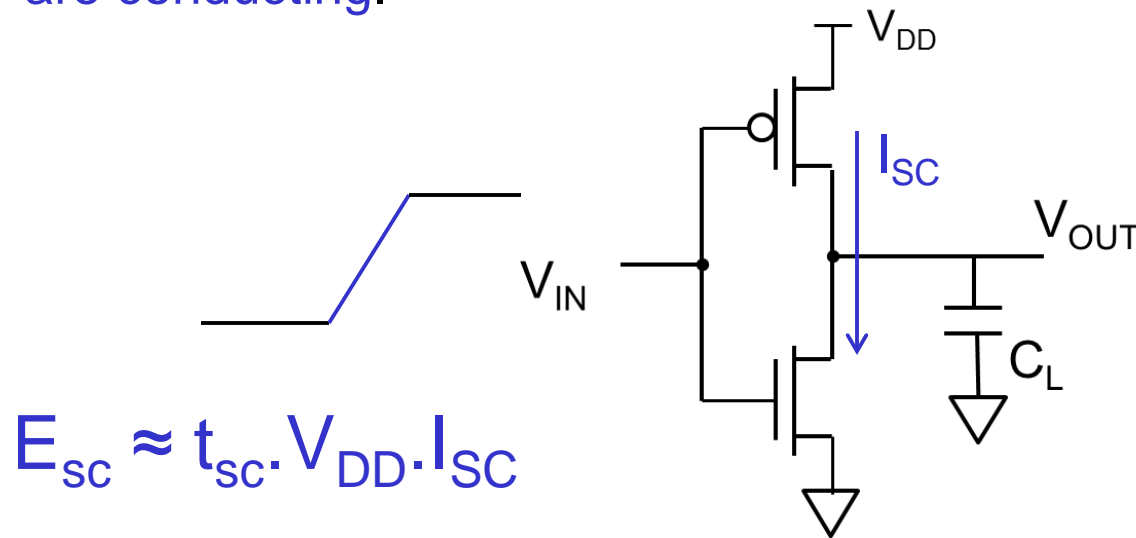
- Finite slope of the input signal
 - sets up a direct current path between V_{DD} and GND for a short period during switching when both the NMOS and PMOS devices are conducting.



- Depends on duration (slope) of the input transition, t_{sc}
- I_{SC} which is determined by
 - saturation current of the P and N transistors
 - depends on sizes, process technology, temperature, etc.
 - ratio between input and output slopes (a function of C_L)


Slope Engineering

Small Capacitive Load

 


- Output fall time significantly shorter than input rise time
- Output “tracks” input as per DC transfer function
- Large I_{SC} when $V_{IN} \approx V_{SW}$

Large Capacitive Load

 

- Output fall time significantly longer than input rise time
- Output transition lags input
- When $V_{IN} = V_{SW}$, V_{dSP} is still very small, so small I_{SC}

Impact of C_L on I_{SC}

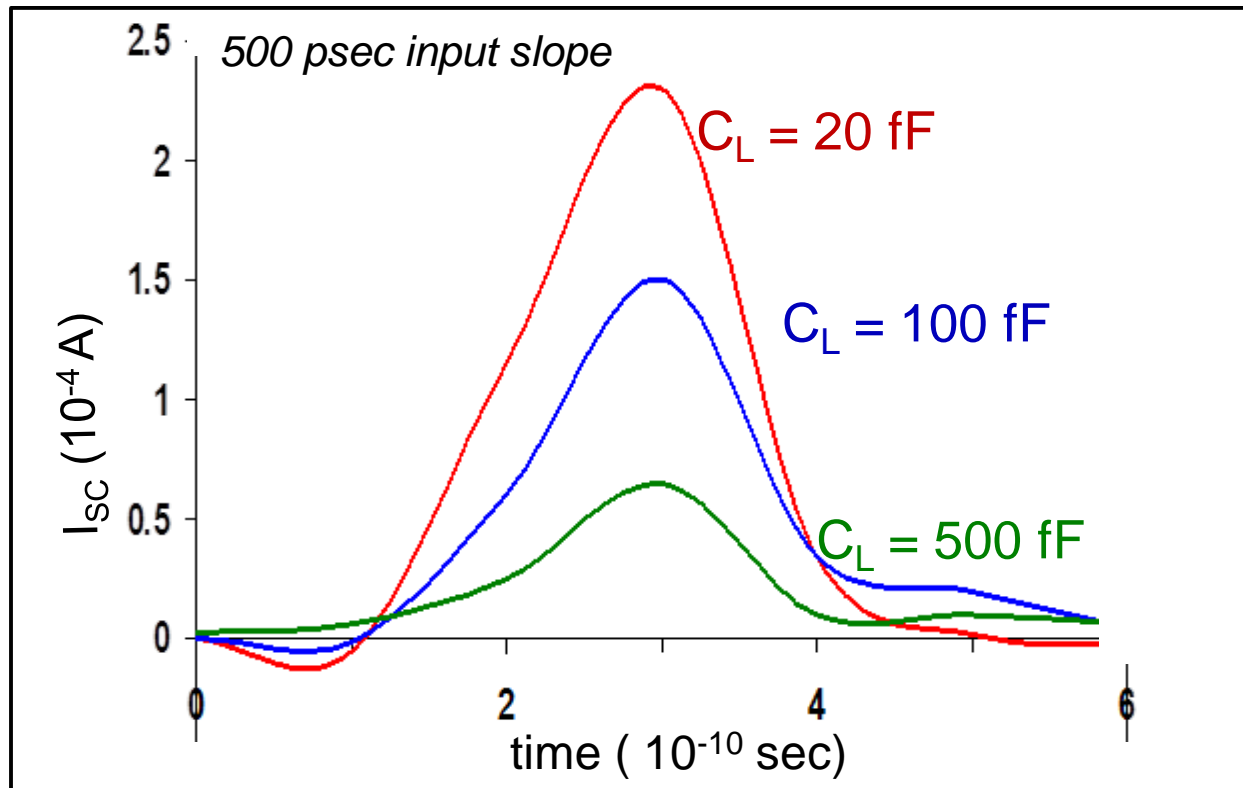


- When C_L is small, I_{SC} is large!
 - Short circuit dissipation is minimized by matching the rise/fall times of the input and output signals - [slope engineering](#).
- Typically less than 10% of dynamic power if rise/fall times are comparable for input and output

Static Power Dissipation

- Static power is consumed even when chip is quiescent
 - i.e. powered up but not running
- Leakage consumes power from current passing through normally off devices
 - sub-threshold current
 - gate leakage current
 - diode junction leakage current

Leakage Sources

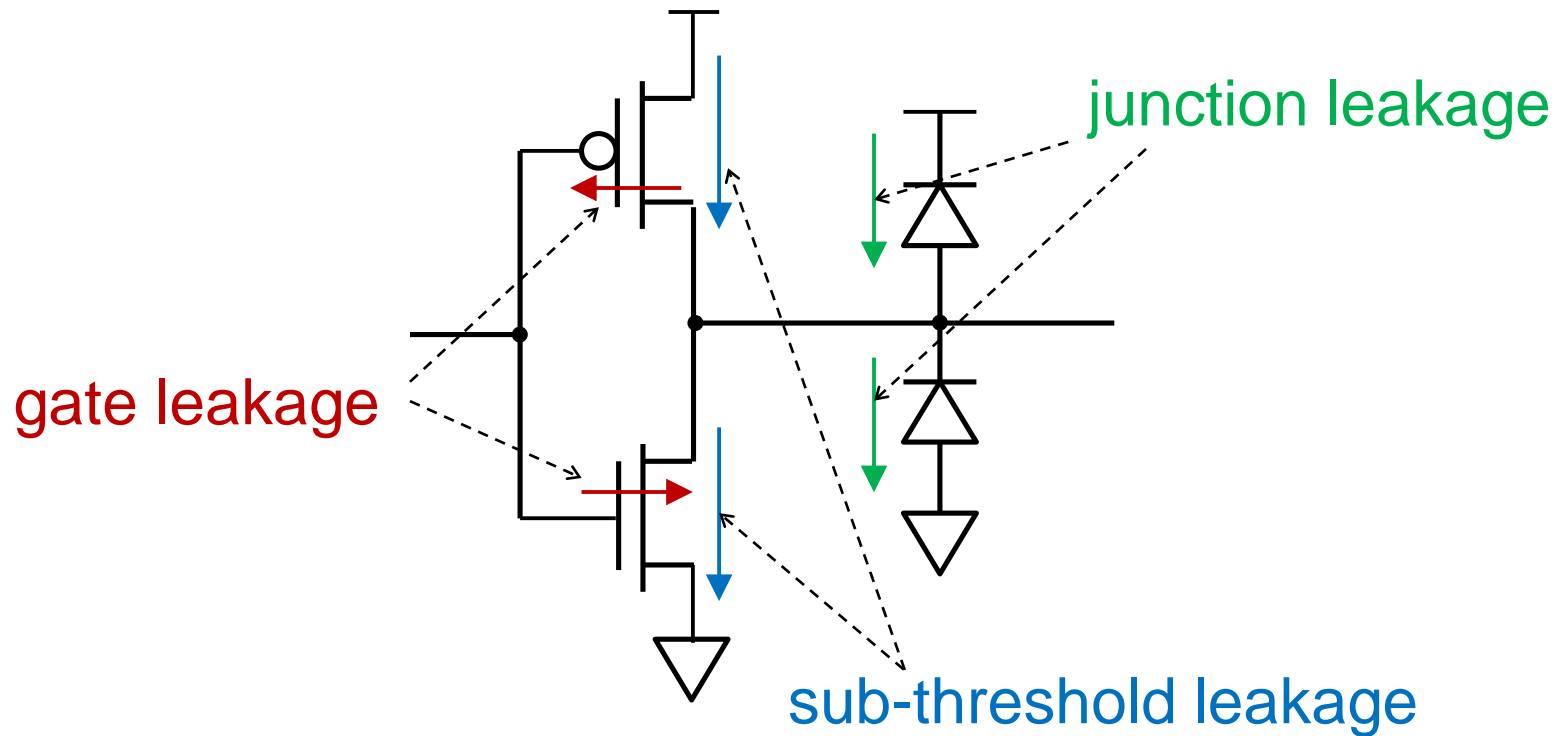


- Leakage currents are very small (per transistor basis)
 - prior to 130 nm, not usually an issue (except in sleep mode of battery operated devices)
 - but when multiplied by hundreds of millions of nanometer devices, can account for as much as 1/3 of active power
- All increase exponentially with temperature

Sub-threshold Leakage

- Shockley model assumes $I_{ds} = 0$ when $V_{gs} \leq V_t$
- But in real transistors, $I_{ds} \approx 100nA \times (W/L)$ when $V_{gs} = V_t$
- For $V_{gs} < V_t$, I_{ds} decreases exponentially with V_{gs}

$$I_{ds} = I_0 10^{\frac{(V_{gs}-V_t)}{S}} \quad \text{where } S \text{ is sub-threshold slope } \approx 100\text{mV/decade}$$

 - In nanometer processes, as we reduce V_{DD} , we also reduce V_t to maintain good *on-current*
 - But reducing V_t increases the *off-current*



Max. “on current”: $I_{sat} = \beta/2m(V_{DD} - V_t)^2$

Min. “off current”: $I_{sub} = I_0 10^{(0-V_t)/S}$

Sub-threshold Leakage

- Tradeoff between “on current” (performance) and “off current” (static power dissipation) as we adjust V_t
- Typical values for *off-current* in 65nm with $V_{DD}=1V$


$$I_{\text{off}} = 100 \text{ nA}/\mu\text{m} \quad @ \quad V_t = 0.3 \text{ V}$$

$$I_{\text{off}} = 10 \text{ nA}/\mu\text{m} \quad @ \quad V_t = 0.4 \text{ V}$$

$$I_{\text{off}} = 1 \text{ nA}/\mu\text{m} \quad @ \quad V_t = 0.5 \text{ V}$$

Stack Effect

- Series OFF transistors have less leakage
 - for N1 to have any leakage, $V_x > 0$
 - so N2 has negative V_{gs}
 - leakage through 2-stack reduces $\sim 10x$
 - leakage through 3-stack reduces further
- Leakage and delay trade off
 - Aim for low leakage in sleep and low delay in active mode
- To reduce leakage:
 - Increase V_t : *multiple* V_t
 - Use low V_t only in speed critical circuits
 - Increase V_s : *stack effect*
 - *Input vector control* in sleep

 


Gate & Junction Leakage

- **Gate leakage** extremely strong function of t_{ox} and V_{gs}
 - Negligible for older processes
 - Approaches sub-threshold leakage at 65 nm
- An order of magnitude less for pMOS than nMOS
- Control gate leakage in the process using $t_{\text{ox}} > 10 \text{ \AA}$
 - High-k gate dielectrics help
 - Some processes provide multiple t_{ox}
 - e.g. thicker oxide for 3.3 V I/O transistors
- **Junction leakage** usually negligible
 - becoming little more significant in nanometer processes
- Control gate & junction leakage in circuits by limiting V_{DD}

Power Gating

- Turn OFF power to blocks when they are idle to save leakage

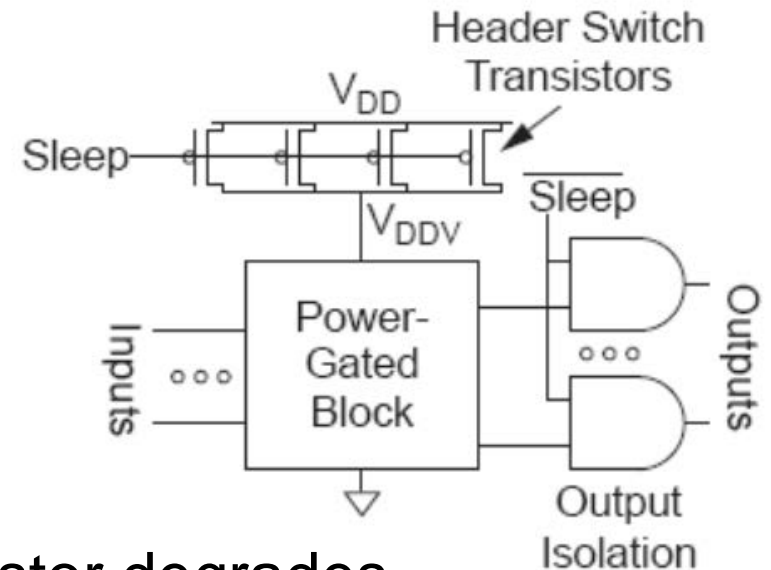- Use virtual V_{DD} (V_{DDV})
- Gate outputs to prevent invalid logic levels to next block



- Voltage drop across sleep transistor degrades performance during normal operation
 - Size the transistor wide enough to minimize impact
- Switching wide sleep transistor costs dynamic power
 - Only justified when circuit sleeps long enough

Voltage & Frequency Control

- Run each block at the lowest possible voltage and frequency that meets performance requirements
- Multiple Voltage Domains
 - Provide separate supplies to different blocks
 - Level converters required when crossing from low to high V_{DD} domains
- Dynamic Voltage Scaling
 - Adjust V_{DD} and f according to workload

