

Lecture 9

CMOS Digital Circuits





Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology

Hoboken, NJ 07030

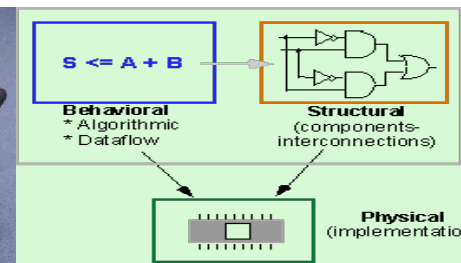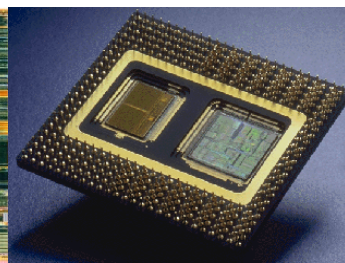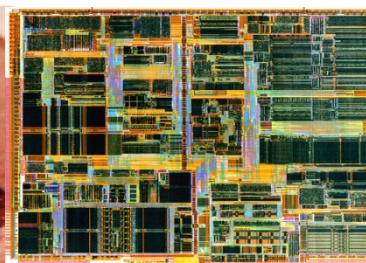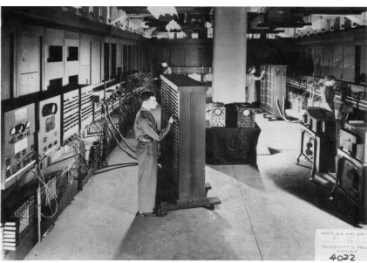Adapted from Modern Semiconductor Devices for Integrated Circuits, Chenming Hu, 2010



CMOS Power Supply Voltages

- $V_{SS} \approx$ negative rail \approx GND ≈ 0 V
- In 1980's, positive rail $V_{DD} = 5$ V
- V_{DD} has decreased in modern processes
 - Smaller transistors require increased gate oxide capacitance C_{ox} to provide necessary current drive
 - achieved through use of thinner gate oxide ~ 2 nm
 - High V_{DD} would break down gate oxide (destructively)
 - Lower V_{DD} also saves power



Process: 0.35 μ \Rightarrow 0.25 μ \Rightarrow 180nm \Rightarrow 130nm \Rightarrow 90nm \Rightarrow 65nm

VDD: 3.3V \Rightarrow 2.5V \Rightarrow 1.8V \Rightarrow 1.5V \Rightarrow 1.2V \Rightarrow 1.0V \Rightarrow ??



- In CMOS digital circuits, conventionally define:
 - GND \equiv logical '0'
 - V_{DD} \equiv logical '1'

CMOS Logic Transistors

NFET or NMOS transistor

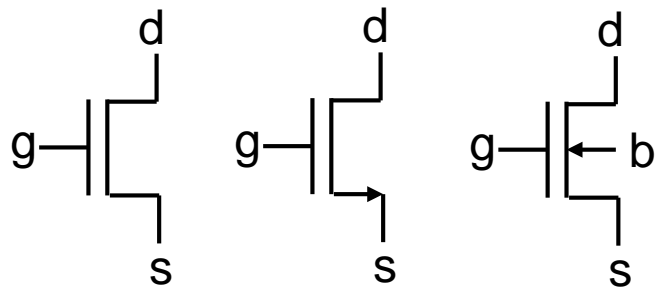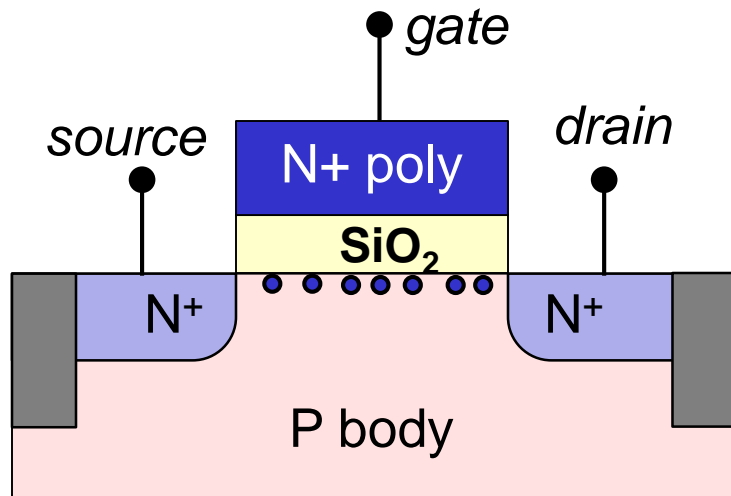

PFET or PMOS transistor

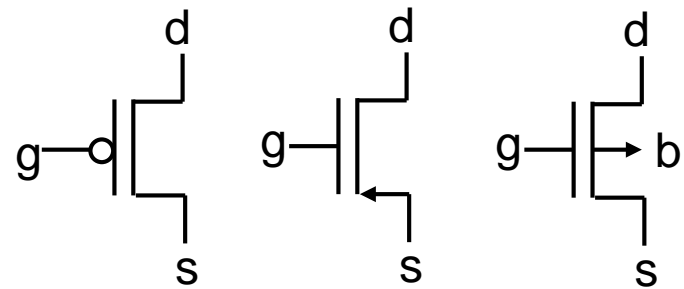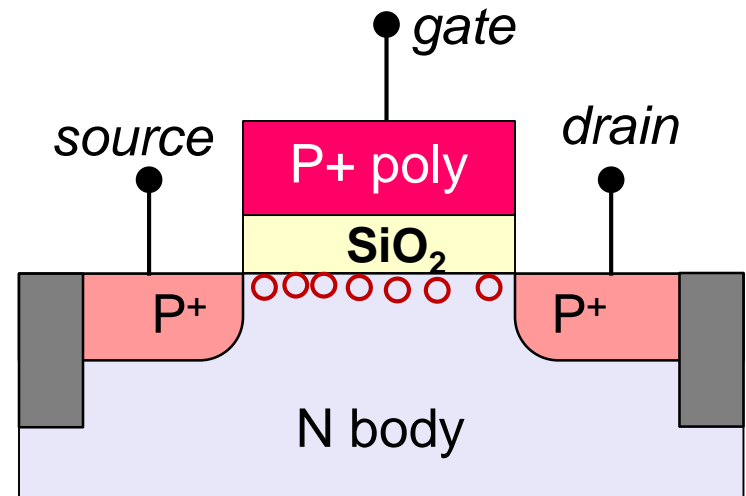


- P body normally connected to most negative voltage (0V, gnd)
- N body normally connected to most positive voltage (V_{DD})
- Both are enhancement devices with $|V_t| \approx 20 \text{ to } 30\% \text{ of } V_{DD}$


Transistors as Switches

- In simplest model, we can view MOS transistors as electrically controlled switches
- Voltage at gate controls path from source to drain


nMOS

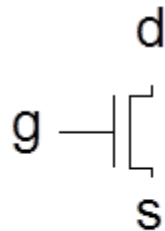




$g = 0$

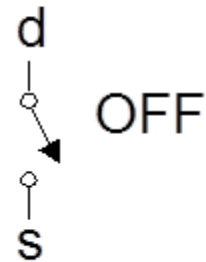

$g = 1$


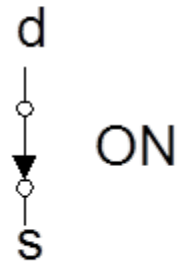


pMOS

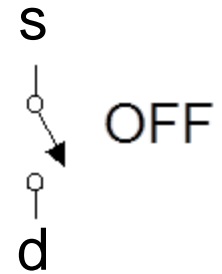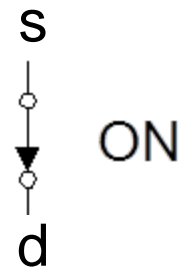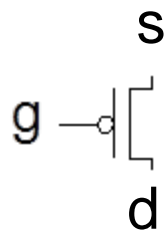



CMOS Inverter

A	Y
0	
1	

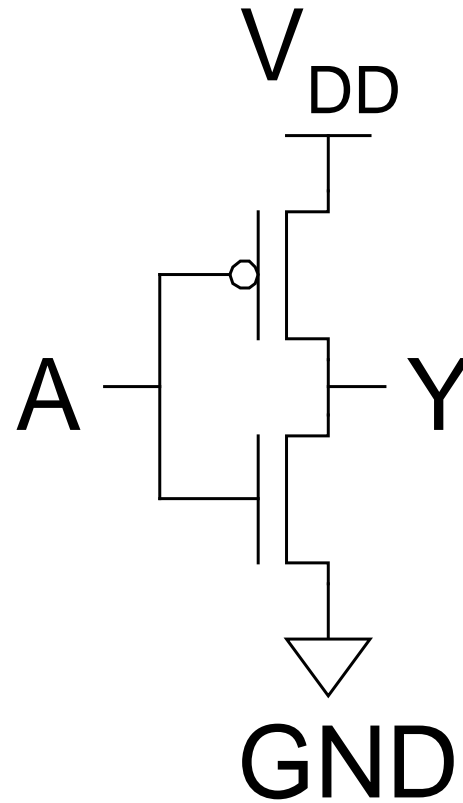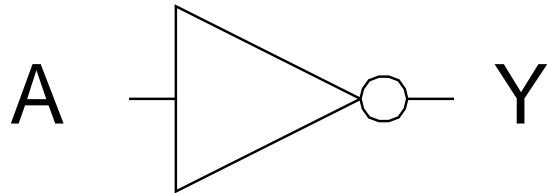



CMOS Inverter

A	Y
0	
1	0

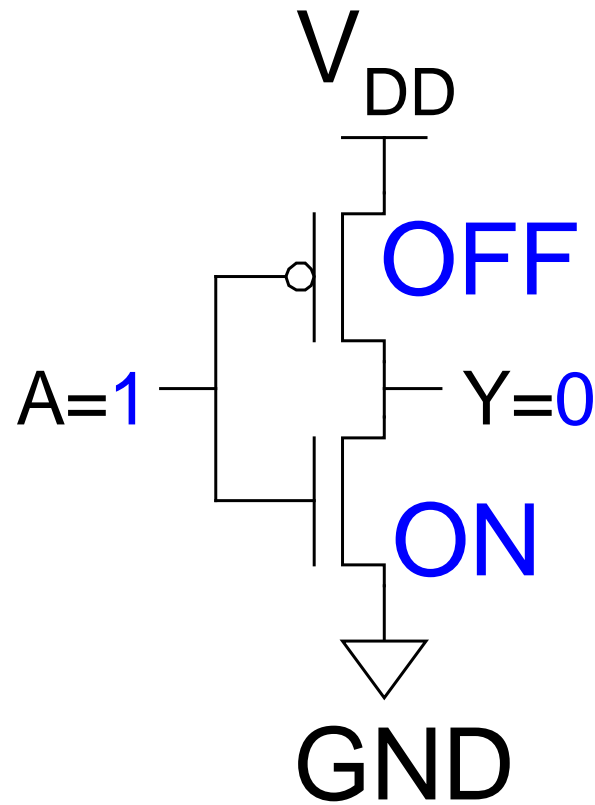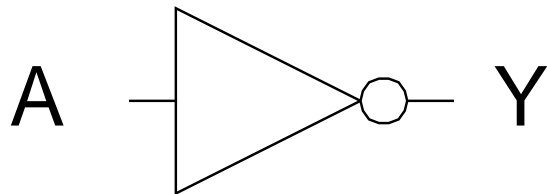


CMOS Inverter

A	Y
0	1
1	0

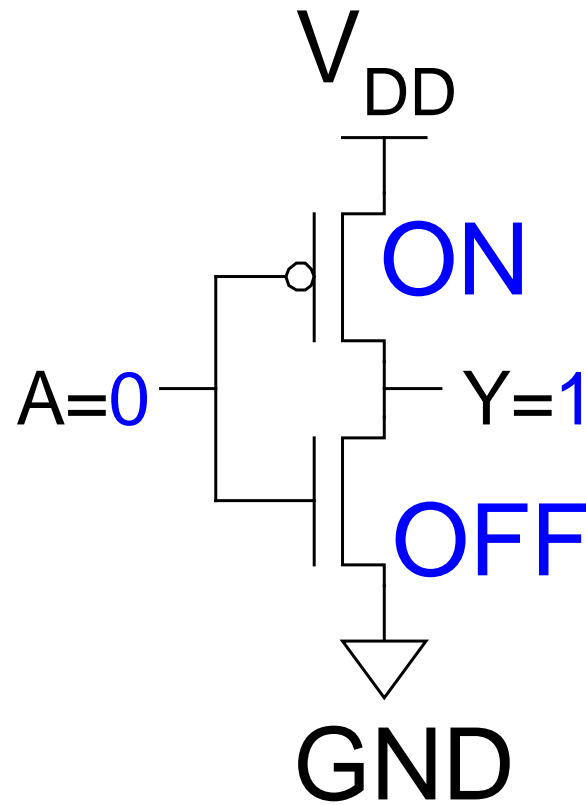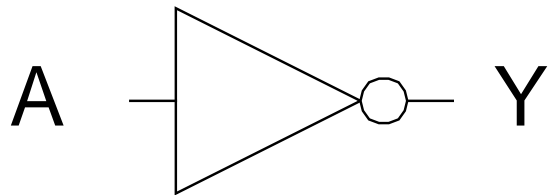


CMOS 2-input NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

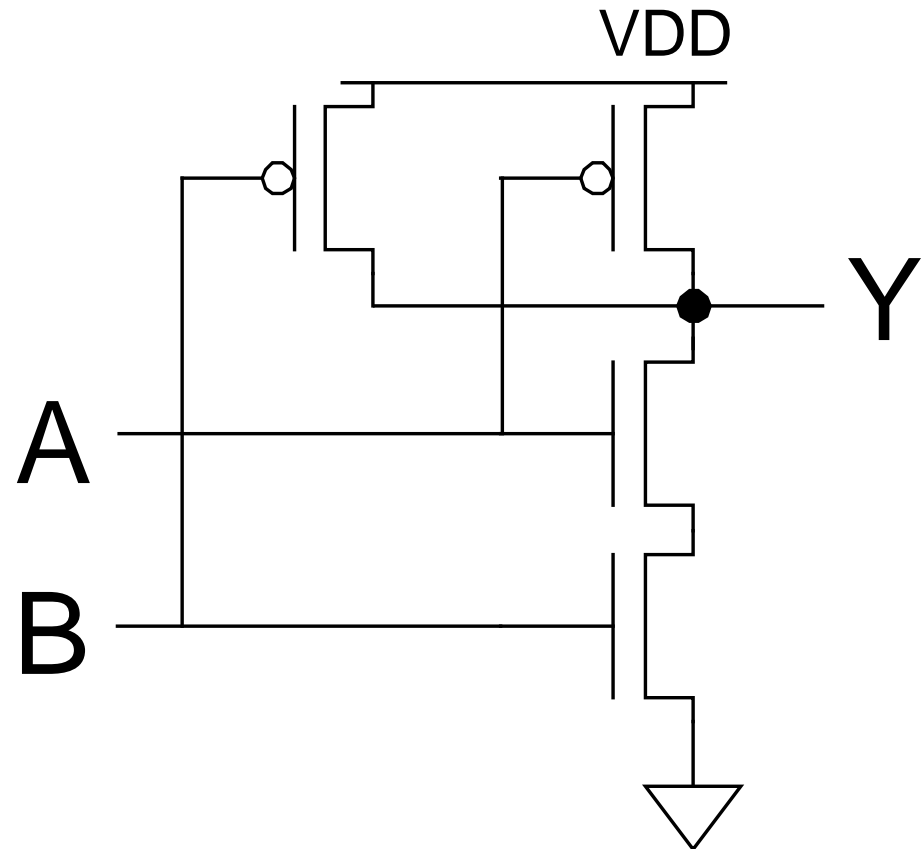


CMOS 2-input NAND Gate

A	B	Y
0	0	1
0	1	
1	0	
1	1	

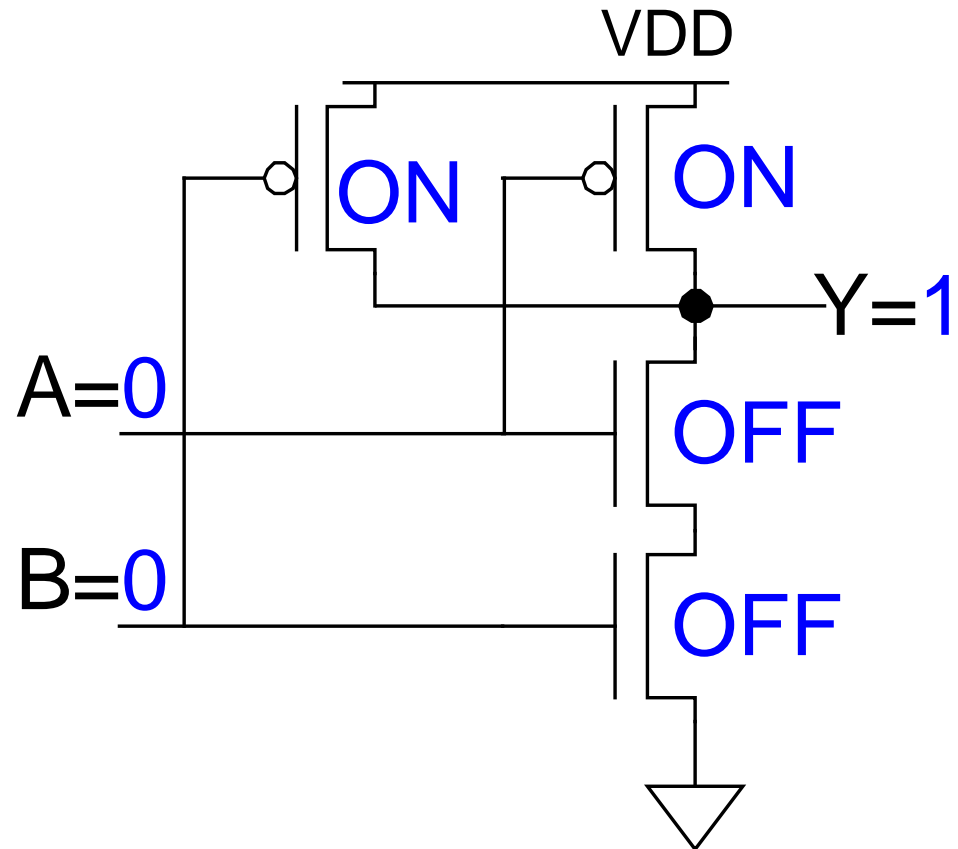


CMOS 2-input NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	
1	1	

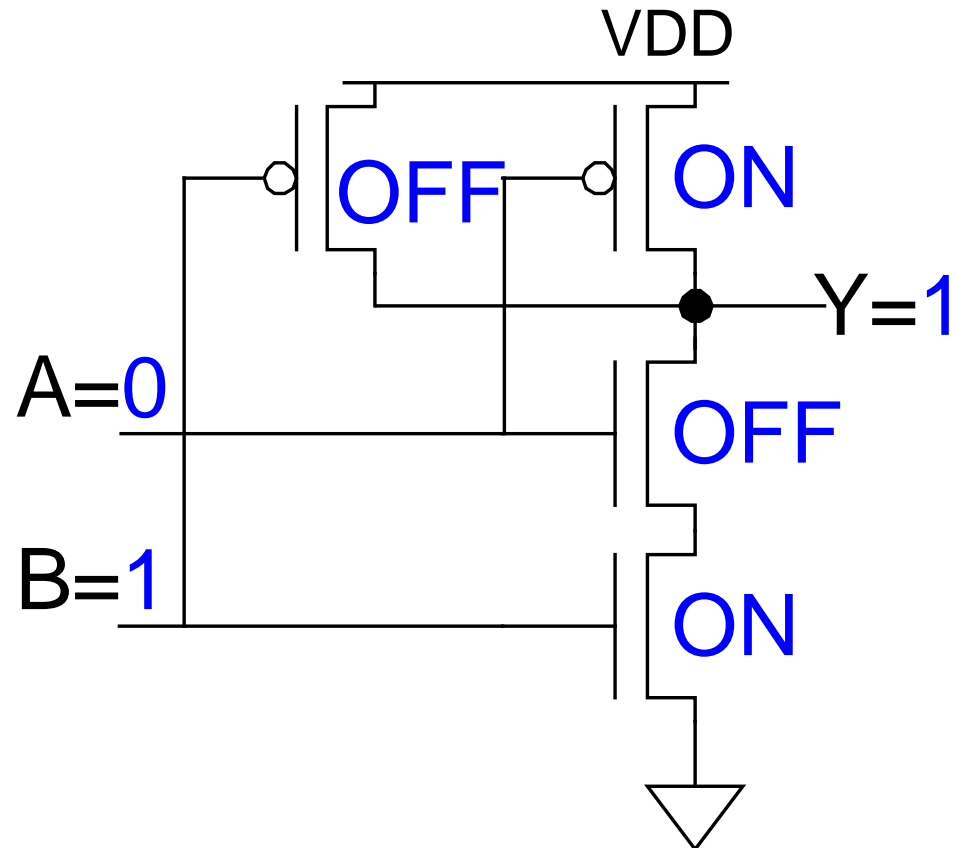




CMOS 2-input NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	

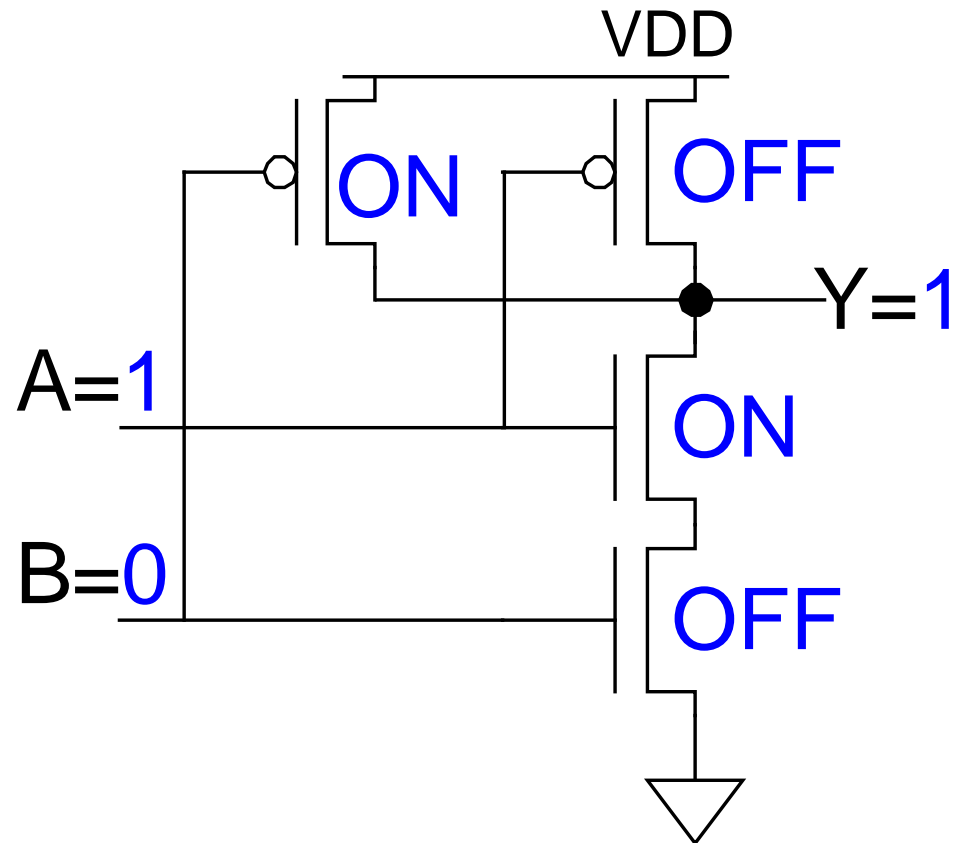




CMOS 2-input NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

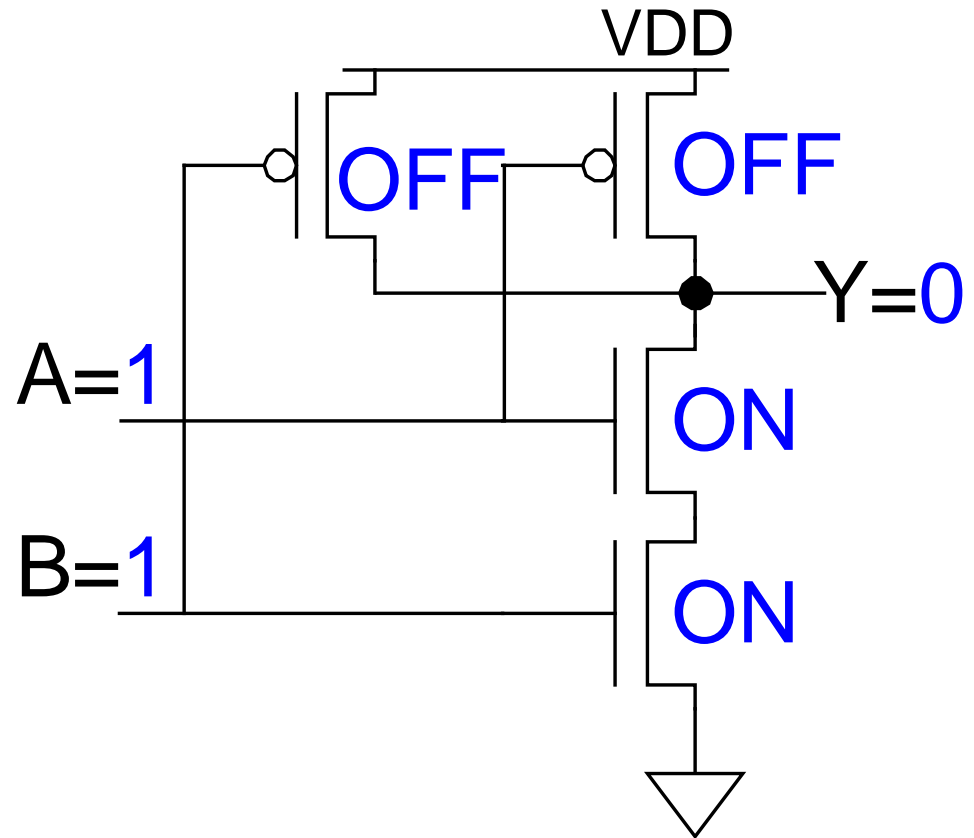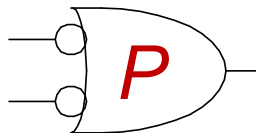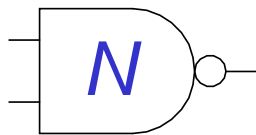


CMOS 2-input NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

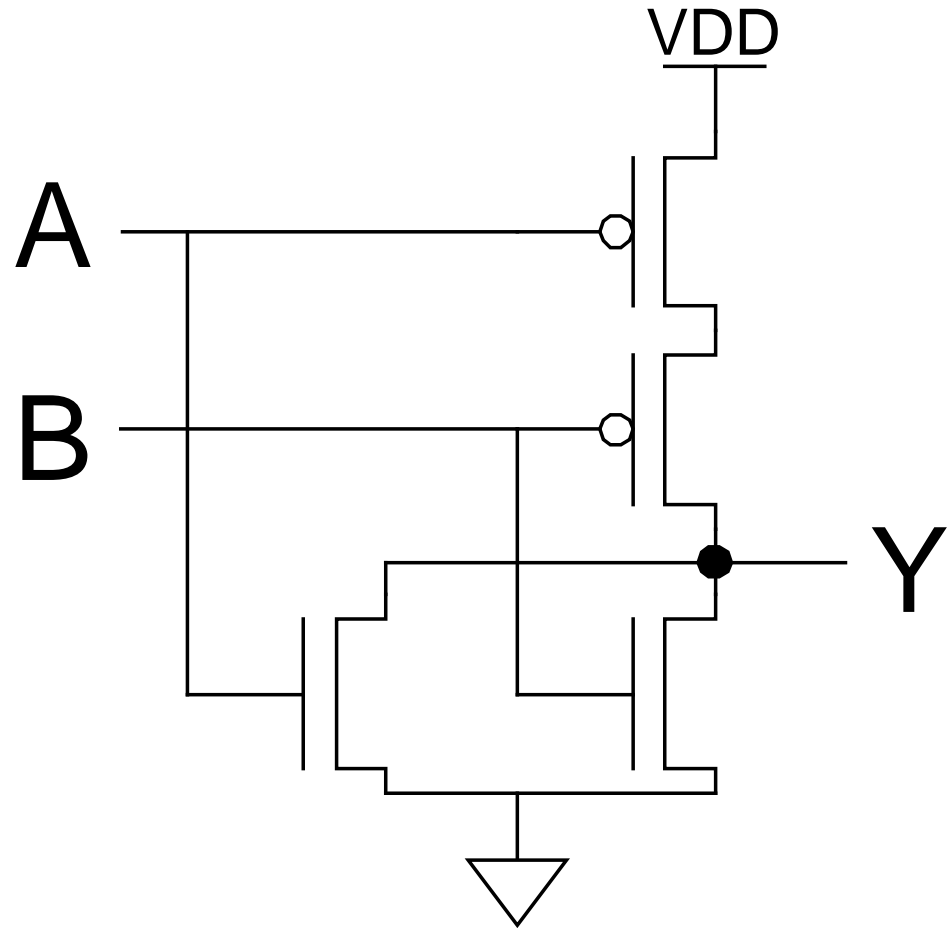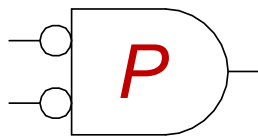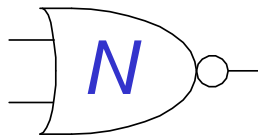


CMOS Gate Design

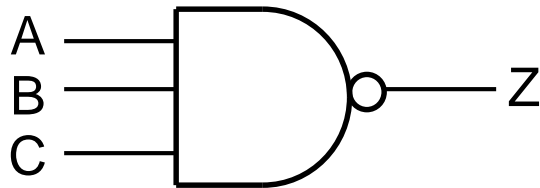- Draw the transistor level schematic of a 3-input CMOS NAND gate:




Complementary CMOS Gates

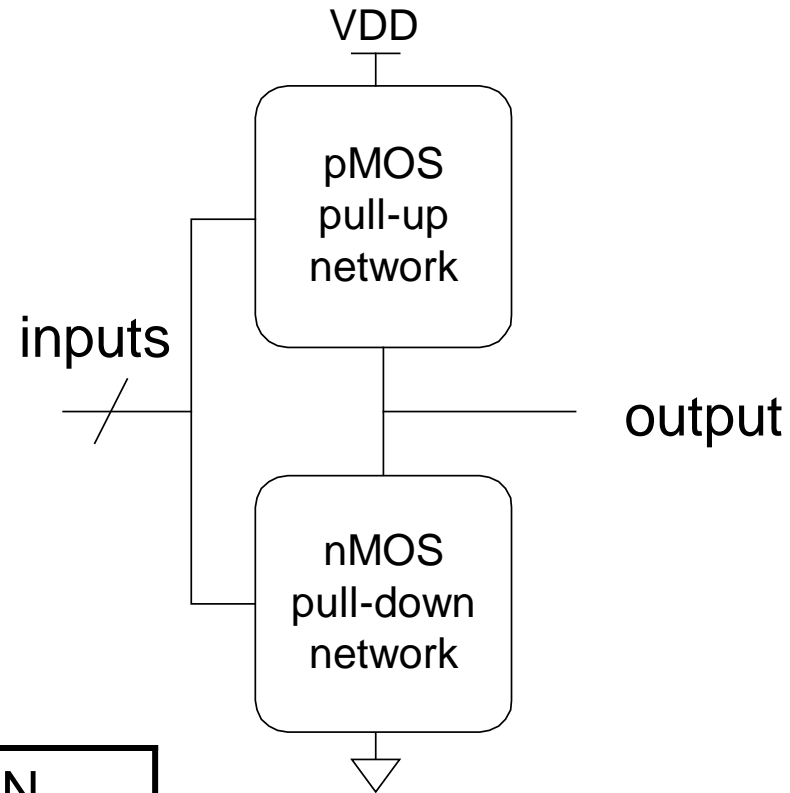- nMOS pull-down network
- pMOS pull-up network
- static combinational CMOS logic



	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)




Series & Parallel Conduction Paths

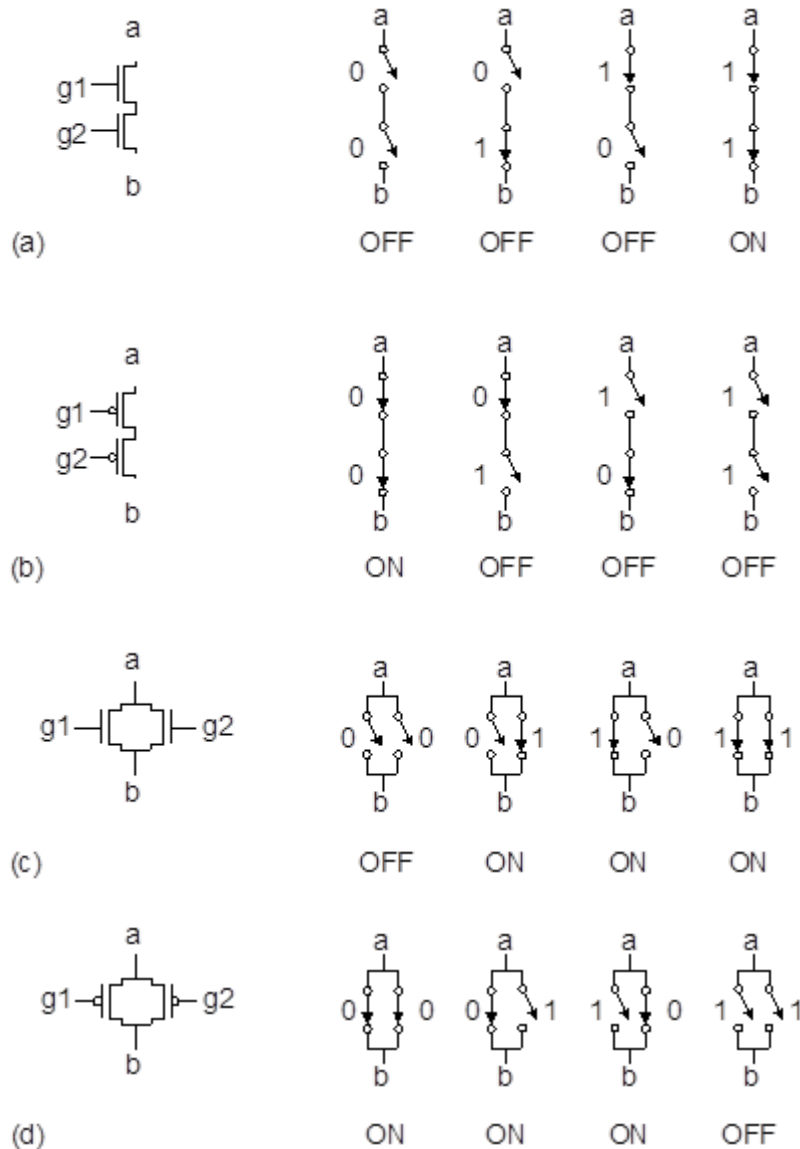

- nMOS: 1 = ON
- pMOS: 0 = ON
- Series: both must be ON
- Parallel: either can be ON
- To ensure that gate is always driven to 0 or 1:
- Pull-up network must be topological complement of pull-down network
 - parallel \Leftrightarrow series
 - series \Leftrightarrow parallel


Compound Gates

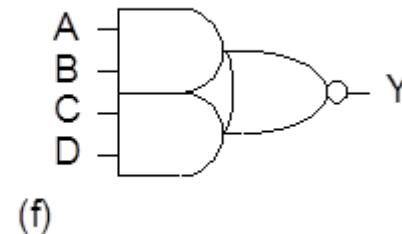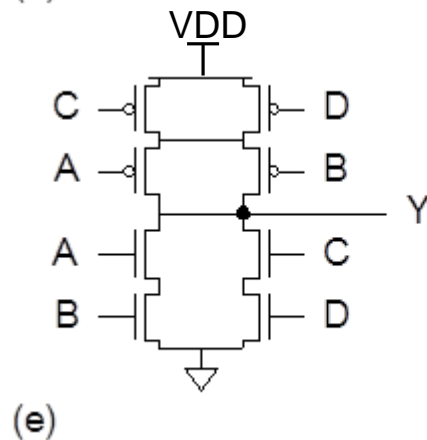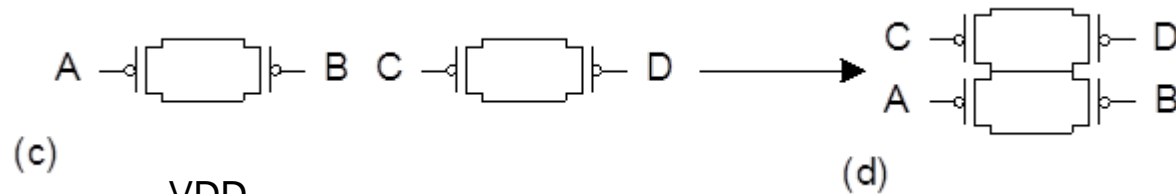- We can generate any **inverting** combinatorial function with a network of series and parallel nMOS transistors and a complementary network of pMOS transistors
- e.g., $Y = \overline{A.B + C.D}$ *and-or-invert gate: AOI22*





Example: O3AI

- $Y = \overline{(A + B + C)}.D$

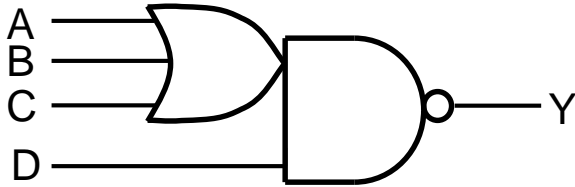



Signal Strength

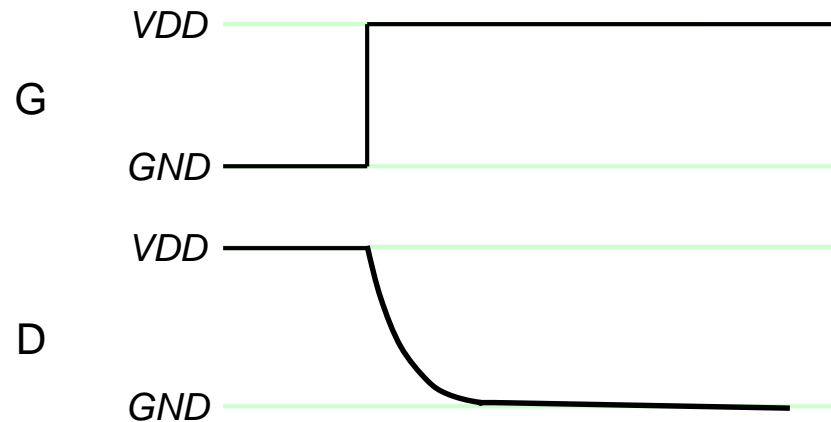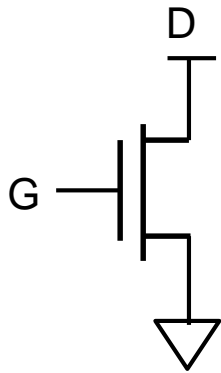- In a complementary gate, nMOS transistors are always used to pull down to GND and pMOS are always used to pull up to V_{DD}




- Once gate goes high, $V_g - V_s = V_{DD} > V_{th}$
- Transistor stays on as drain is pulled all way down to GND
- Could we use an nMOS transistor to pull-up to V_{DD} ?

Pulling up with an nMOS

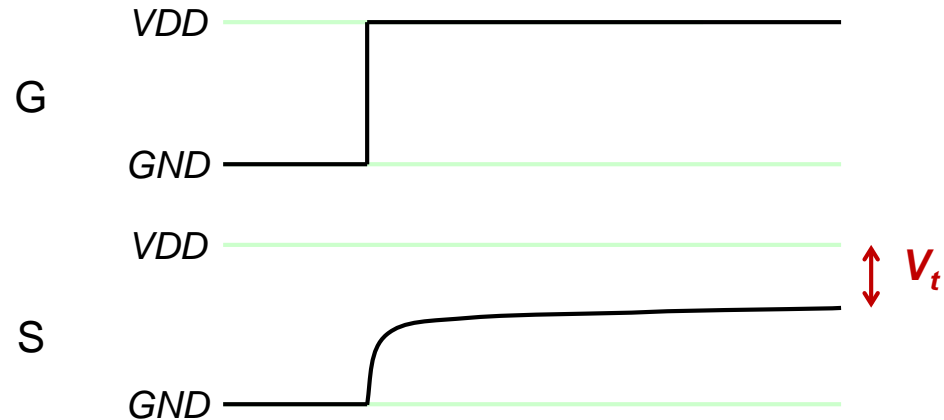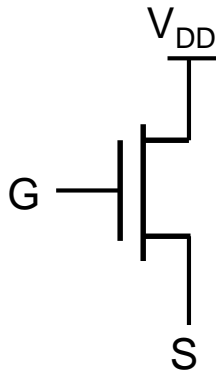


- In this configuration, source voltage is changing
- As $V_g - V_s$ approaches V_{th} , transistor starts to turn off
- Weak conduction leads to degraded final value
 - never reaches V_{DD} . V_s asymptotes towards $V_{DD} - V_t$
- Furthermore, body effect increases V_t when $V_{sb} > 0$
- As a switch, we say nMOS drives (passes) a strong 0 but a degraded or weak 1
 - Similarly pMOS drives a strong 1 but a degraded or weak 0

Degraded Time Constant

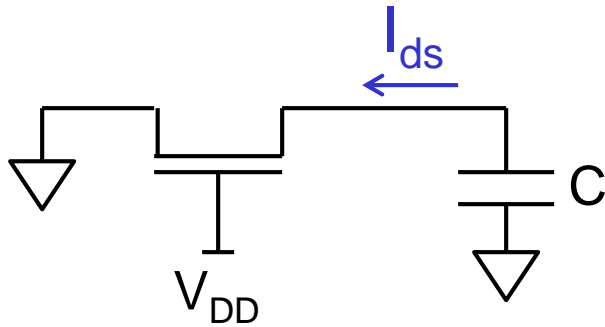


pull-down device is
in linear (mostly):

$$I_{ds} \propto V_d$$

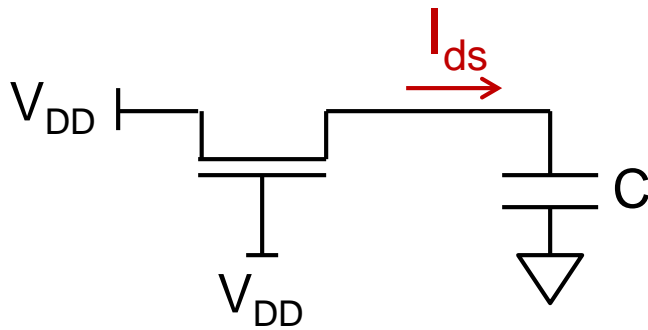

pull-up device
is in saturation:

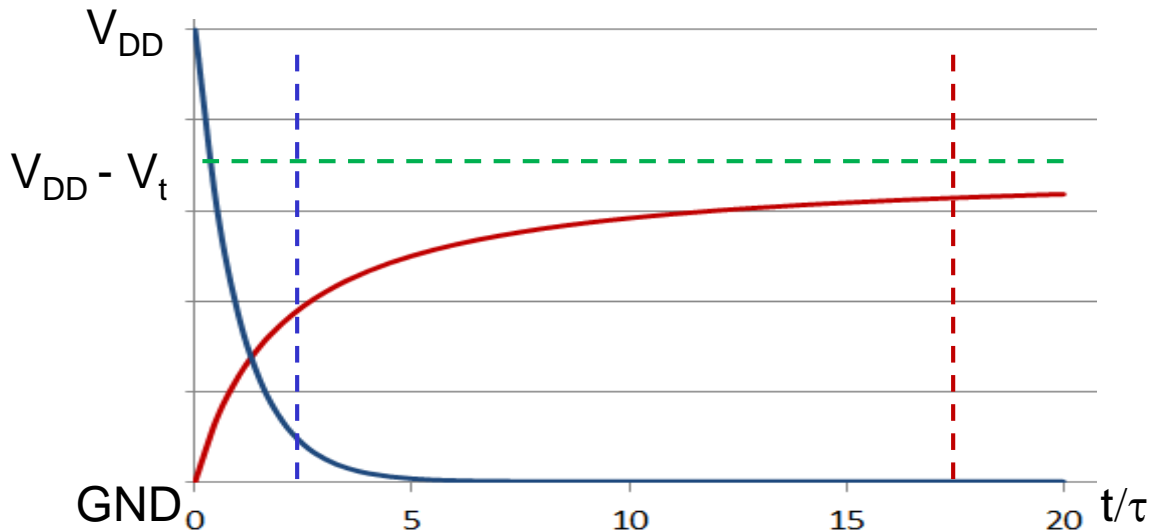
$$I_{ds} \propto ((V_{DD} - V_t) - V_s)^2$$







Pull-up time constant (to
90% final value) can be 6x
pull-down time constant!

Pass Transistors

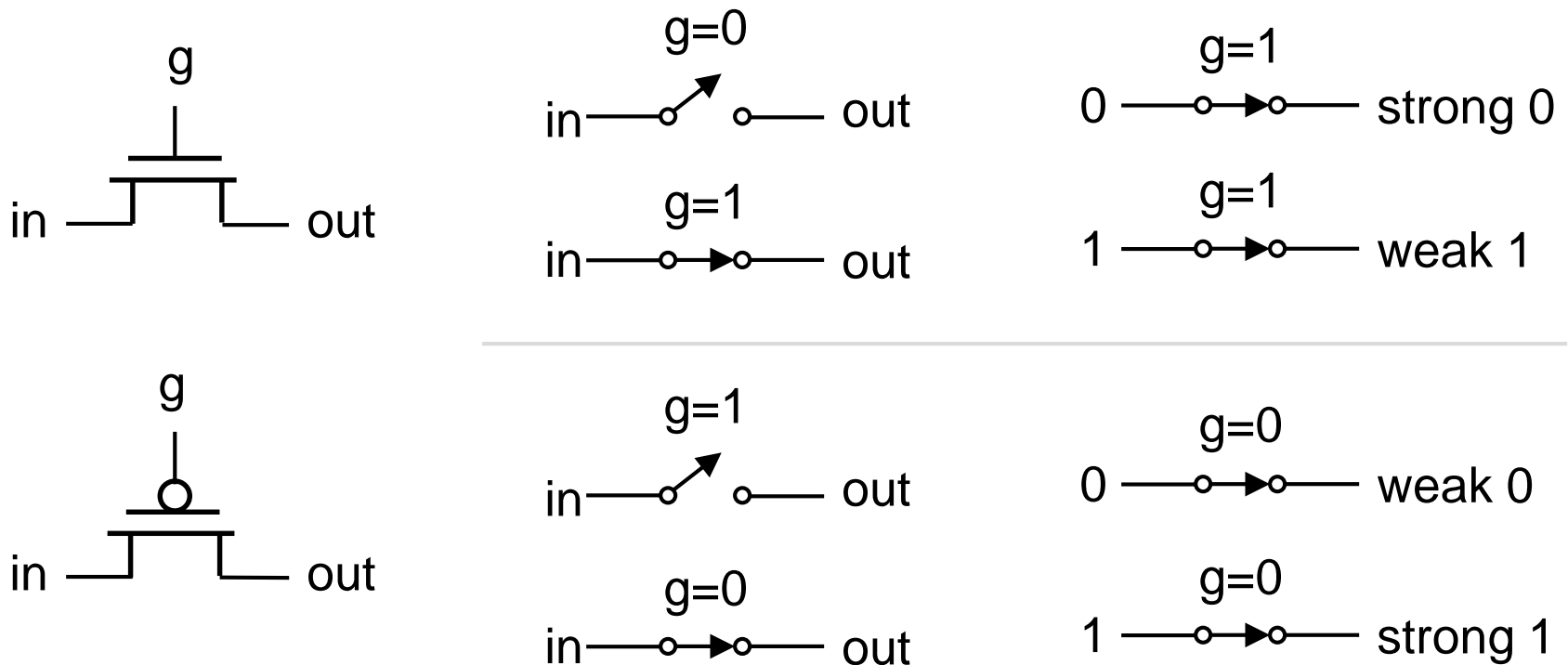- So far, we have used nMOS to switch (drive) output to GND and pMOS to switch (drive) output to VDD in response to various input signals
- We can also use MOS transistors to switch the input signals themselves








Cascaded Pass Transistors

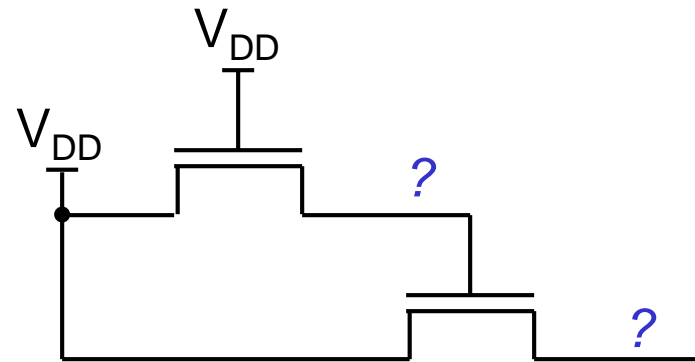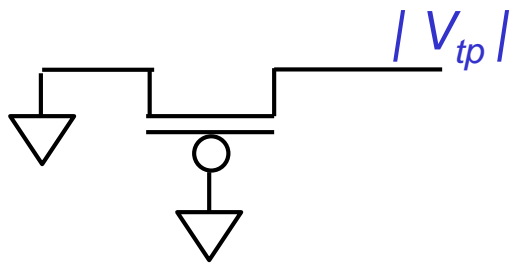
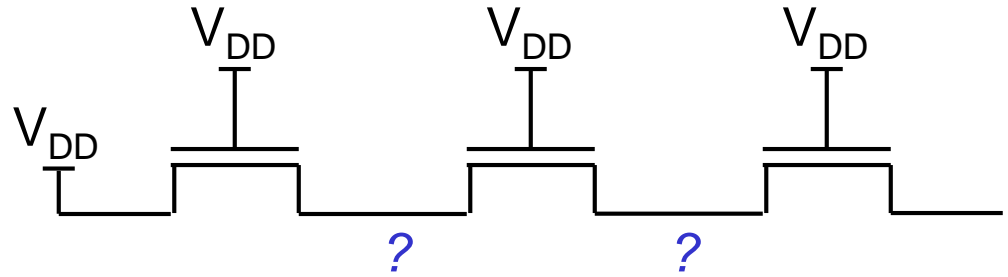
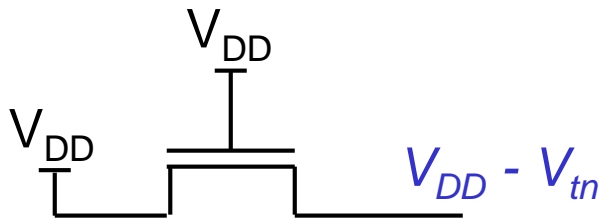


Transmission Gate

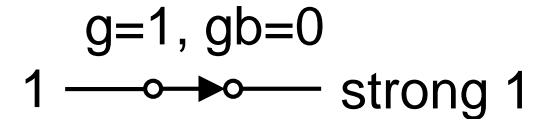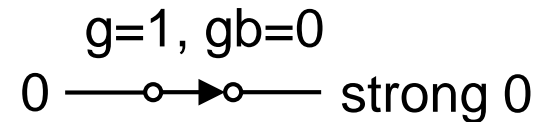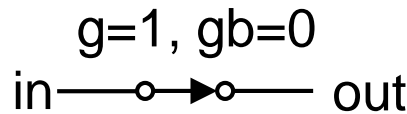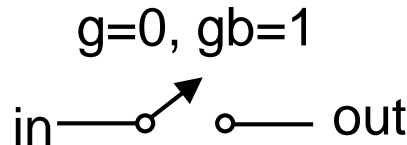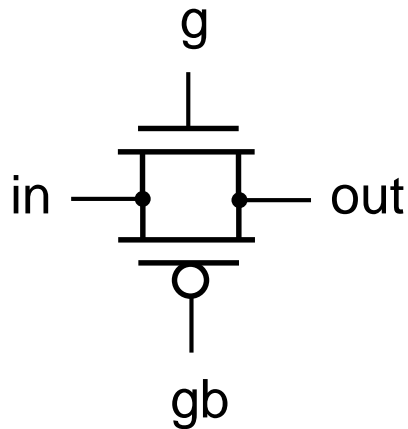
- Transmission gate is a pMOS and nMOS pass transistor in parallel
- Passes a strong 0 and a strong 1



- Common schematic symbols:

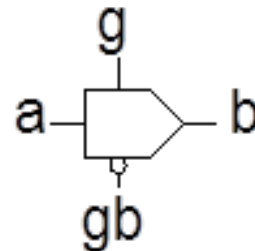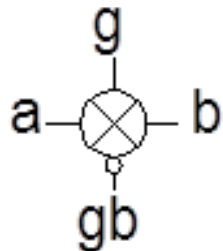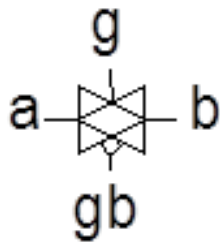


2:1 Multiplexer

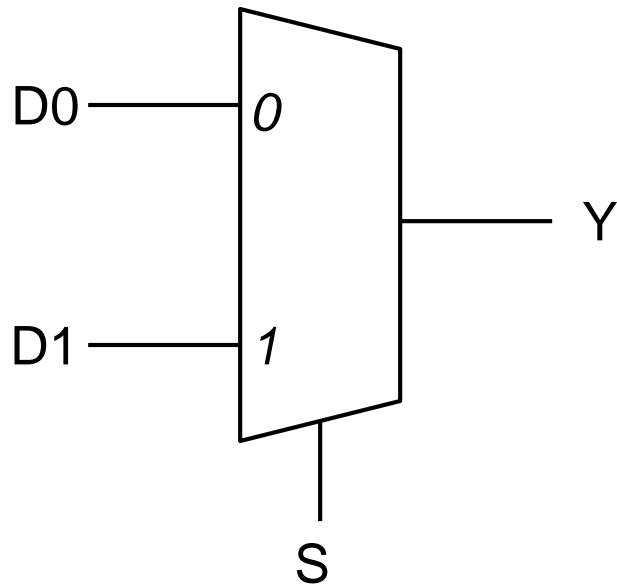


S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

Mux Design using Standard Logic Gates

- $Y = \overline{S}.D0 + S.D1$


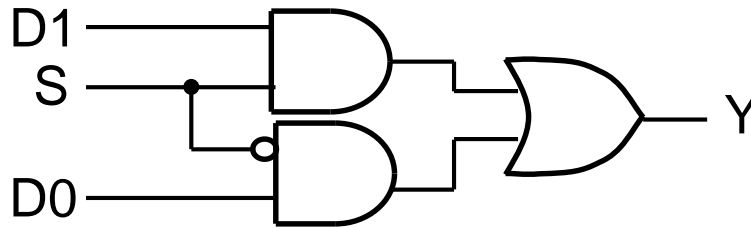


↓ *using complimentary inverting gates*

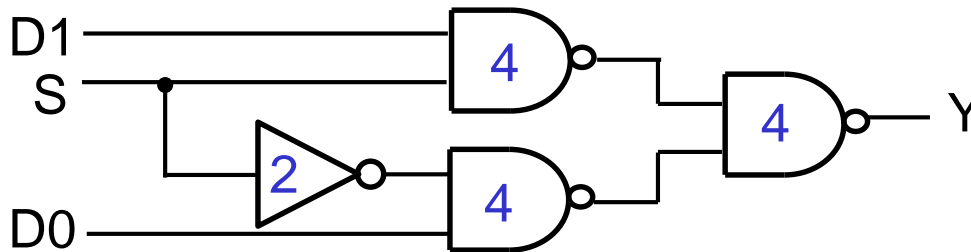

- Requires 14 transistors


Mux Design using Transmission Gates

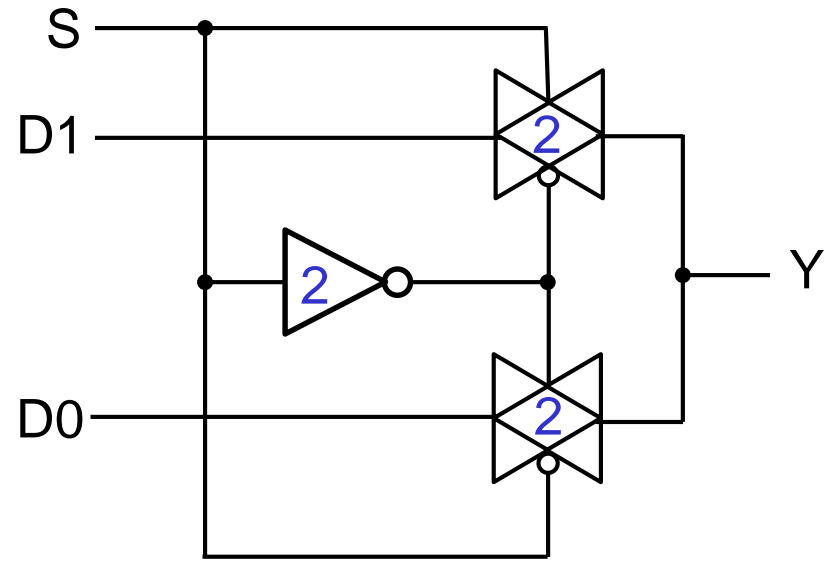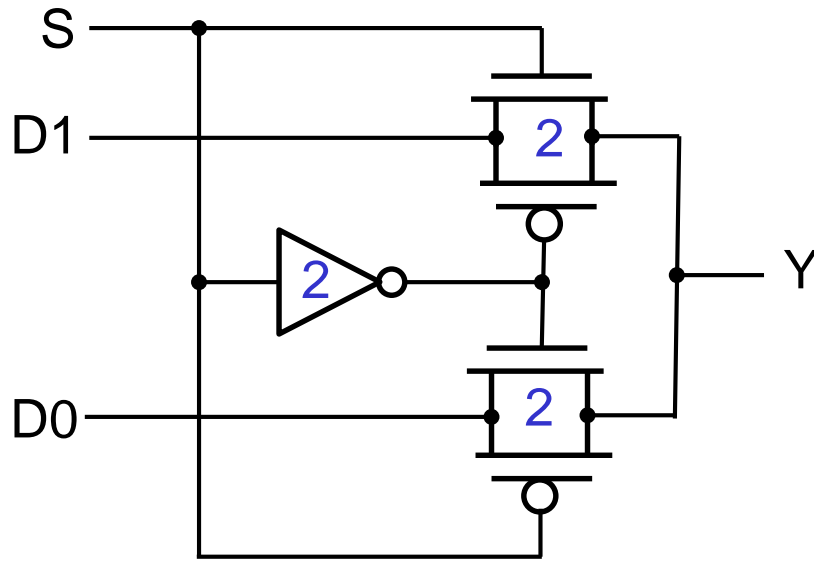

- Requires only 6 transistors
- Use with caution: non-restored logic
- Long chains of transmission gates lead to long delays and degraded levels

Storage Elements

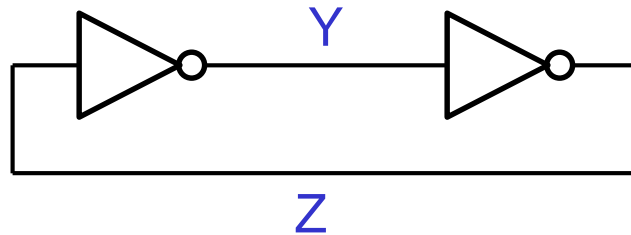
- Basic static storage element is cross-coupled inverter



- Positive feedback drives circuit into one of two stable states
- Either: $(Y=1, Z=0)$ **OR** $(Y=0, Z=1)$
- Circuit will hold state indefinitely
 - restoring effect of digital logic eliminates degradation of stored levels over time
- How do we change the state?

RS Latch

- Simple “writable” storage element

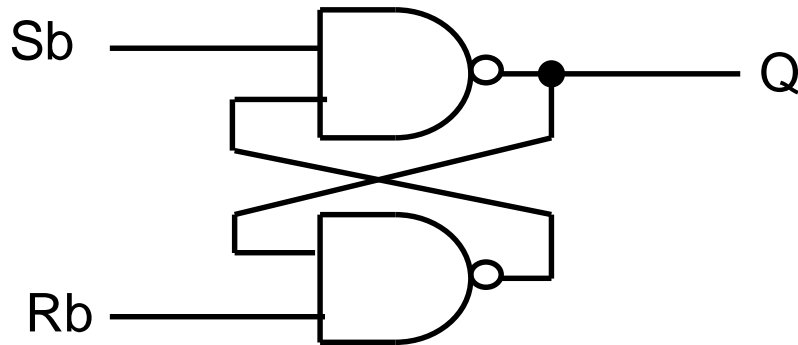



Rb	Sb	Q
0	1	0
1	0	1
1	1	<i>no change</i>
0	0	<i>illegal</i>

- Normally, S_b and R_b are both 1
- When $S_b=0$, Q is set to 1
- When $R_b=0$, Q is reset to 0


D Latch

- When CLK = 1, latch is transparent
- D flows through to Q like a buffer
- When CLK = 0, the latch is opaque
- Q holds its old value independent of D
- a.k.a. transparent latch or level-sensitive latch


D	CLK	Q
0	1	0
1	1	1
0	0	<i>no change</i>
1	0	<i>no change</i>

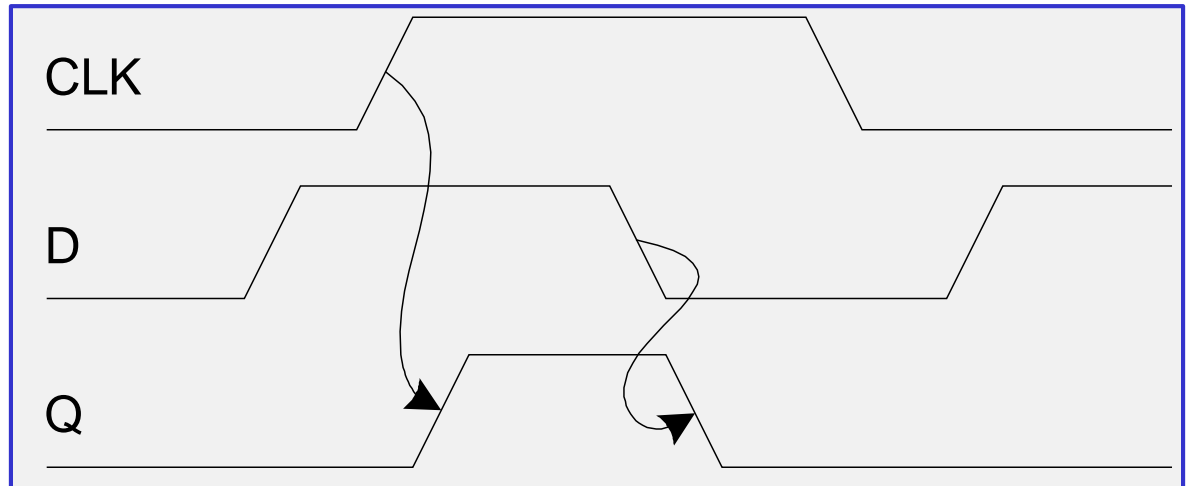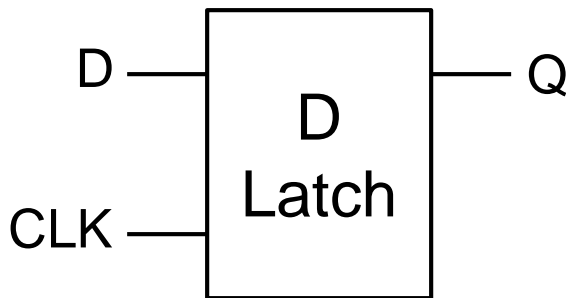

D Latch using Standard Logic Gates


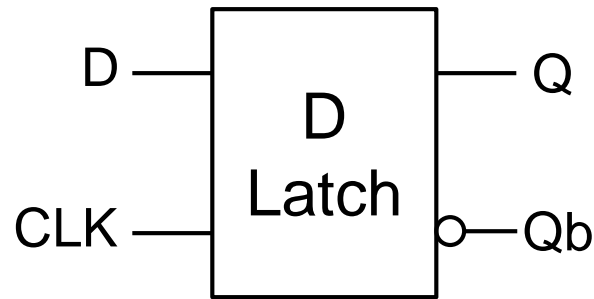


D	CLK	Q	Qb
0	1	0	1
1	1	1	0
0	0	<i>no change</i>	<i>no change</i>
1	0	<i>no change</i>	<i>no change</i>

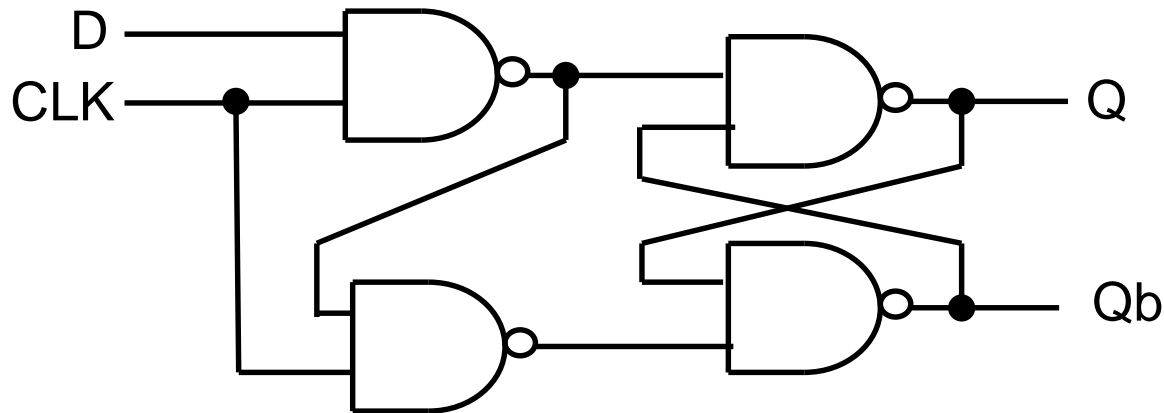



- Uses 16 transistors
- Up to 4 gate delays (D to Q)

D Latch using Transmission Gate

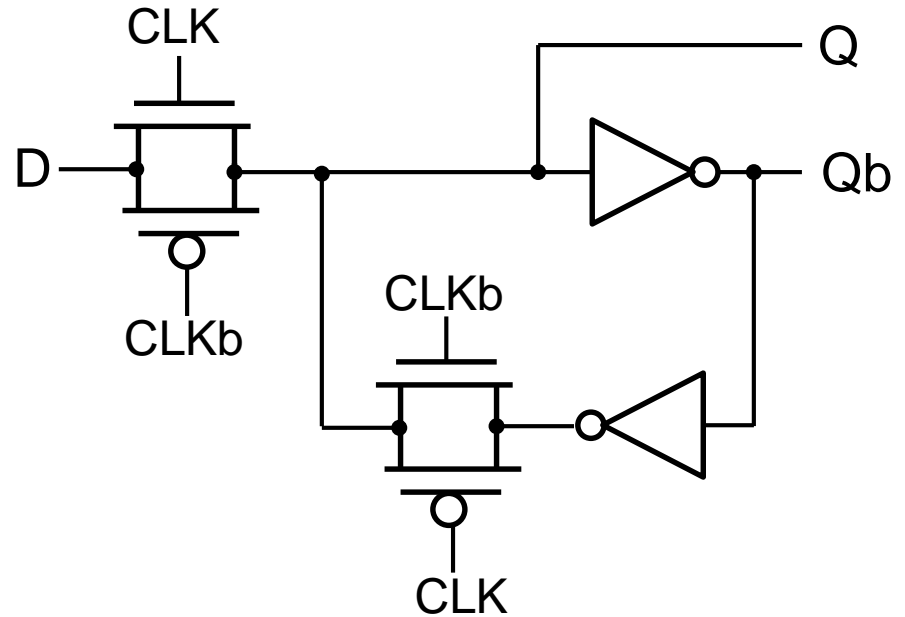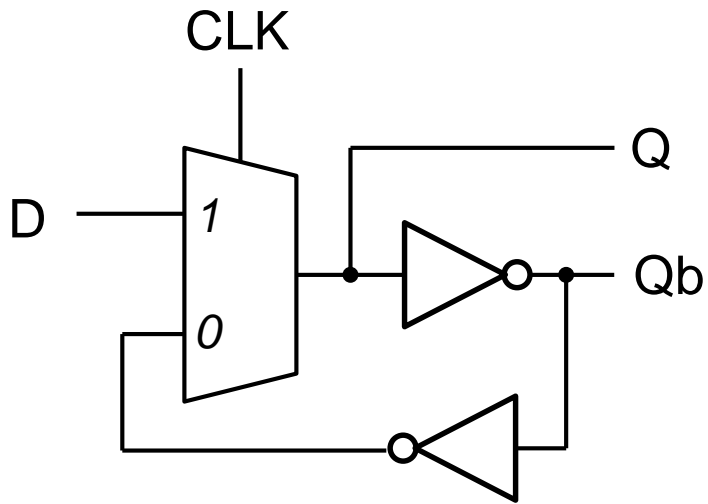


- Multiplexer chooses D or stored Q
- Uses 8 (+2) transistors
- Fast response D to Q
- Q is non-restored

D Latch using Transmission Gate

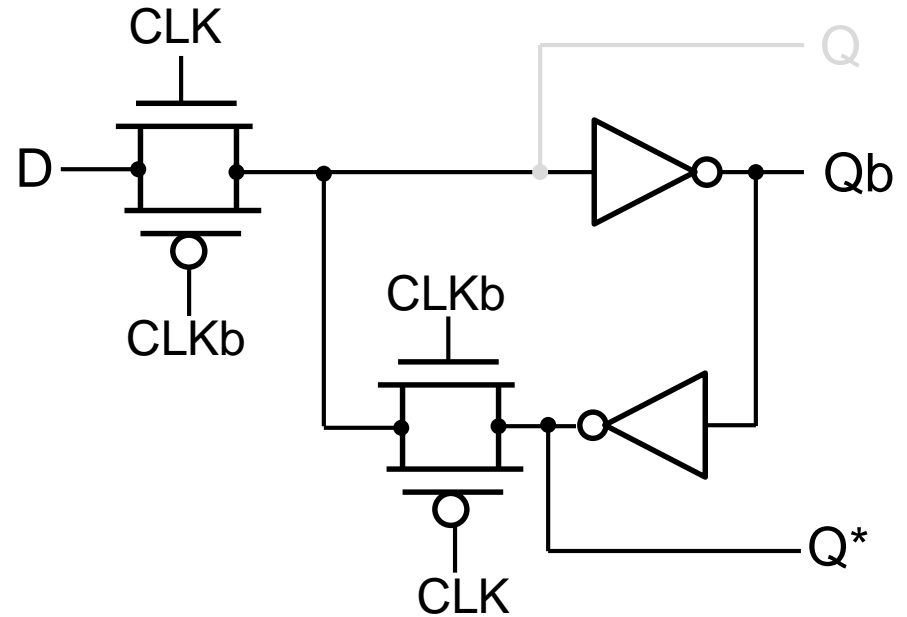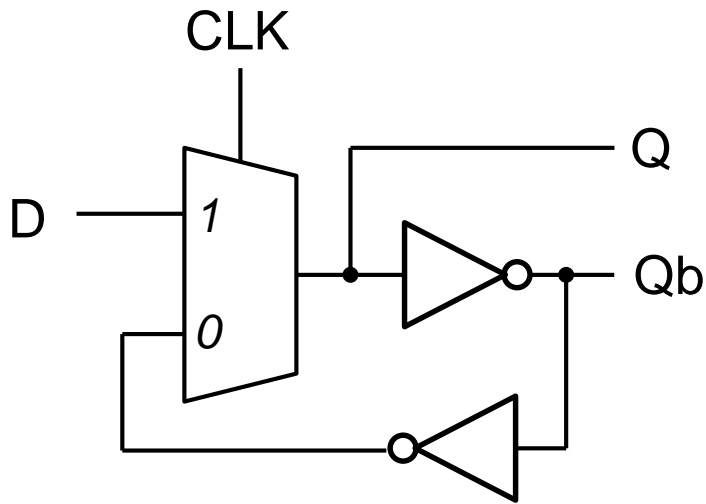


- Multiplexer chooses D or stored Q
- Uses 8 (+2) transistors
- Fast response D to Q
- Q is non-restored
- Q* is slower response, but fully restored

Alternative CMOS D Latch

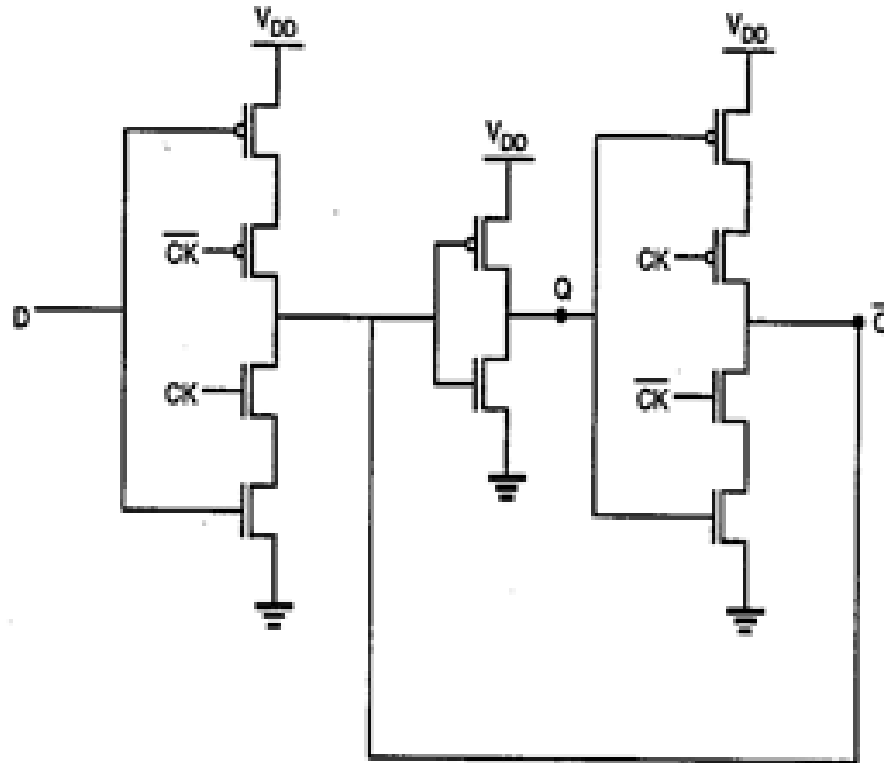


- What is happening here?

D Flip-flop

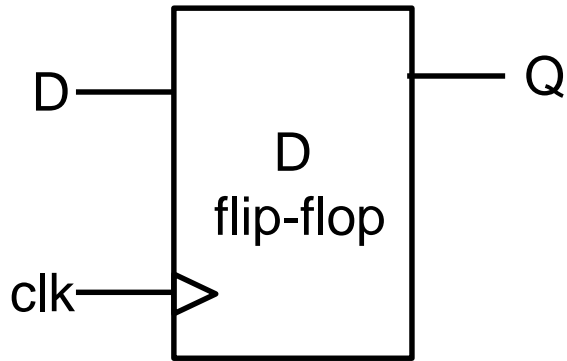



clk	D	Q
0	X	no change
1	X	no change
↑	1	1
↑	0	0

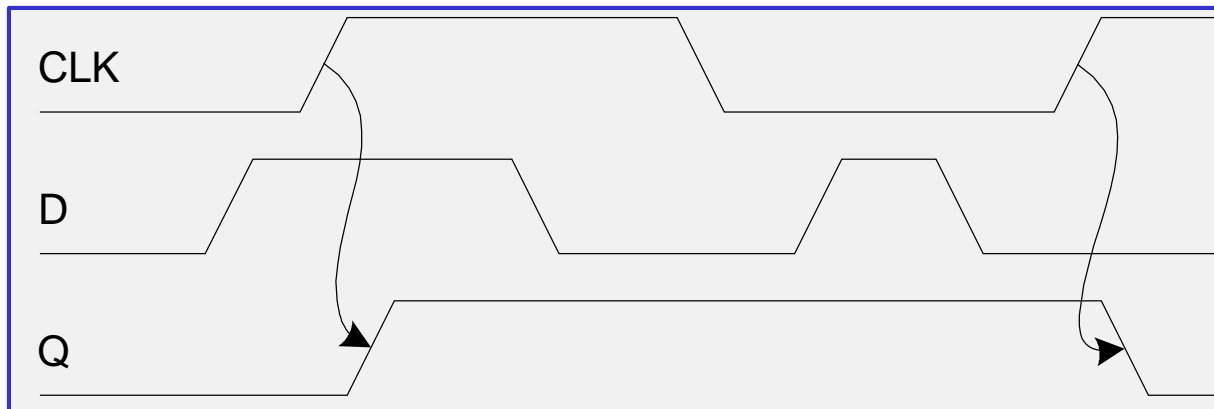- When CLK rises, D is copied to Q
- At all other times, Q holds its value
- a.k.a. edge-triggered flip-flop, master-slave flip-flop





Master-Slave Latches

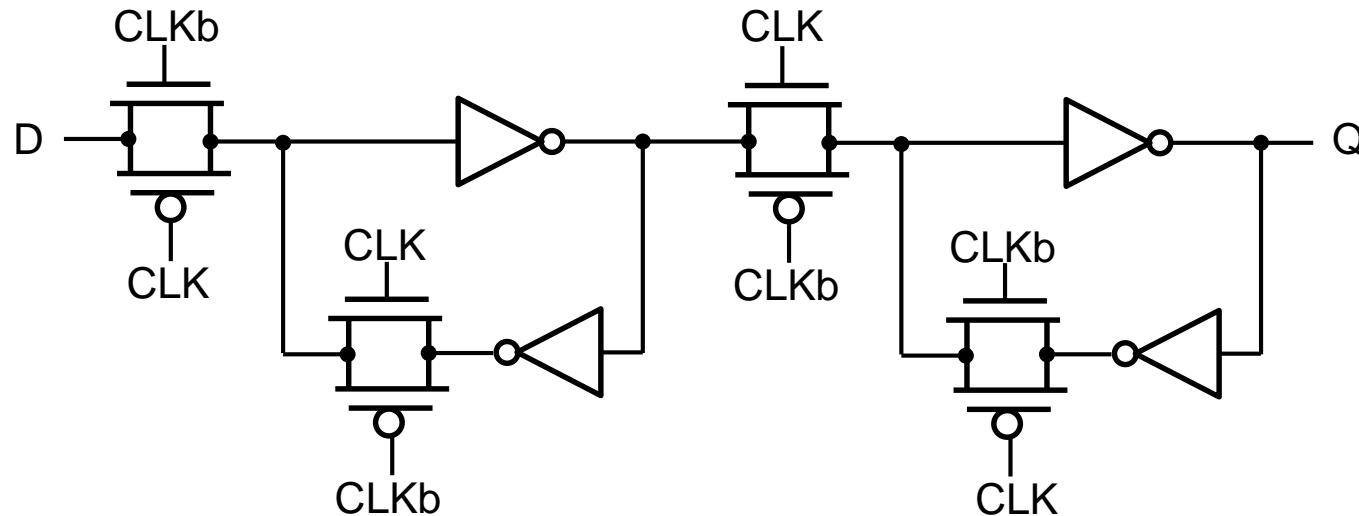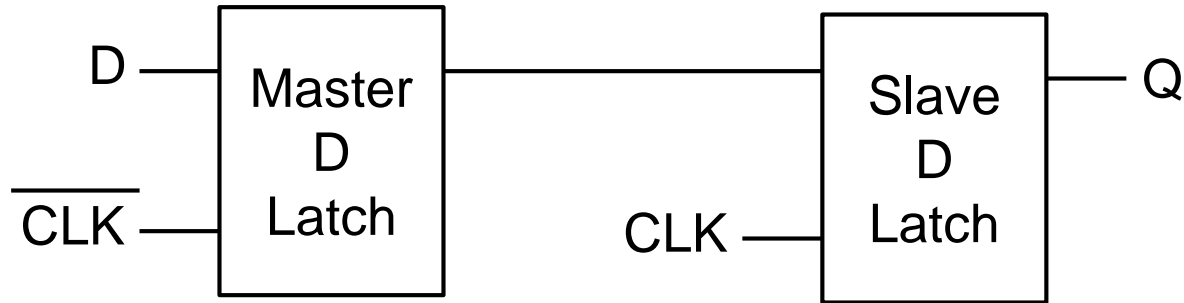
- D Flip-flop is built from two D latches




D Flip-flop Operation

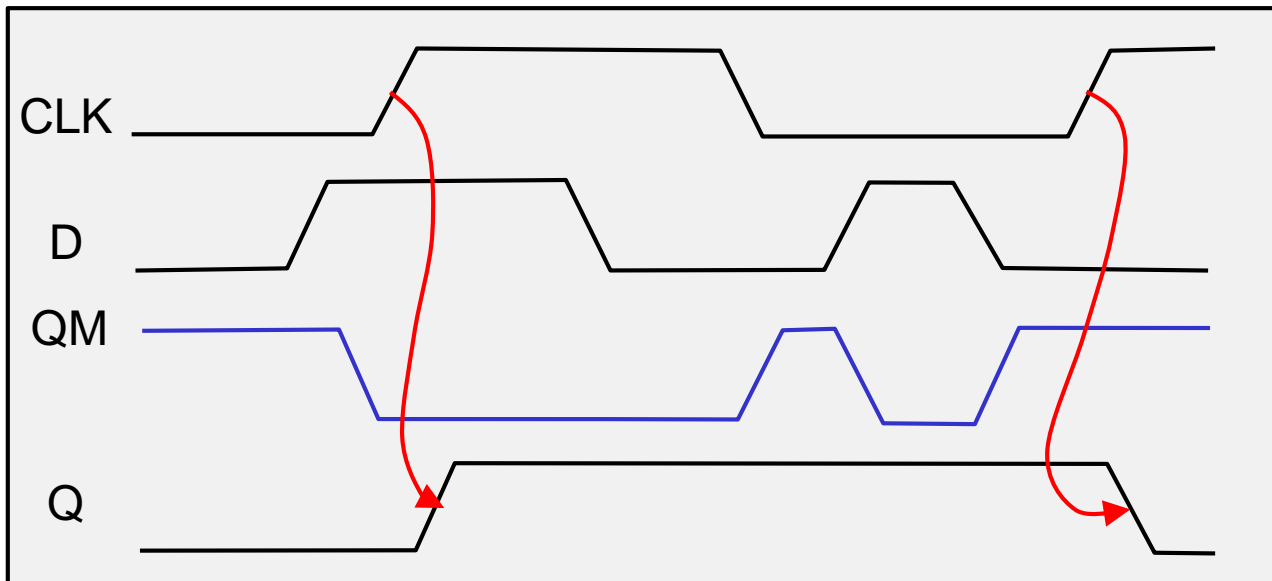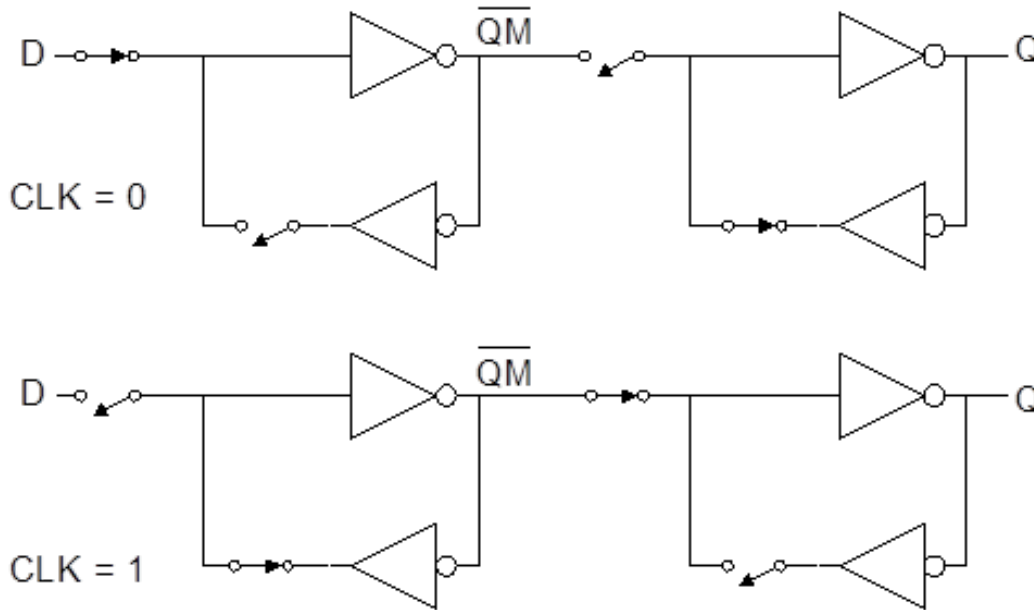

Another D-Flip-flop Implementation

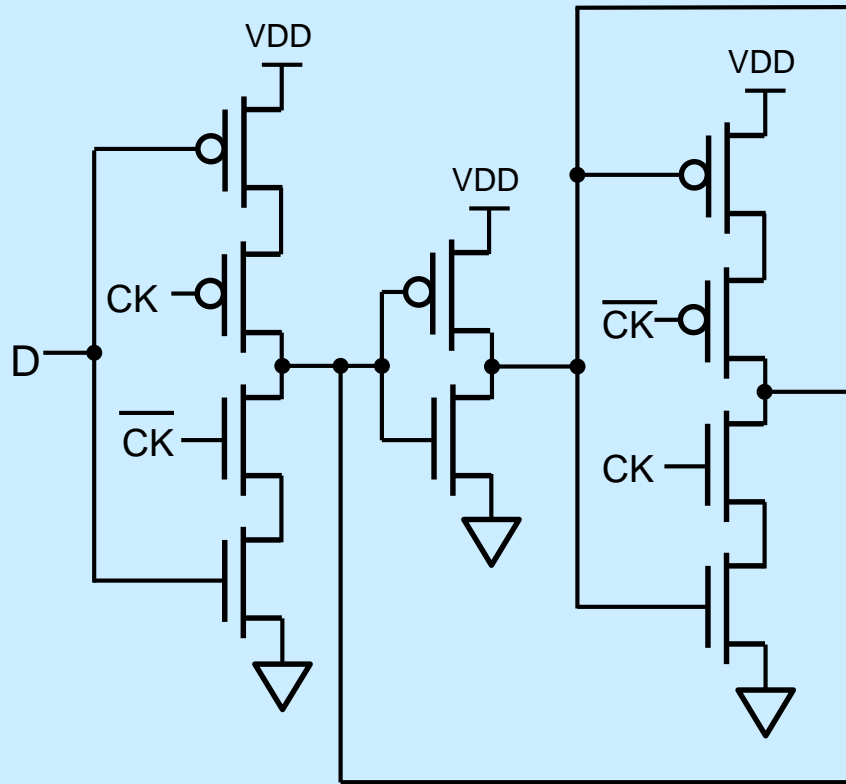

master

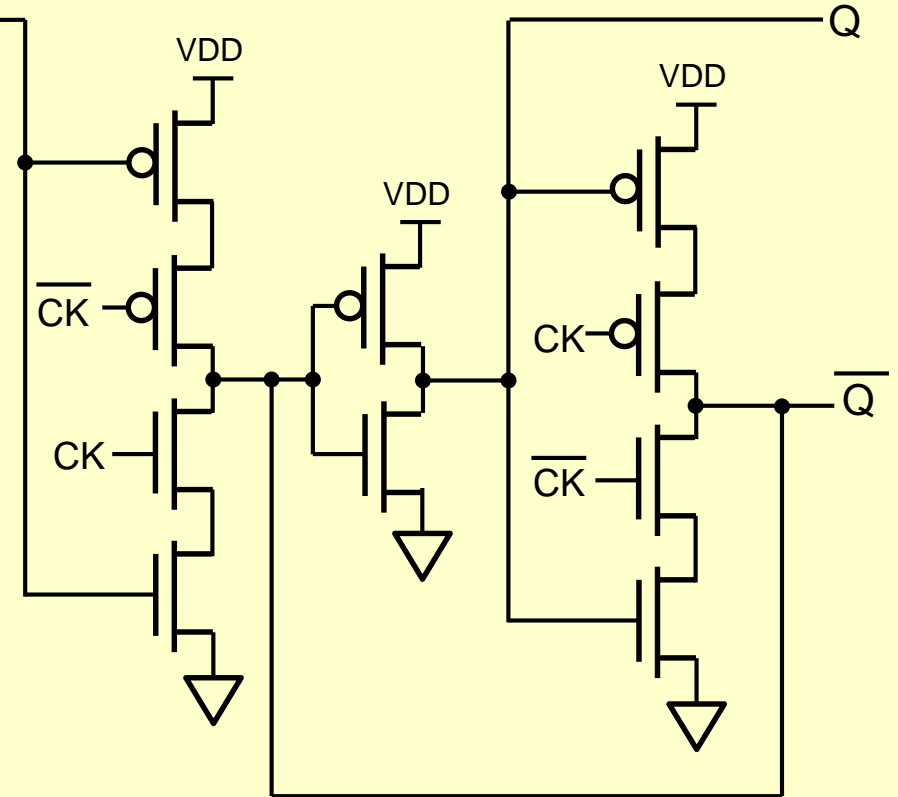


slave

DC Response: Inverter

- Digital circuits are merely analog circuits used over a constrained portion of their range
- Derive DC transfer function for static CMOS inverter
- When $V_{in} = 0 \Rightarrow V_{out} = V_{DD}$
- When $V_{in} = V_{DD} \Rightarrow V_{out} = 0$
- In between, V_{out} depends on transistor size and current
- By KCL, must settle such that


$$I_{dsn} = |I_{dsp}|$$

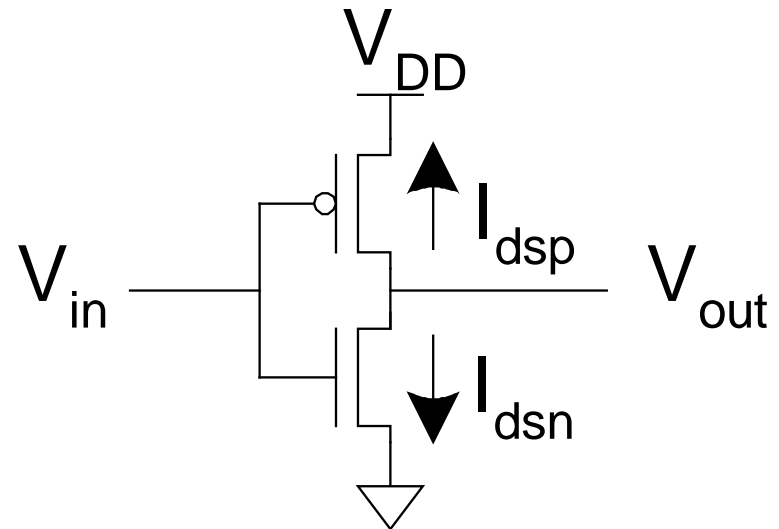

- We could solve equations, but ...
- Graphical solution gives more insight

Transistor Operation

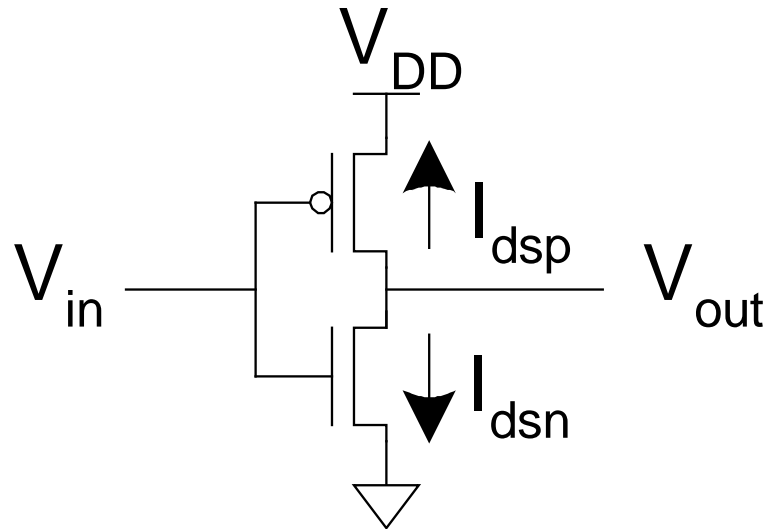- Current (I_{dsn} , I_{dsp}) depends on region of transistor behavior
- For what V_{in} and V_{out} are nMOS and pMOS in
- Cutoff?
- Linear?
- Saturation?




Inverter: nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

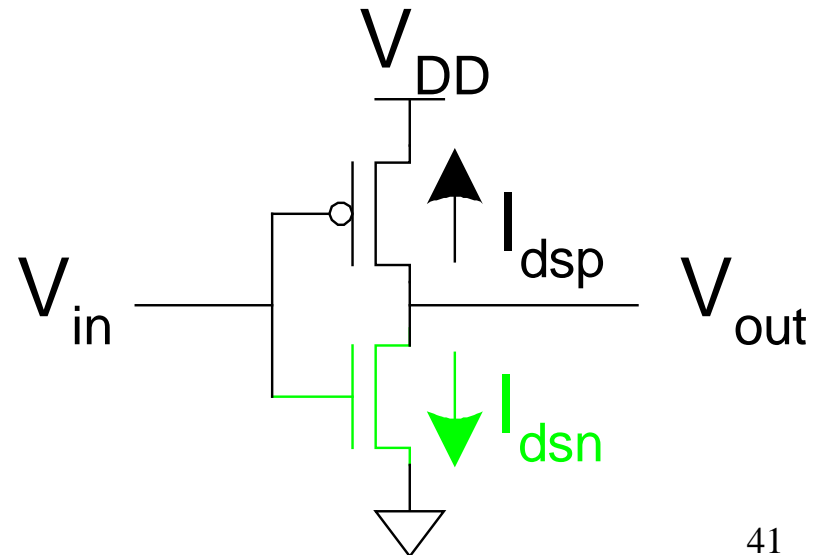


Inverter: pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$


$$V_{dsp} = V_{out} - V_{DD}$$

(remember: V_{dsp} and $V_{tp} < 0$)

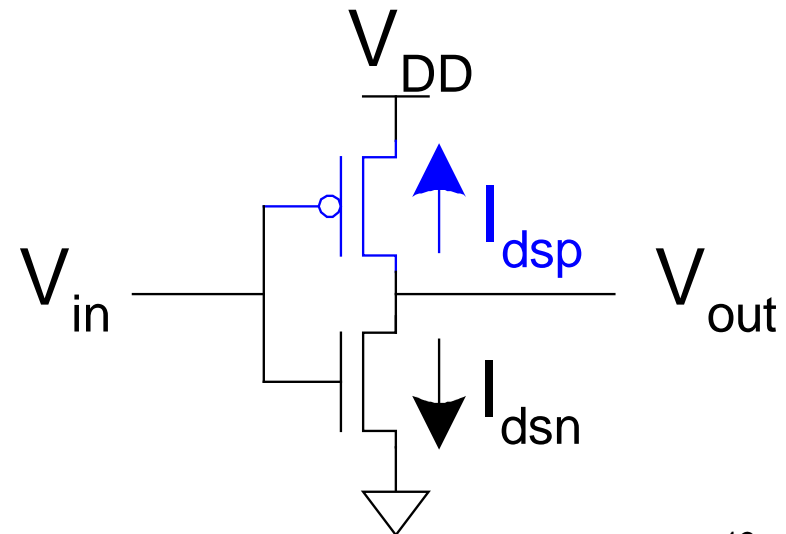


I-V Characteristics


- Mobility of holes is 2-3x less than mobility of electrons
- Usually make pMOS 2x wider than nMOS
 - so that $\beta_n \approx \beta_p$

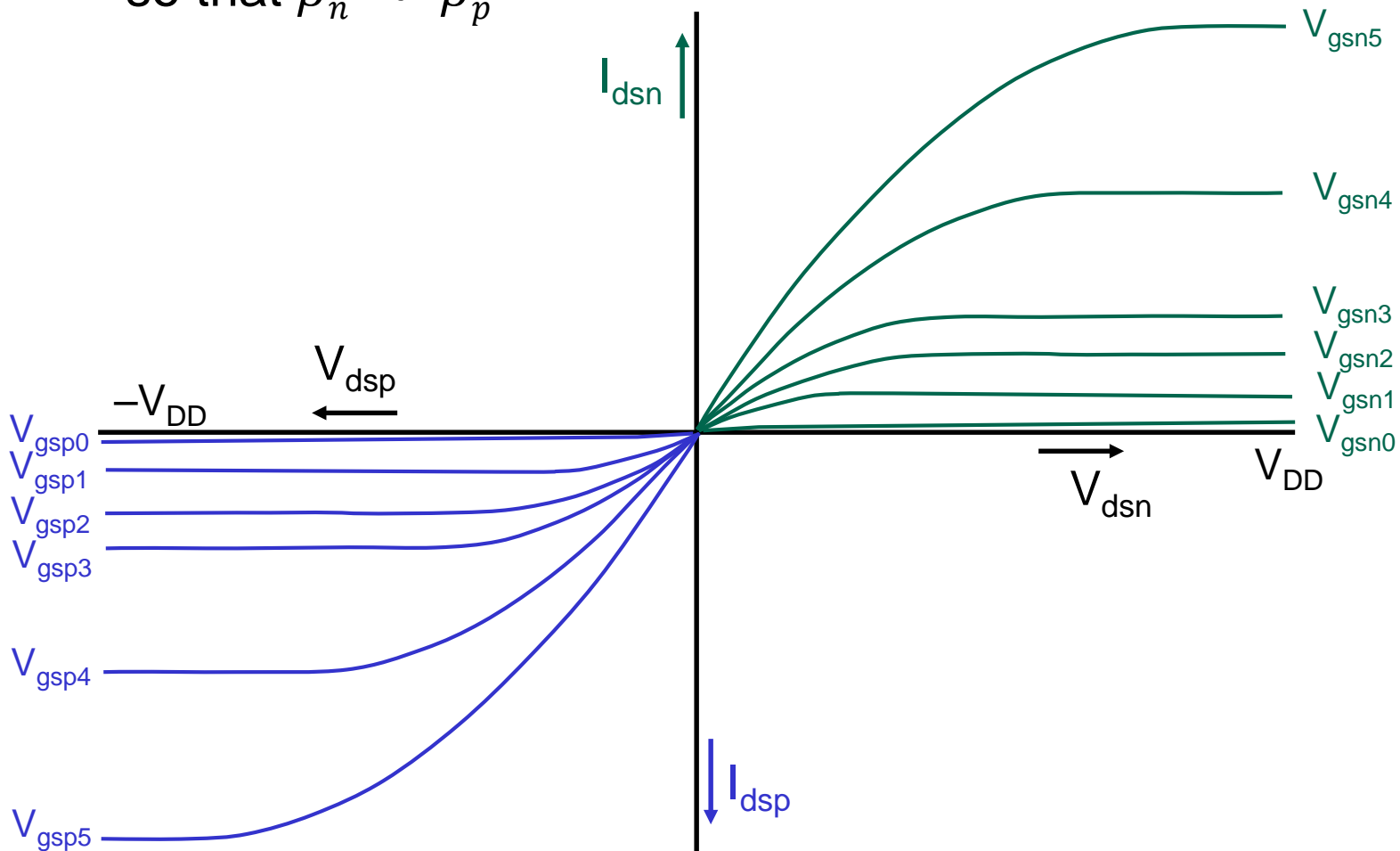

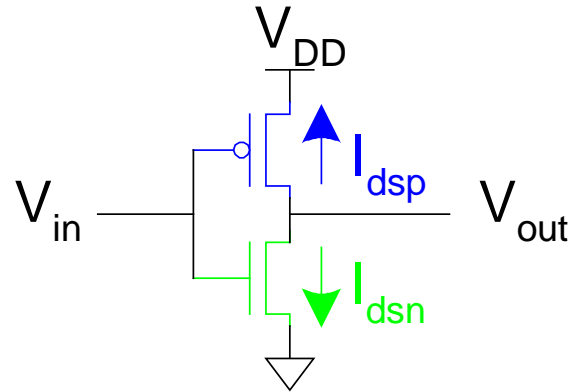Replot I-V as function of V_{out} & V_{in}





V_{out} is where $I_{dn} = -I_{dp}$

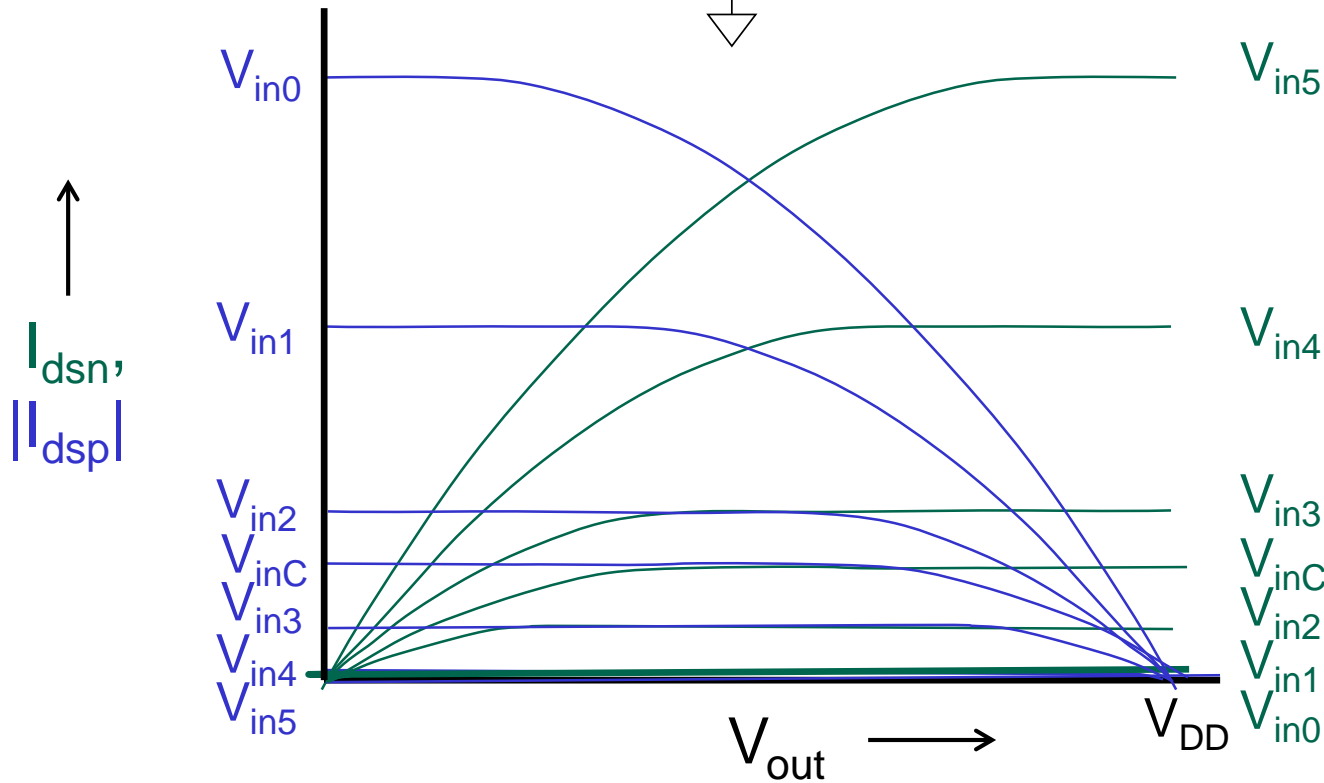



Load Line Analysis

- $V_{in} = 0$

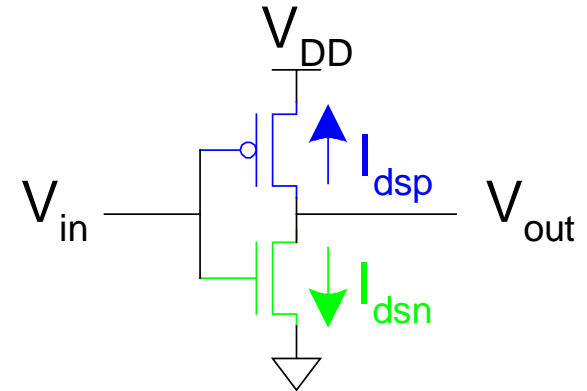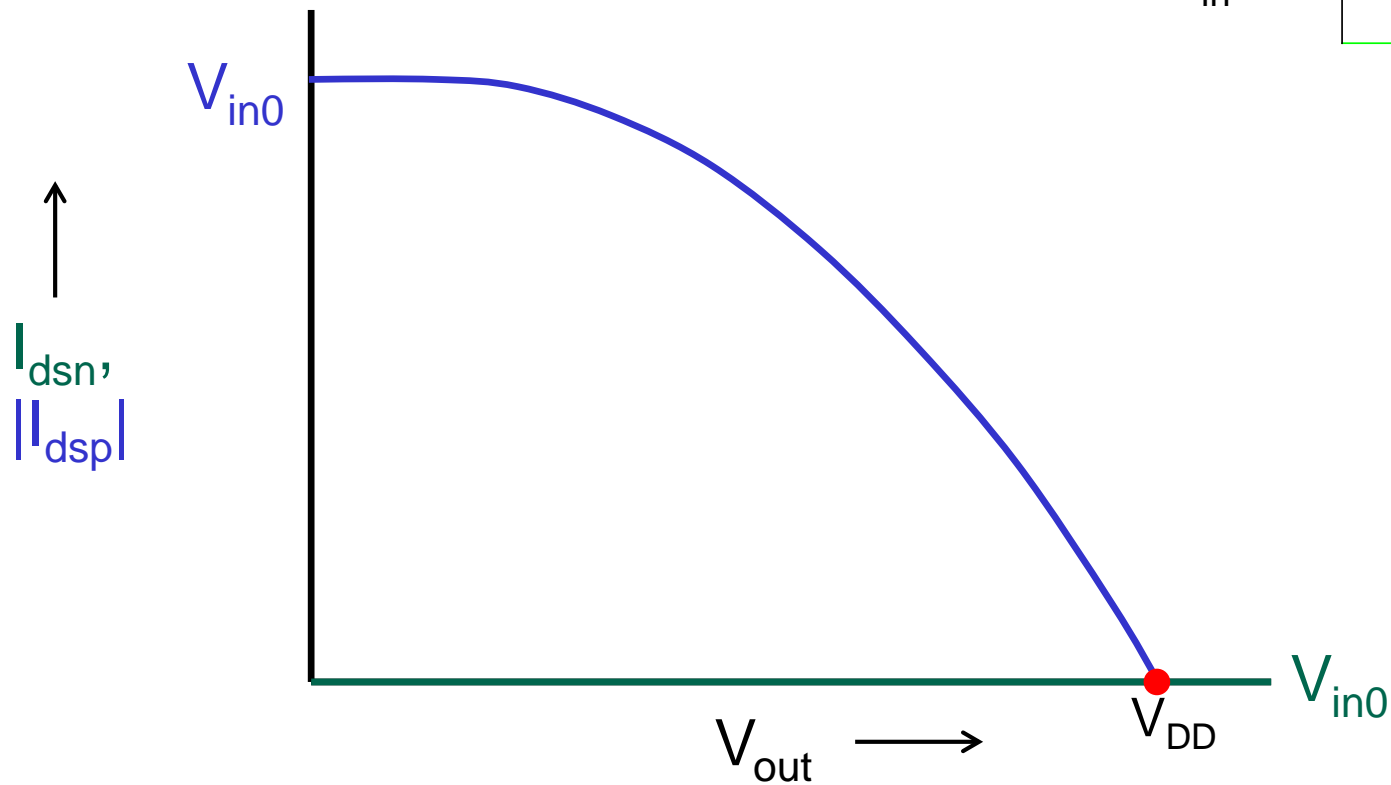



Load Line Analysis

- $V_{in} = 0.2V_{DD}$

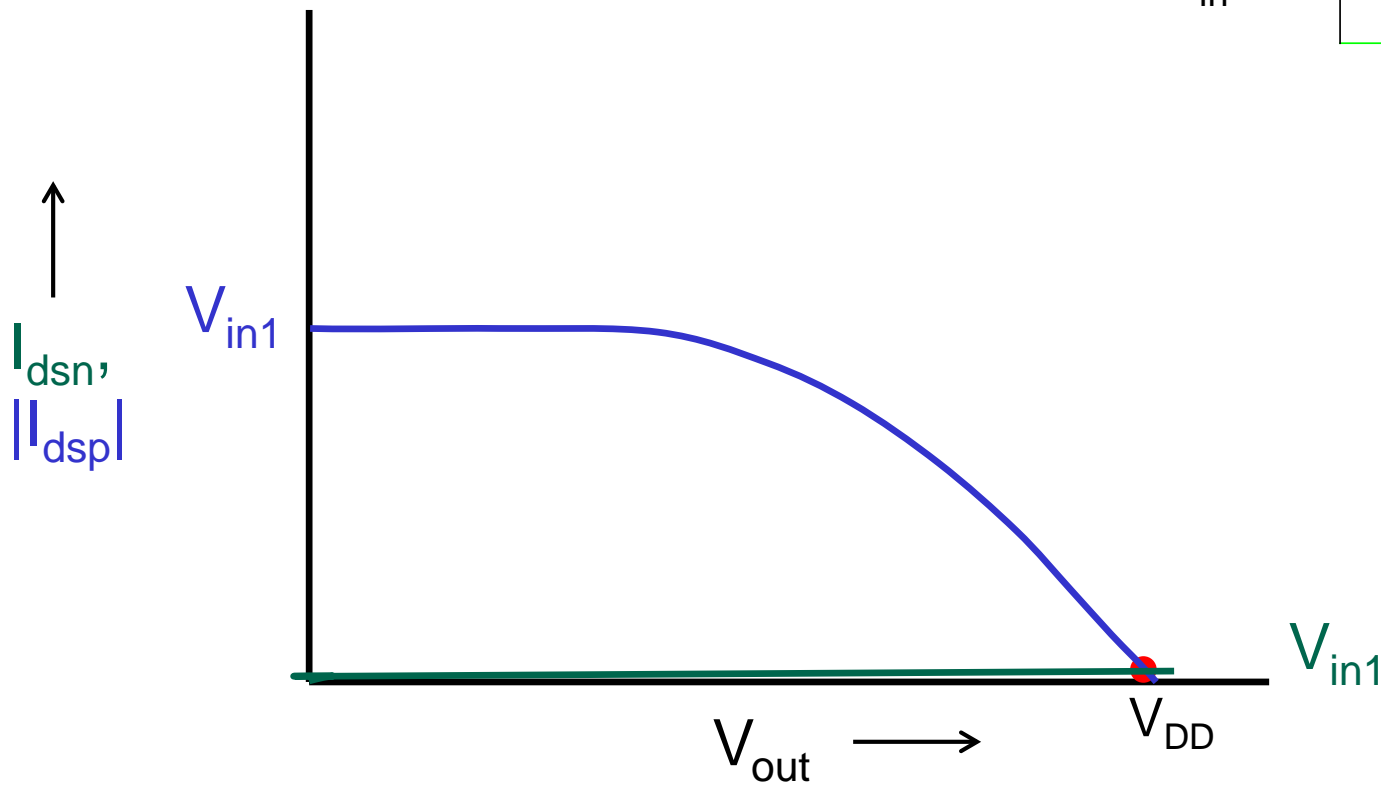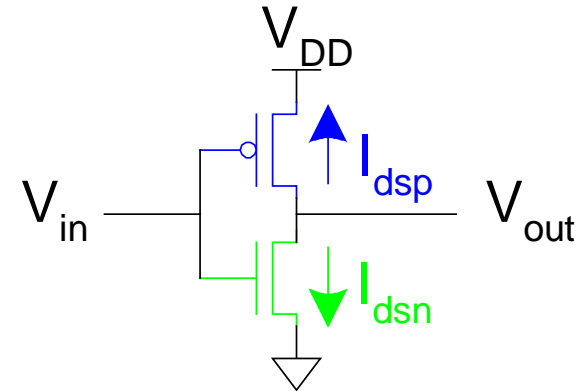



Load Line Analysis

- $V_{in} = 0.4V_{DD}$

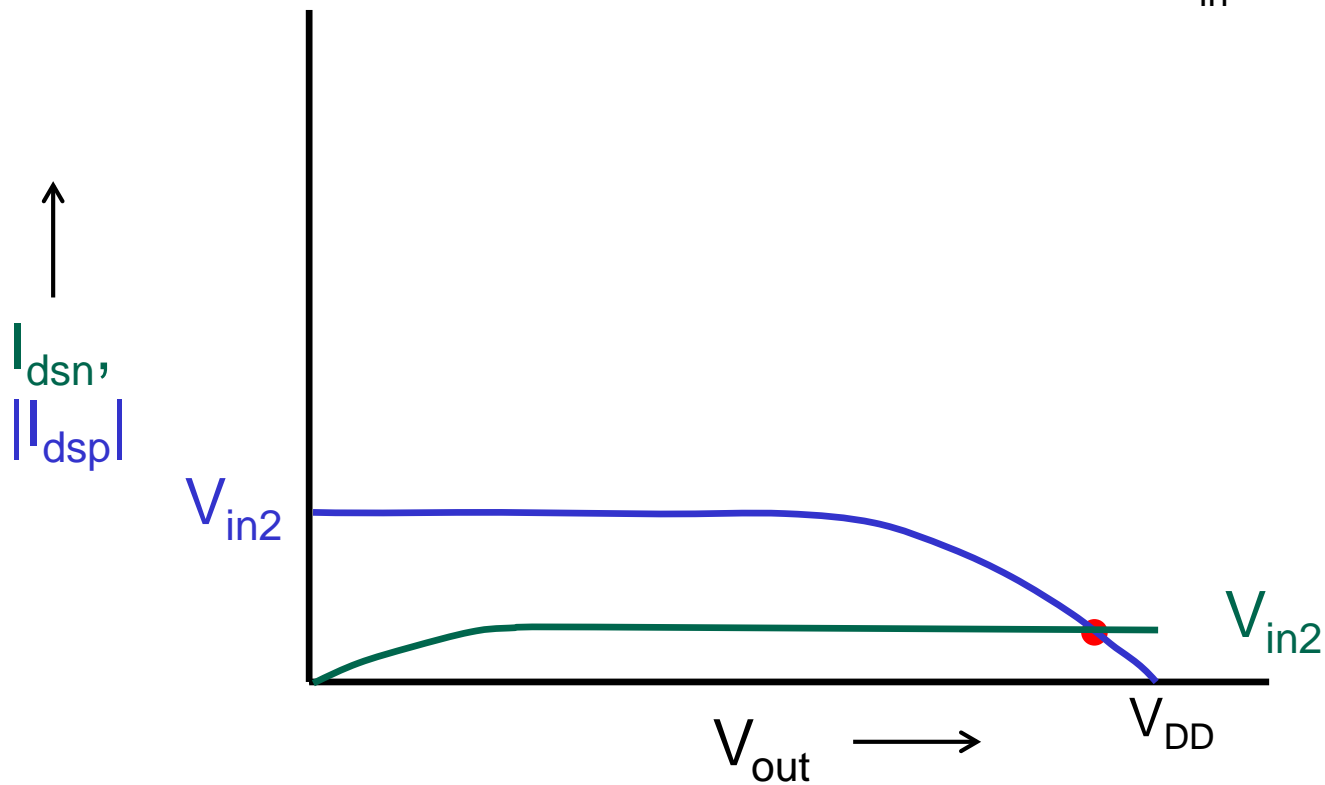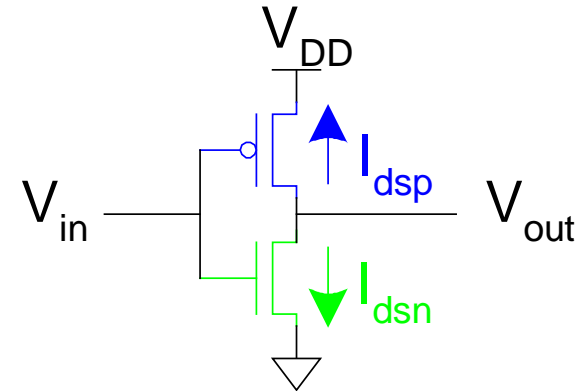



Load Line Analysis

- $V_{in} = 0.5V_{DD}$

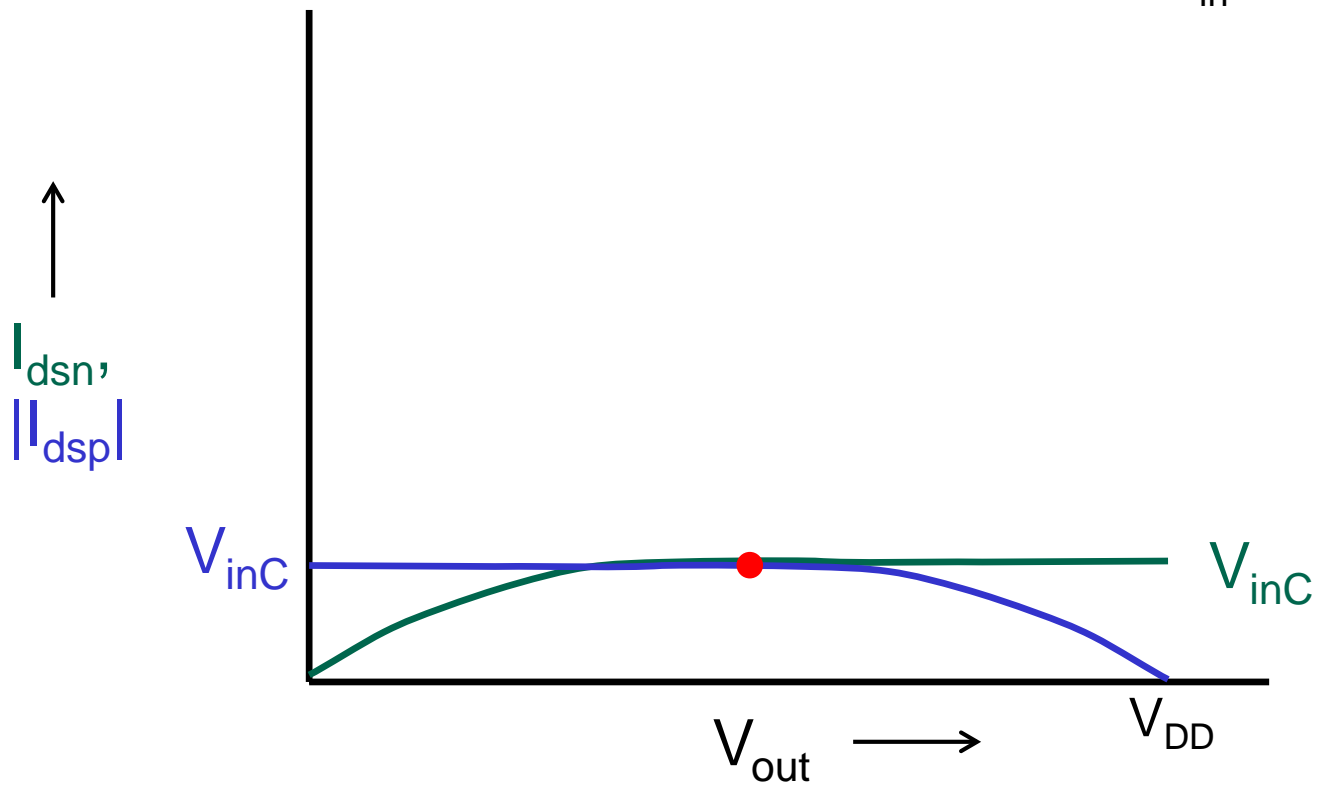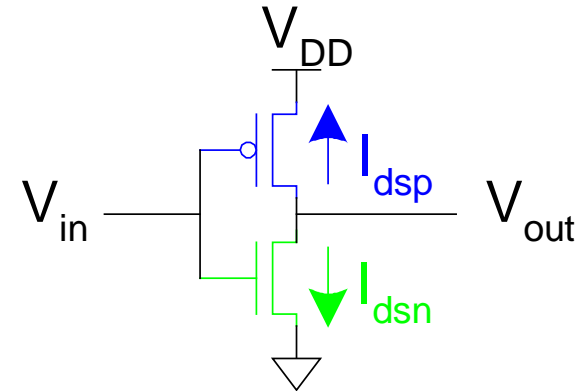



Load Line Analysis

- $V_{in} = 0.6V_{DD}$

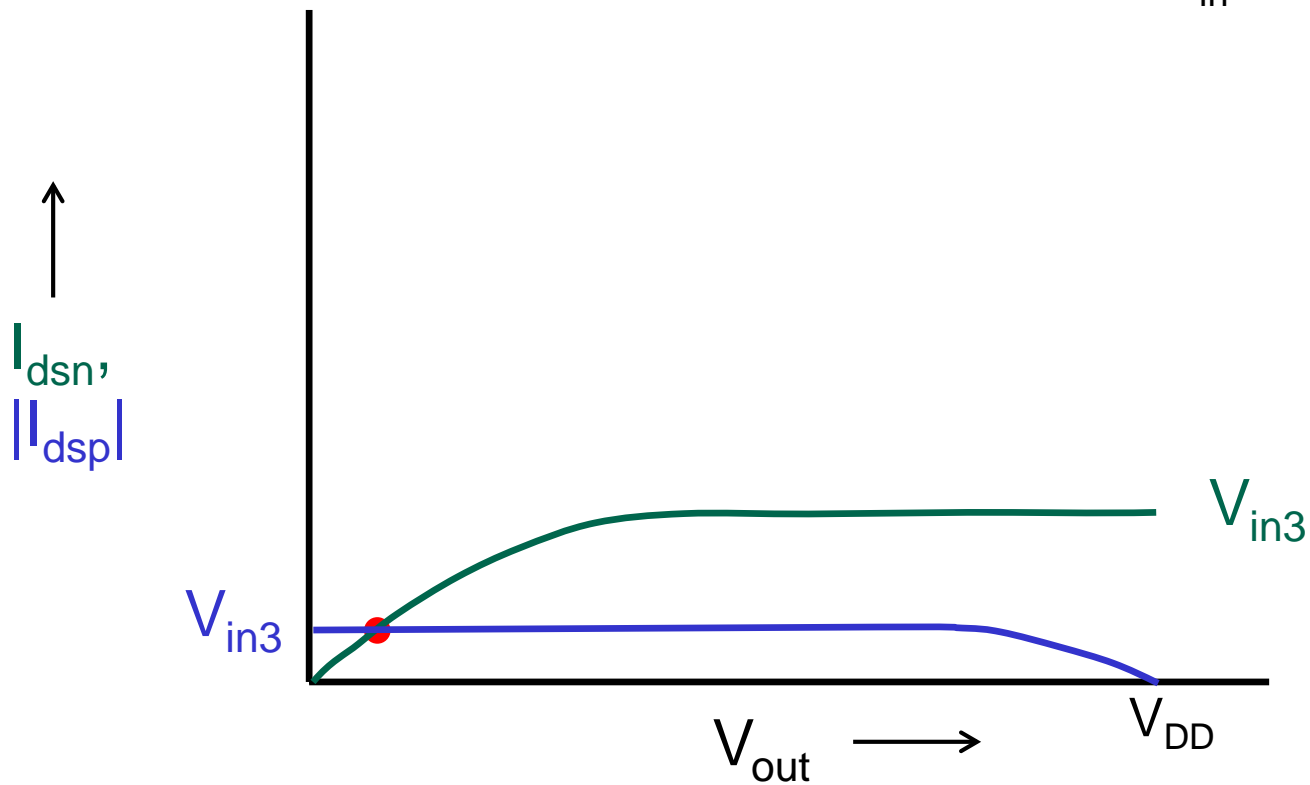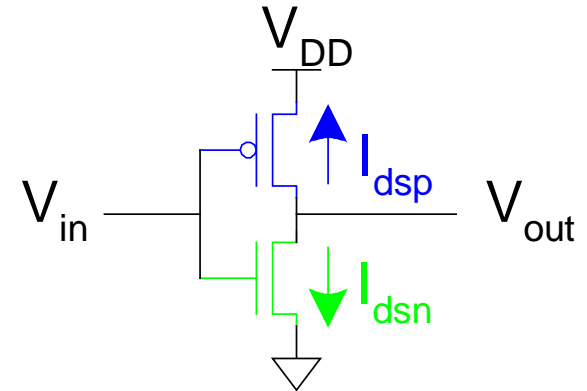



Load Line Analysis

- $V_{in} = 0.8V_{DD}$

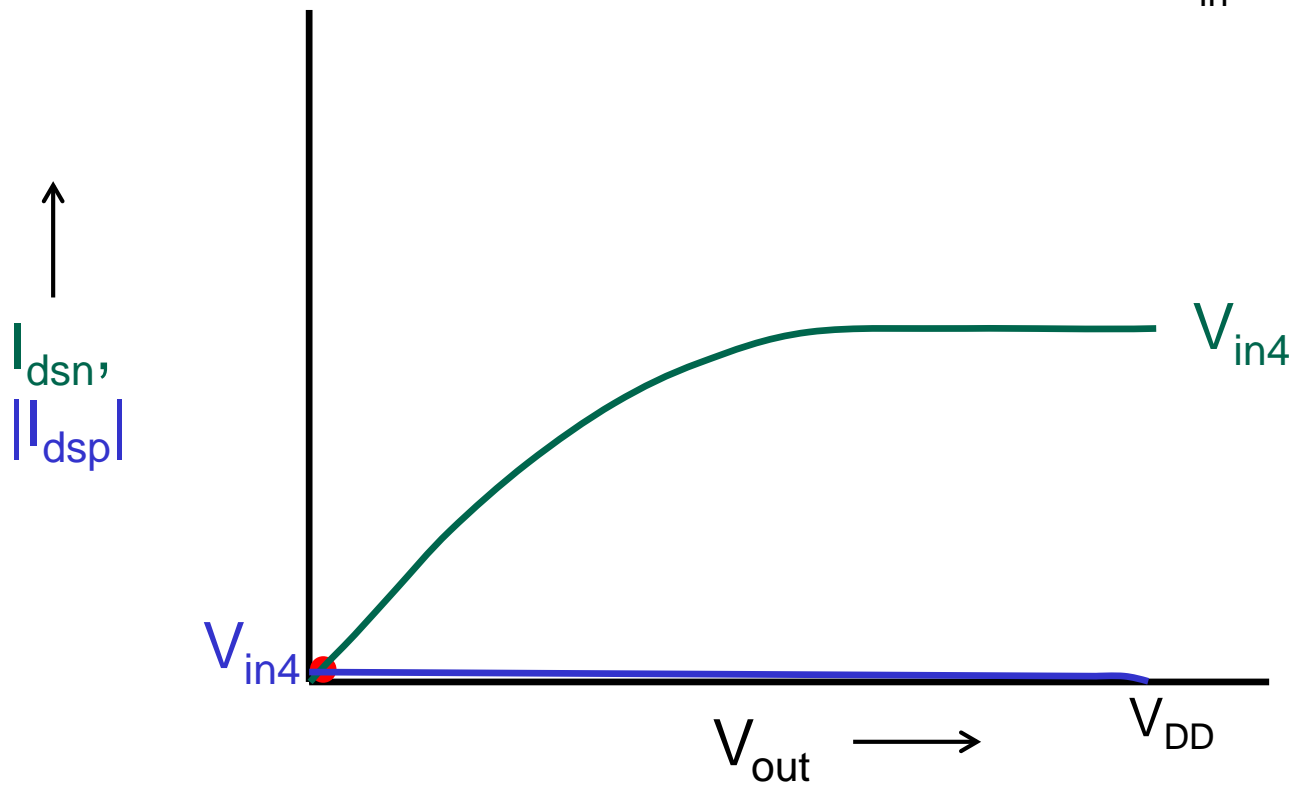
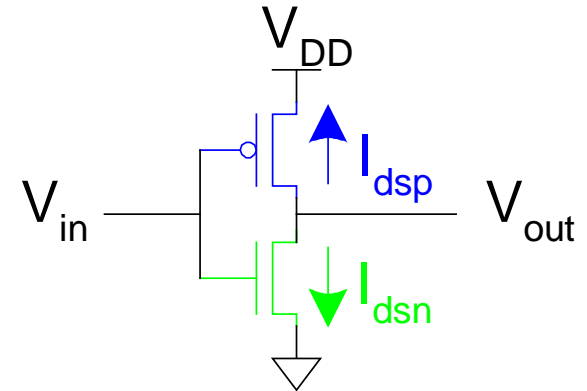


Load Line Analysis

- $V_{in} = V_{DD}$

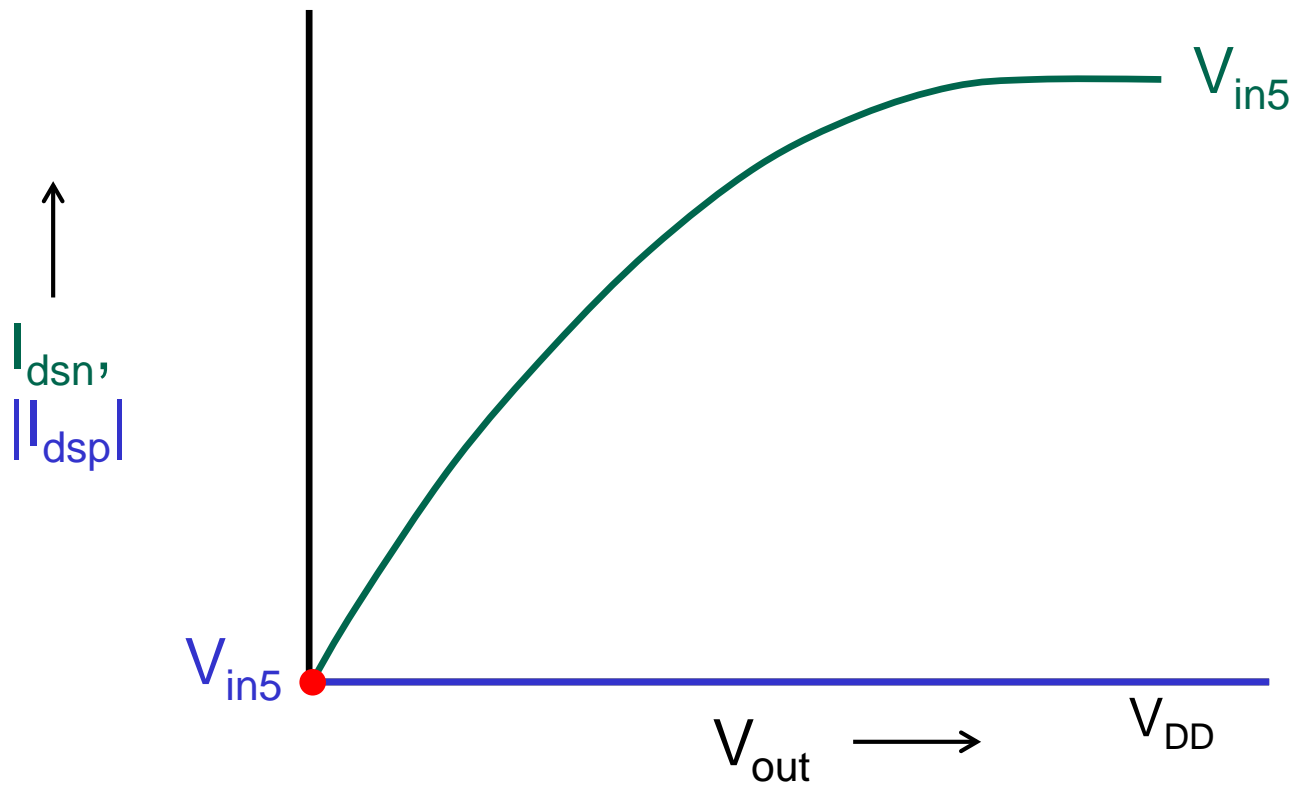
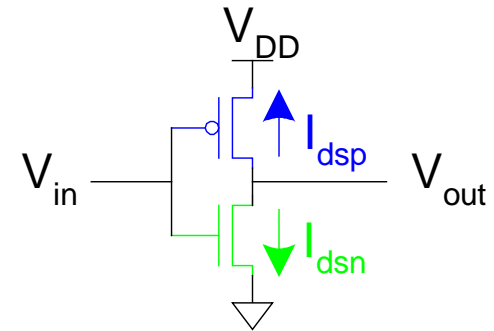


Load Line Analysis

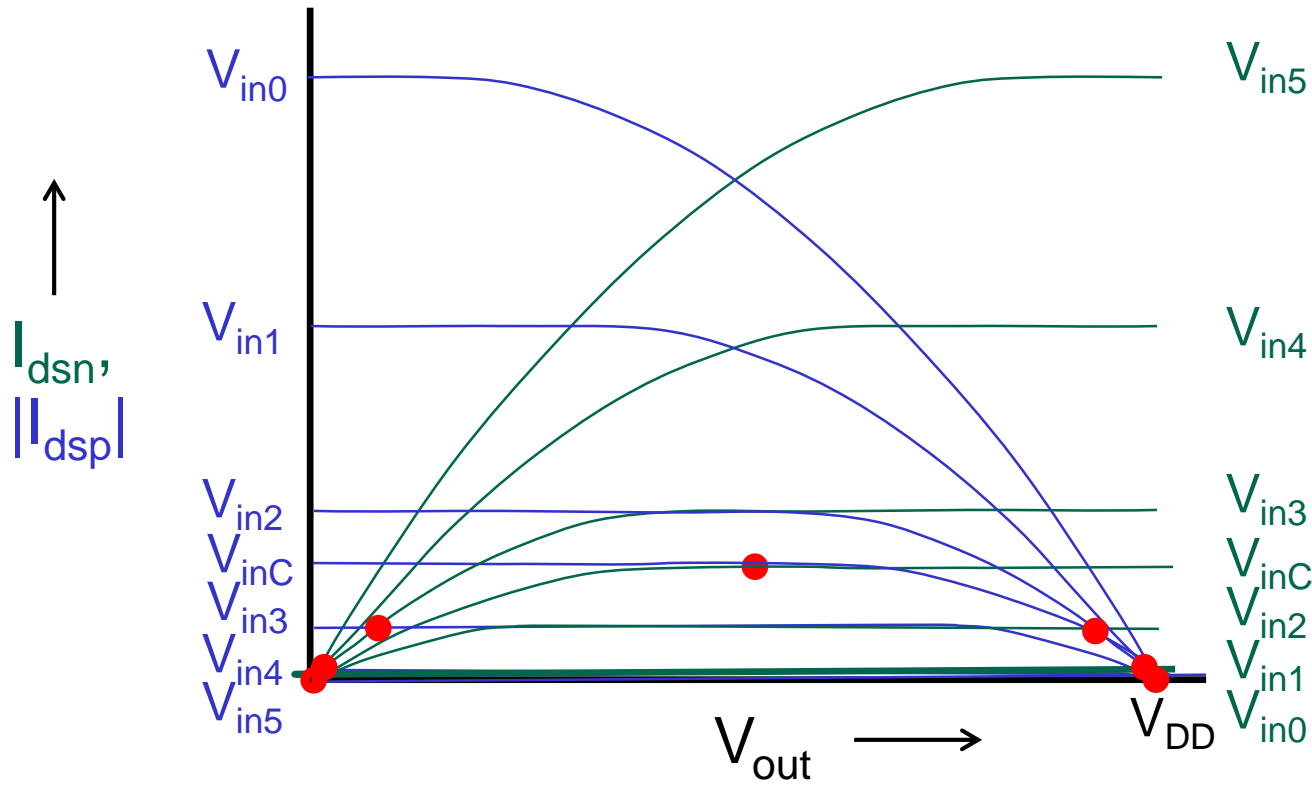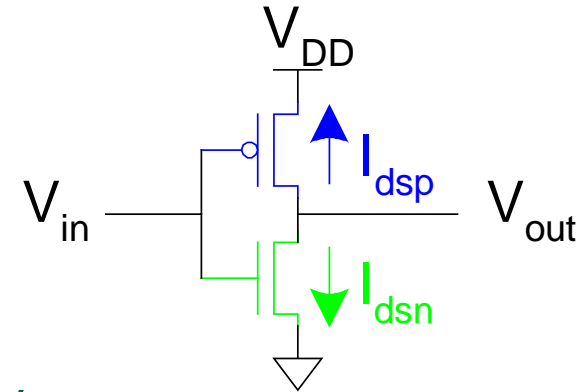



DC Transfer Curve

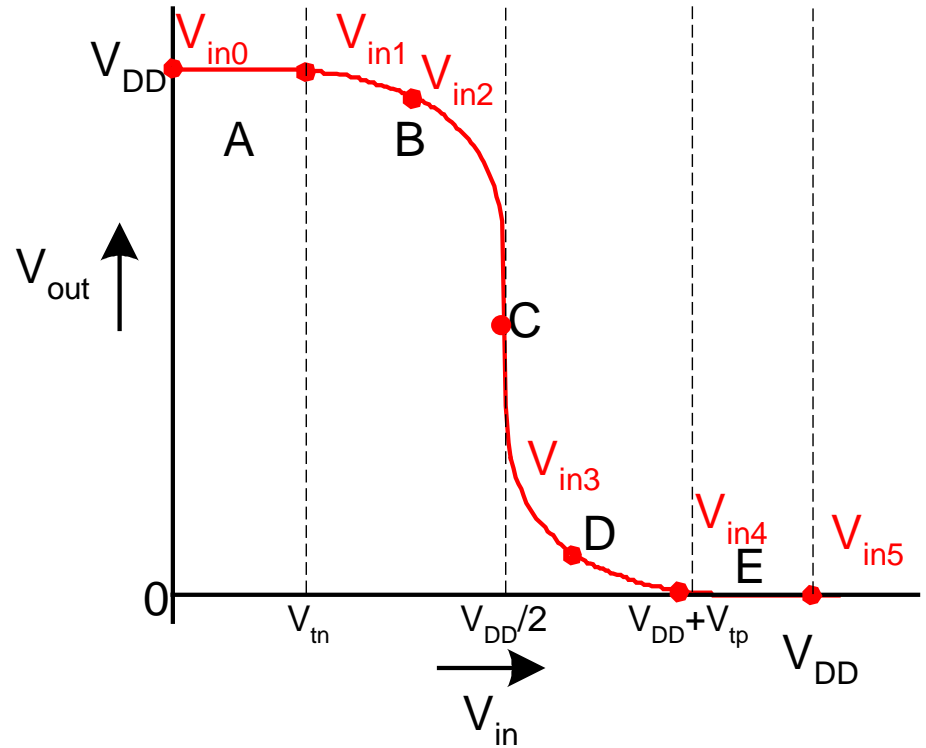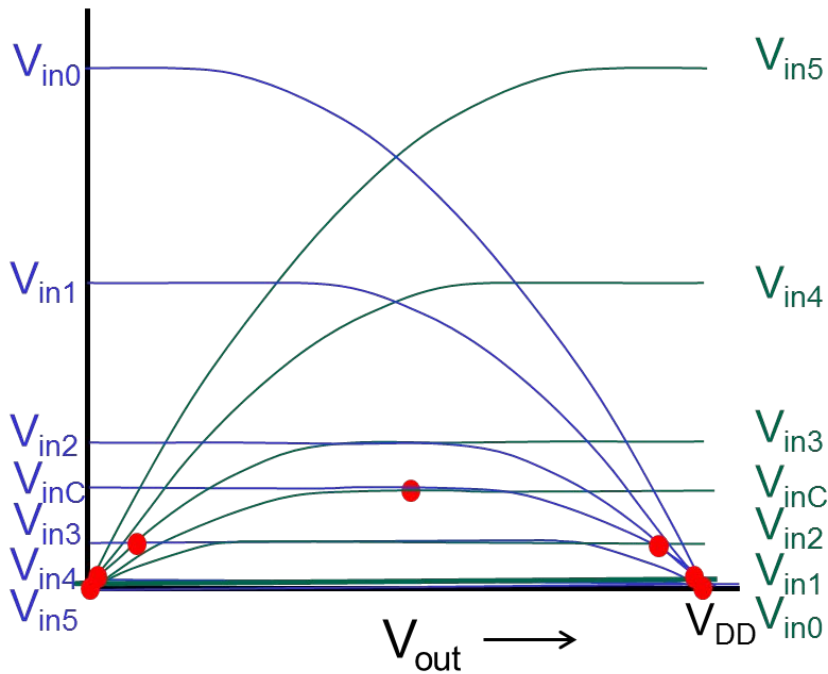- Trans-scribe points onto V_{in} vs. V_{out} plot



Supply Current

- $I_{DD} = I_{dsn} = -I_{dsp}$

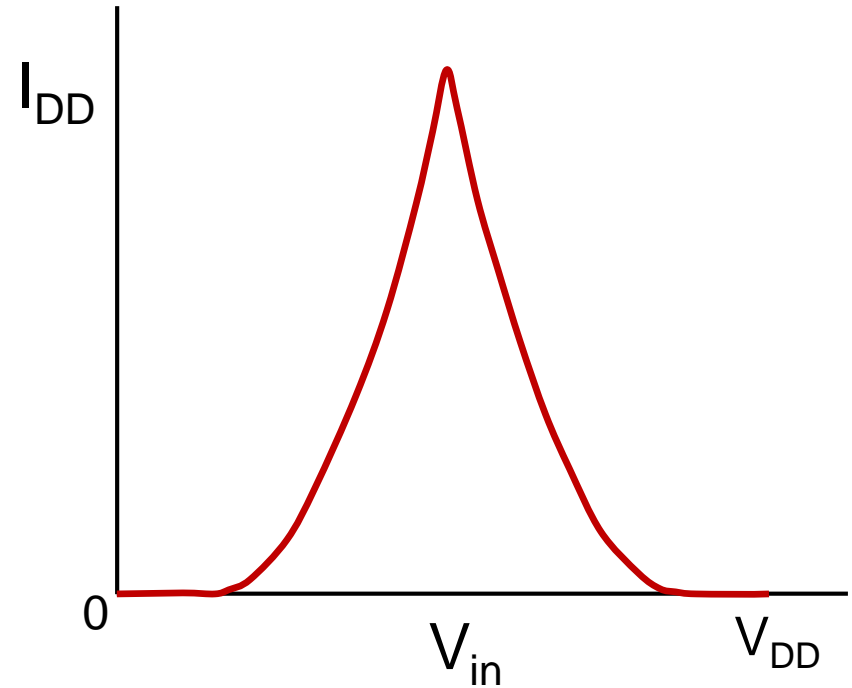
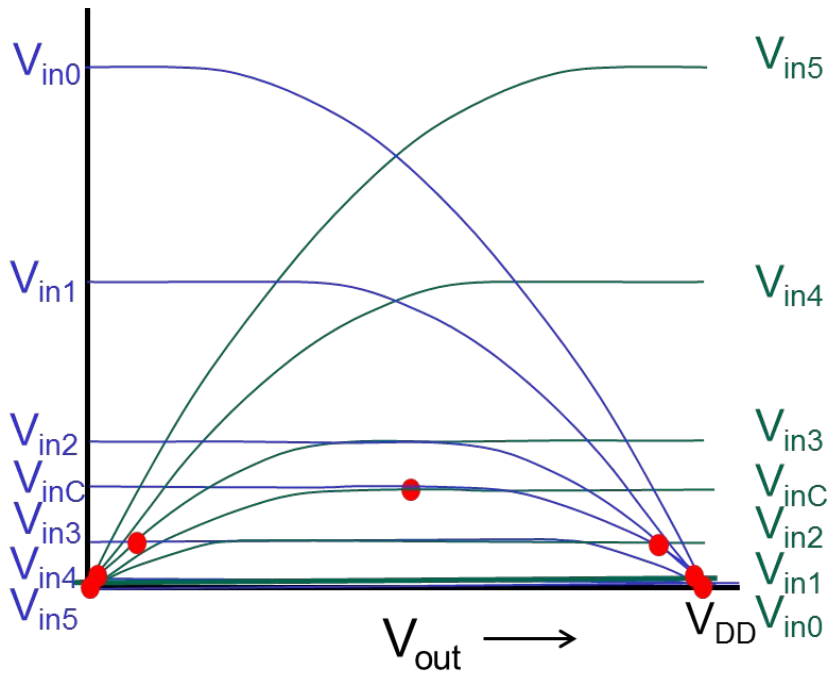


- Zero current when in normal logic range
- Transient current pulse drawn from V_{DD} supply on each switching event


Operating Regions

- Re-visit operating regions

Region	nMOS	pMOS
A	Cutoff	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Cutoff

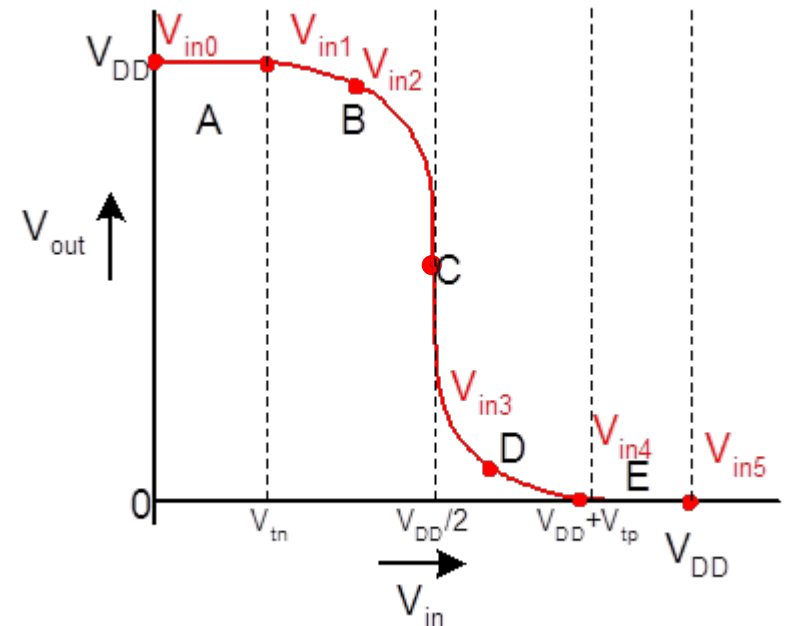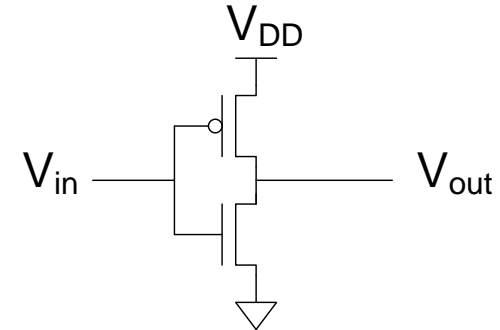


Simulated 65nm DC Characteristic

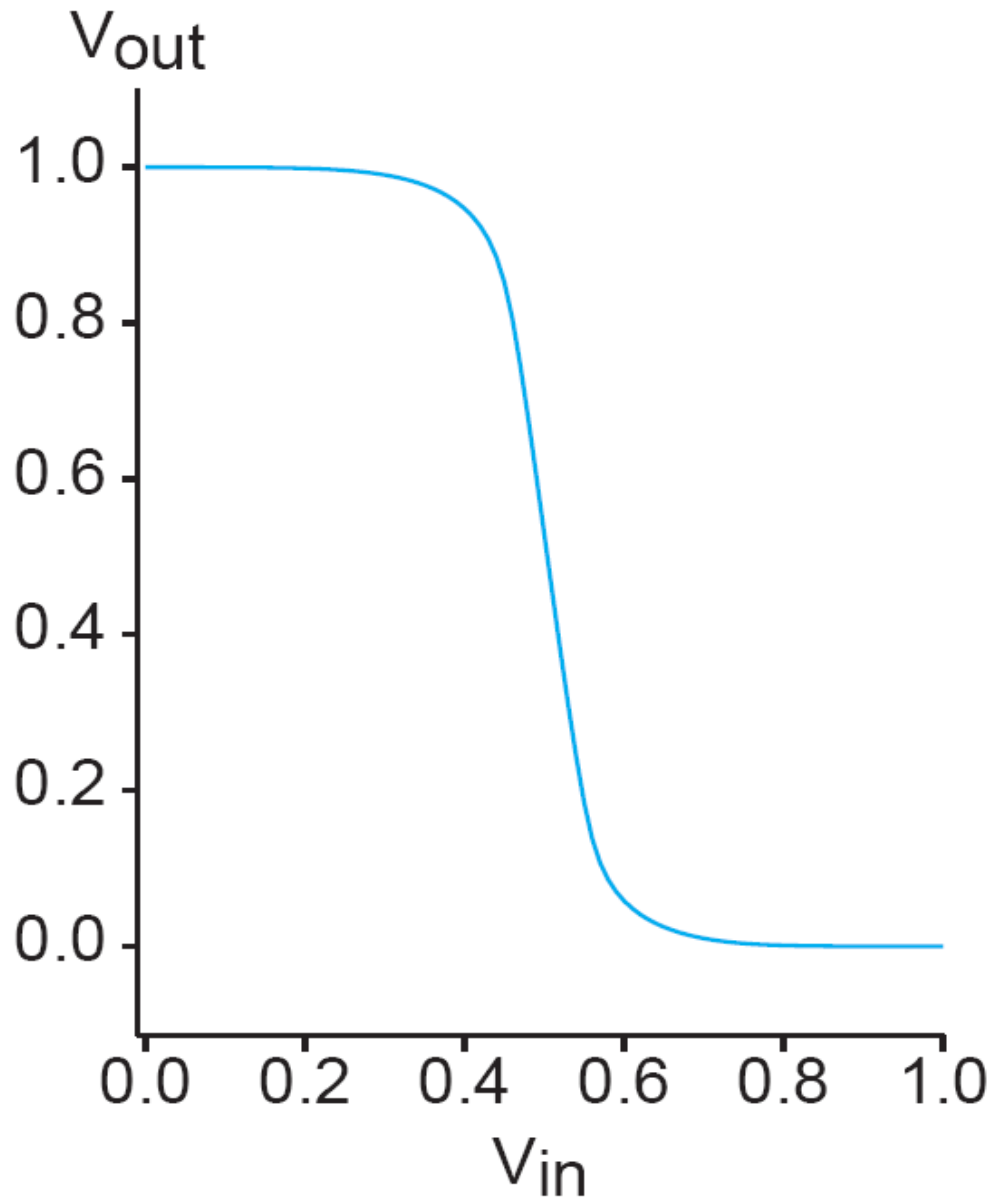


Beta Ratio

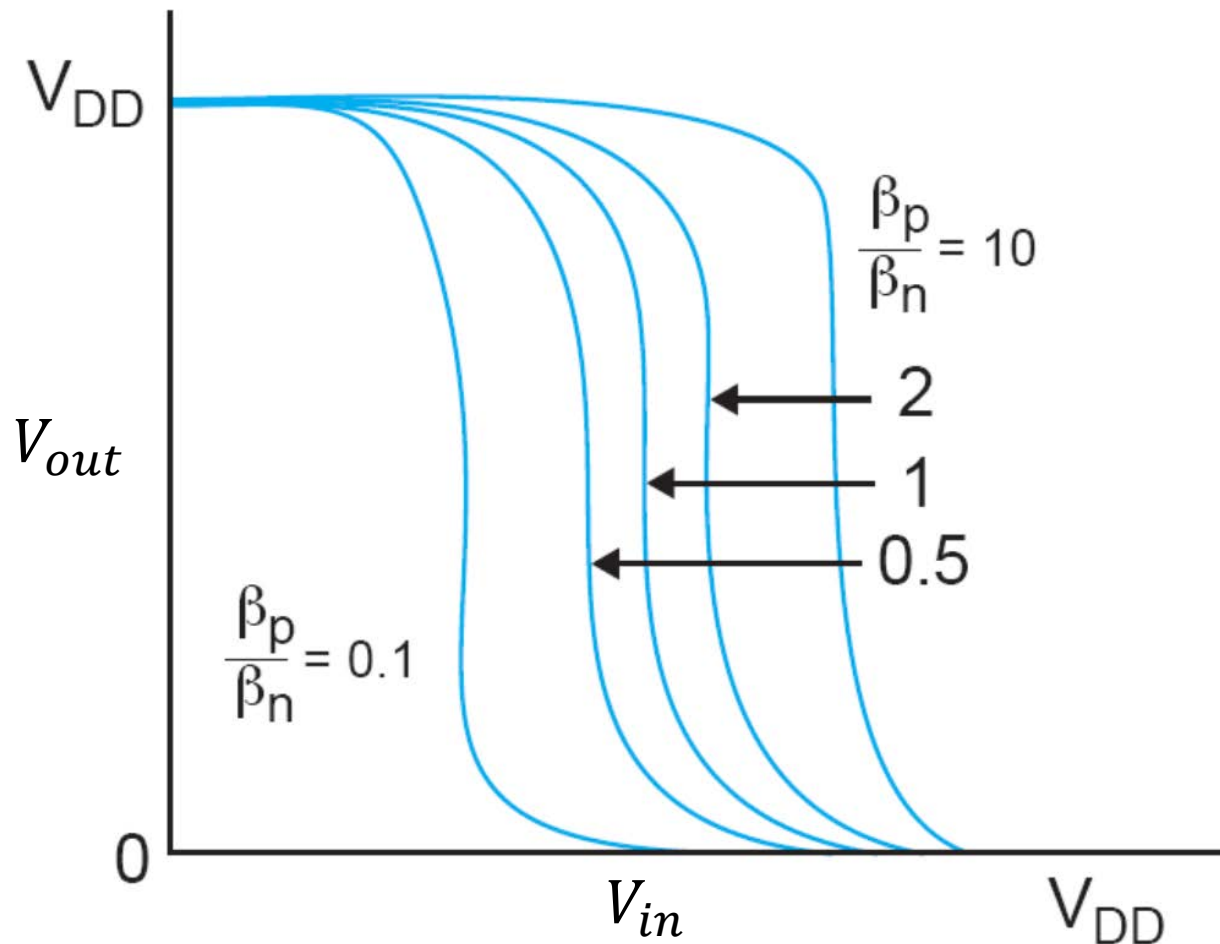- If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- Called *skewed gate*
- Other gates: collapse into equivalent inverter




Restoring Logic

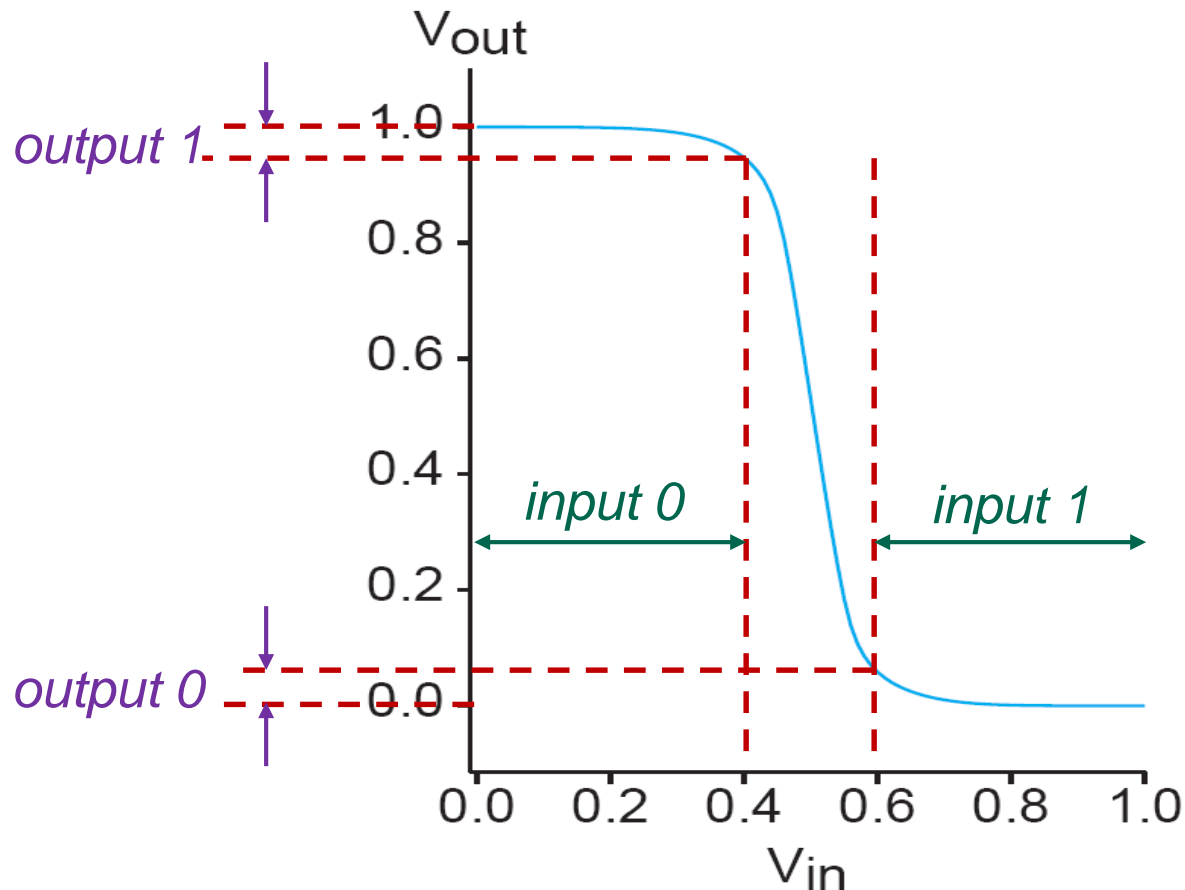- Reason that we can build digital circuits with millions of gates and always get same answer is:
- Most CMOS logic gates are “restoring”
 - output logic level is better than input logic level




Noise Margins

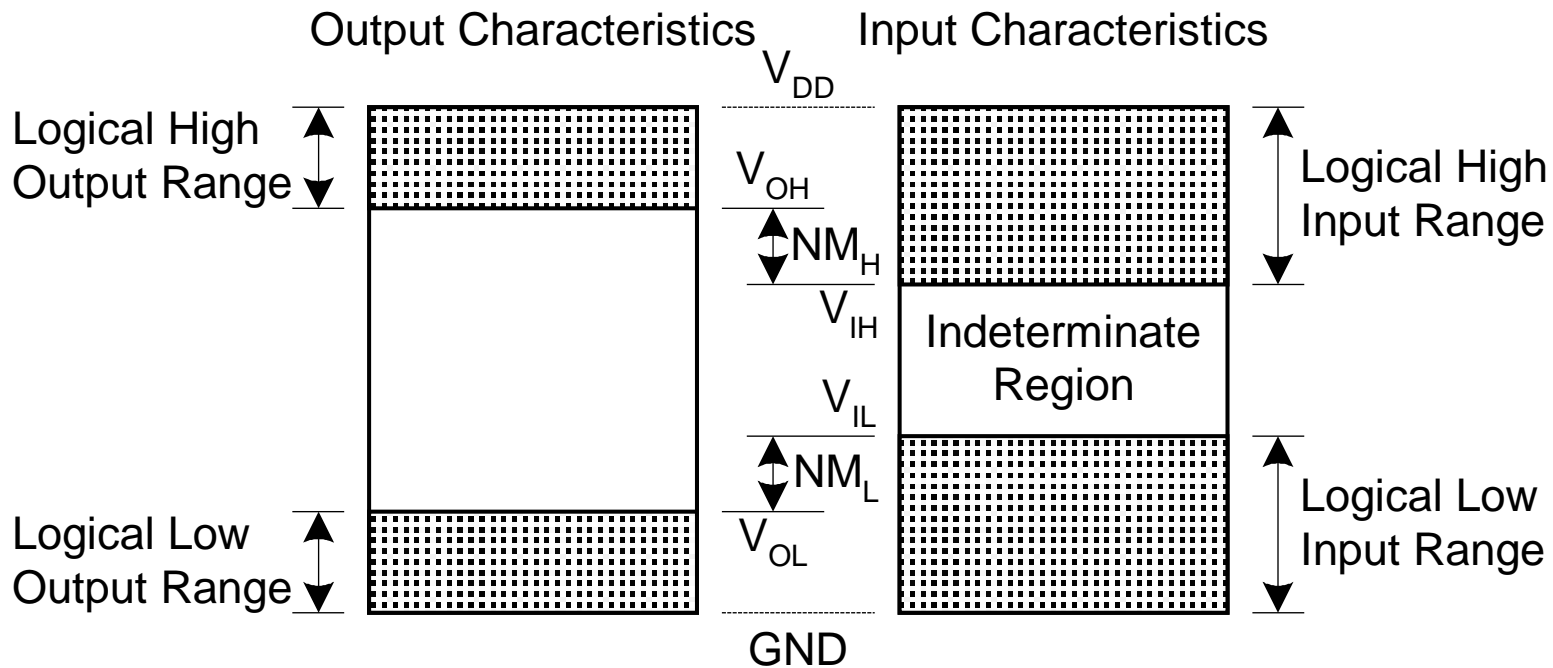- How much noise can a gate input see before it does not recognize the input?




Nominal Logic Levels

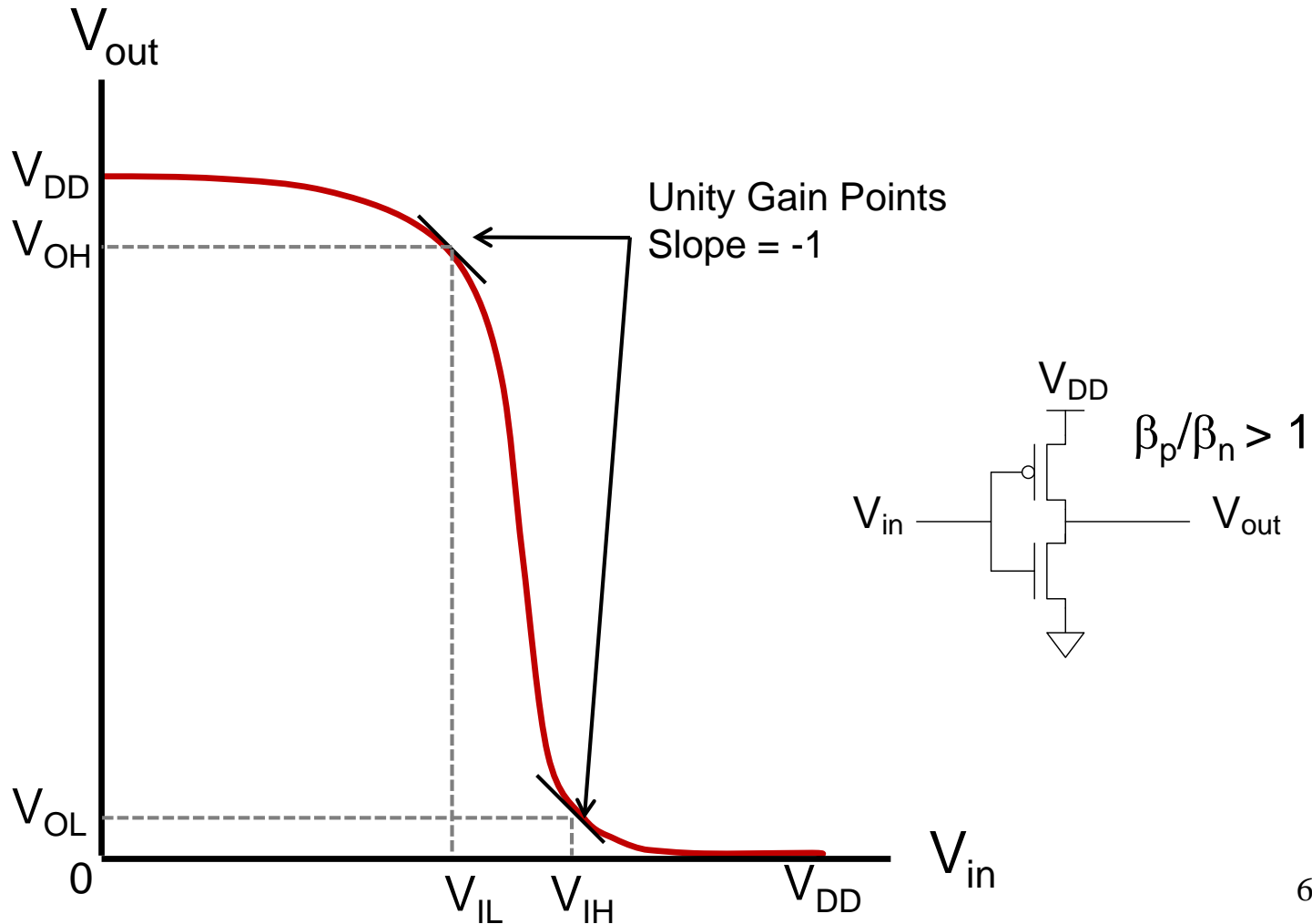- To maximize noise margins, select worst case logic levels at
 - unity gain point of DC transfer characteristic



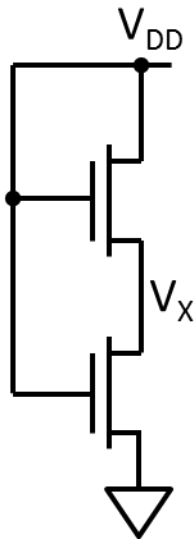Example: MOS IV Formula

Suppose we connect two identical nMOS devices in series between V_{DD} and GND and connect the gates of each to V_{DD} :



Assuming $V_{DD} > V_T$,

1. In which region is the upper transistor operating? Why?
2. In which region is the lower transistor operating? Why?
3. Derive an expression for the voltage V_x at the intermediate node (assume $m=1$).