

CPE 487 Mid-Term Exam

- Friday March 9 @ 10:00 am in:
 - Carnegie 315 (last name A-K)
 - Carnegie 316 (last name L-Z)
- You can use lecture notes, homeworks and Yalamanchili text book
- No cell phones or on-line access

HW4 Solutions 1(a)

```
entity twos_comp is
    Port ( din : in  STD_LOGIC_VECTOR (7 downto 0);
          clk : in  STD_LOGIC;
          dout : out STD_LOGIC_VECTOR (7 downto 0));
end twos_comp;

architecture Behavioral of twos_comp is

begin
    process(clk)
        variable one_test: integer;
    begin
        if clk = '1' then
            one_test := 0;
            for i in 0 to 7 loop
                if one_test > 0 then
                    dout(i) <= not din(i);
                elsif din(i) = '1' then
                    dout(i) <= '1';
                    one_test := 1;
                else
                    dout(i) <= '0';
                end if;
            end loop;
        end if;
    end process;

end Behavioral;
```

HW4 Solutions 1(b)

```
--Inputs
signal din : std_logic_vector(7 downto 0) := (others => '0');
signal clk : std_logic := '0';

--Outputs
signal dout : std_logic_vector(7 downto 0);

type TD is array (1 to 10) of std_logic_vector(7 downto 0);
signal test_data: TD := (X"00", X"01", X"05", X"14", X"76", X"FF", X"F5", X"C3", X"CC", X"86");


BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: twos_comp PORT MAP (
        din => din,
        clk => clk,
        dout => dout
    );


    -- Stimulus process
    stim_proc: process
    begin
        for i in 1 to 10 loop
            din <= test_data(i);
            clk <= '0', '1' after 5 ns;
            wait for 10 ns;
        end loop;
    end process;

END;
```


HW4 Solutions 1(b)

 

HW4 Solutions 2

 

HW4 Solutions 3(b)

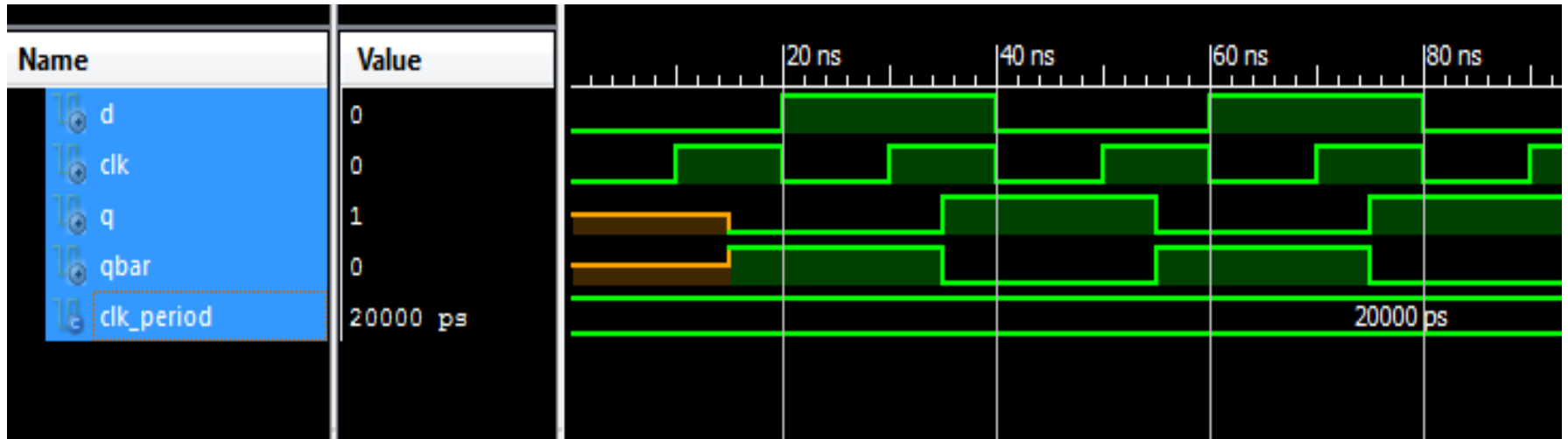

HW4 Solutions 3(b)

```
entity SR4 is
    Port ( clk : in  STD_LOGIC;
          sin : in  STD_LOGIC;
          ZERO: out STD_LOGIC;
          SR  : out  STD_LOGIC_VECTOR (3 downto 0));
end SR4;

architecture Structural of SR4 is

    component dff is
        port(D,clk: in std_logic;
             Q,Qbar: out std_logic);
    end component;
    signal S0, S1, S2, S3: std_logic;
begin
    D0: dff port map(D=>sin, clk=>clk, Q=>S0, Qbar=>open);
    D1: dff port map(D=>S0, clk=>clk, Q=>S1, Qbar=>open);
    D2: dff port map(D=>S1, clk=>clk, Q=>S2, Qbar=>open);
    D3: dff port map(D=>S2, clk=>clk, Q=>S3, Qbar=>open);

    ZERO <= NOT(S0 OR S1 OR S2 OR S3);
    |
    SR(3)<=S3;
    SR(2)<=S2;
    SR(1)<=S1;
    SR(0)<=S0;
end Structural;
```

HW4 Solutions 3(b)

