

## Lecture 12





# VHDL Synthesis

Bryan Ackland

Department of Electrical and Computer Engineering


Stevens Institute of Technology

Hoboken, NJ 07030

   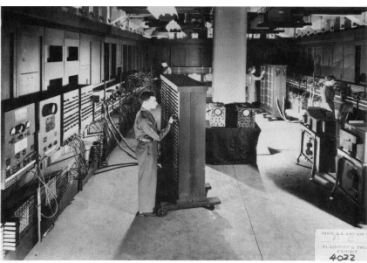

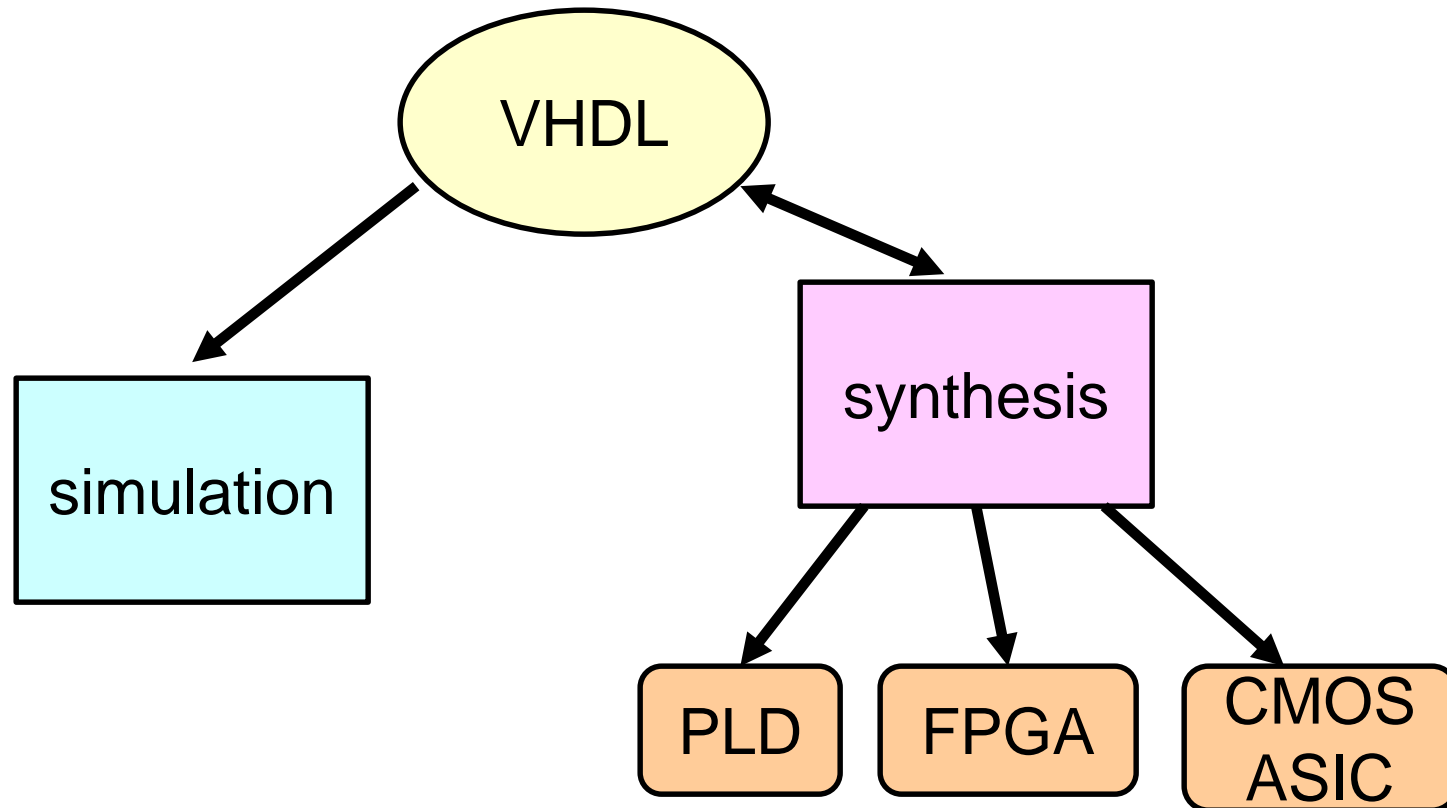
# What is Synthesis?

- Process of creating a RTL or gate level net-list from a VHDL model
- Net-list can be used to create a physical (hardware) implementation



# Synthesis Process

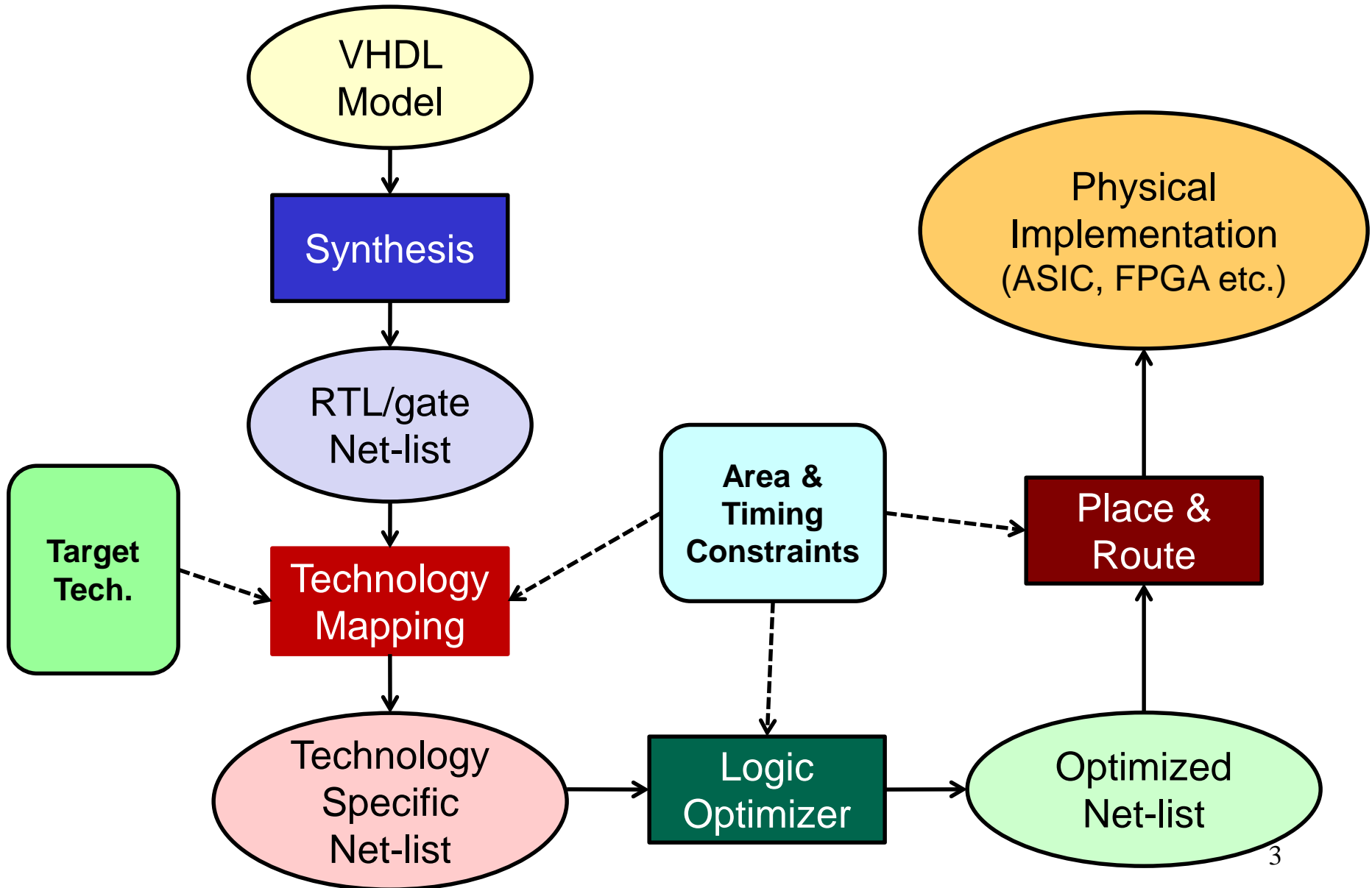

# Limitations of Synthesis

- VHDL can model a hardware system at different levels of abstraction from gate level up algorithmic level
- Synthesis tools cannot, in general, map arbitrary high level behavioral models into hardware.
- Many VHDL constructs have no hardware equivalent:
  - wait for 10 ns;**
  - signal a1: real;**
  - y<= x'last\_value;**
  - assert a=b report “mismatch” severity error;**
- Even if VHDL code is synthesizable, it may lead to very inefficient (in terms of area, speed) implementation
- In moving from VHDL high level behavioral description to synthesizable VHDL hardware description, designer needs to know:
  - What subset of VHDL is **synthesizable**
  - What hardware is **inferred** by various VHDL constructs

# Example of inefficient synthesis

- 8 x 8 matrix multiply:

```
mpr:  process (A,B) is
```

```
variable sum: integer;
```

```
begin
```

```
  for i in 1 to 8 loop
```

```
    for j in 1 to 8 loop
```

```
      sum:=0;
```

```
      for k in 1 to 8 loop
```

```
        sum := sum + A(i)(k)*B(k)(j);
```

```
      end loop;
```

```
      C(i)(j) <= sum;
```

```
    end loop;
```

```
  end loop;
```

```
end process;
```

Uses: 512 multipliers  
448 adders

# Inference

- Synthesis is the process of hardware [inference](#) followed by [optimization](#)
- The synthesis compiler [infers](#) hardware structures from your VHDL code
- Those hardware structures are subsequently [optimized](#) to meet your area and/or speed constraints.
- Part of being a good synthesis designer is being able to put yourself in the place of the compiler and understand what hardware constructs are likely to be inferred from your code.

# Inferring Hardware from VHDL Code

```
entity synth is  
port(A,B,C,D: in integer;  
      sel: in std_logic_vector(1 downto 0);  
      Z: out integer);
```

```
architecture behavioral of synth is  
begin
```

```
  with sel select  
  Z <= A+B when "00"  
  C+D when "10"  
  0 when others;  
end architecture behavioral;
```

- We need an adder (and a multiplexer).
  - How large (how many bits) should the adder be?
  - Integers can be up to 32 bits
  - What if A,B,C and D are in the range 0-20?
- Do we need two adders, or can one adder be shared?
  - Are we more concerned with speed or area?

# Inferring Signals



- In regular programming languages, declared variables & constants are used to allocate storage.
- In VHDL, signals are used to represent timed information flow between subsystems.
  - How are signals represented in hardware?
- When synthesizing from VHDL, the basic hardware implementations of signals are:
  - Wires
  - Latches (level sensitive)
  - Flip-flops (edge triggered)
- Signals generated by combinational expressions (where signal value depends only on the current value of the inputs) will infer wires
- Signals generated by sequential expressions (where signal value depends on current and previous value of inputs) will infer latches or flip-flops



# Flip-flop vs. Latch



## Flip-flop

*stores data when  
clock rises*

  
  
## Latch

*passes data when G is high  
stores data when G is low*



# Inference from Declarations

- When a signal is declared, there needs to be sufficient information to determine the correct number of bits

```
signal result: std_logic_vector (12 downto 0);  
signal count: integer;  
signal index: integer range 0 to 18:= 0;
```

```
type state_type is (state0, state1, state2, state3);  
signal next_state: state_type;
```

- How many bits are required to represent *count* ?
  - Compilers are conservative: they will only perform transformations that are guaranteed not to produce incorrect answers
- Initializations are often ignored
  - Need to include run-time initialization in hardware (e.g. reset)
- How many bits are required to represent *next\_state* ?

# Inference from Simple CSA's

*target\_signal* <= *expression*;

e.g.    A <= (B **nand** C) **or** Y **after** 12 ns;

- A simple CSA assigns a value to a target signal that is a function of the present value of the signals in the RHS expression.
  - Whenever an event occurs on any signal in *expression*, *target\_signal* is re-evaluated.
  - no memory of previous values
- The synthesis compiler will infer a combinational circuit
- Delay information (e.g. **after** 12 ns) will be ignored.
- You can control inferred structure by appropriately grouping logic operations into assignment statements

# Logical Grouping

- Use of intermediate signals can be used to infer different logical (RTL) implementations:

```
entity abc is  
port(w, x, y, z: in std_logic;  
      A, B, C: out std_logic);  
end entity abc;
```

```
architecture dataflow of abc is  
signal s1, s2: std_logic;  
begin
```

```
A <= w and x and y and z;
```

```
s1 <= w and x;
```

```
s2 <= y and z;
```




```
B <= s1 and s2;
```

```
s3 <= w and x;
```

```
s4 <= s3 and y;
```


```
C <= s4 and z;
```

```
end architecture;
```

 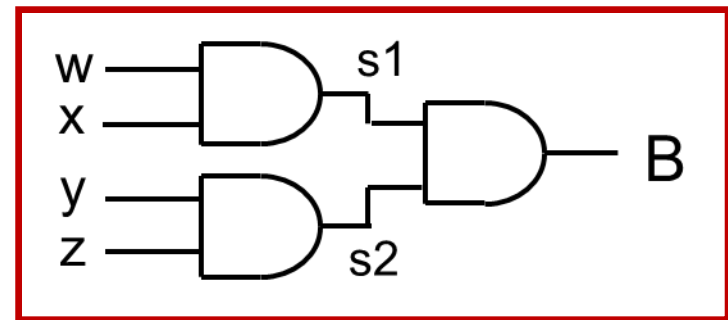 

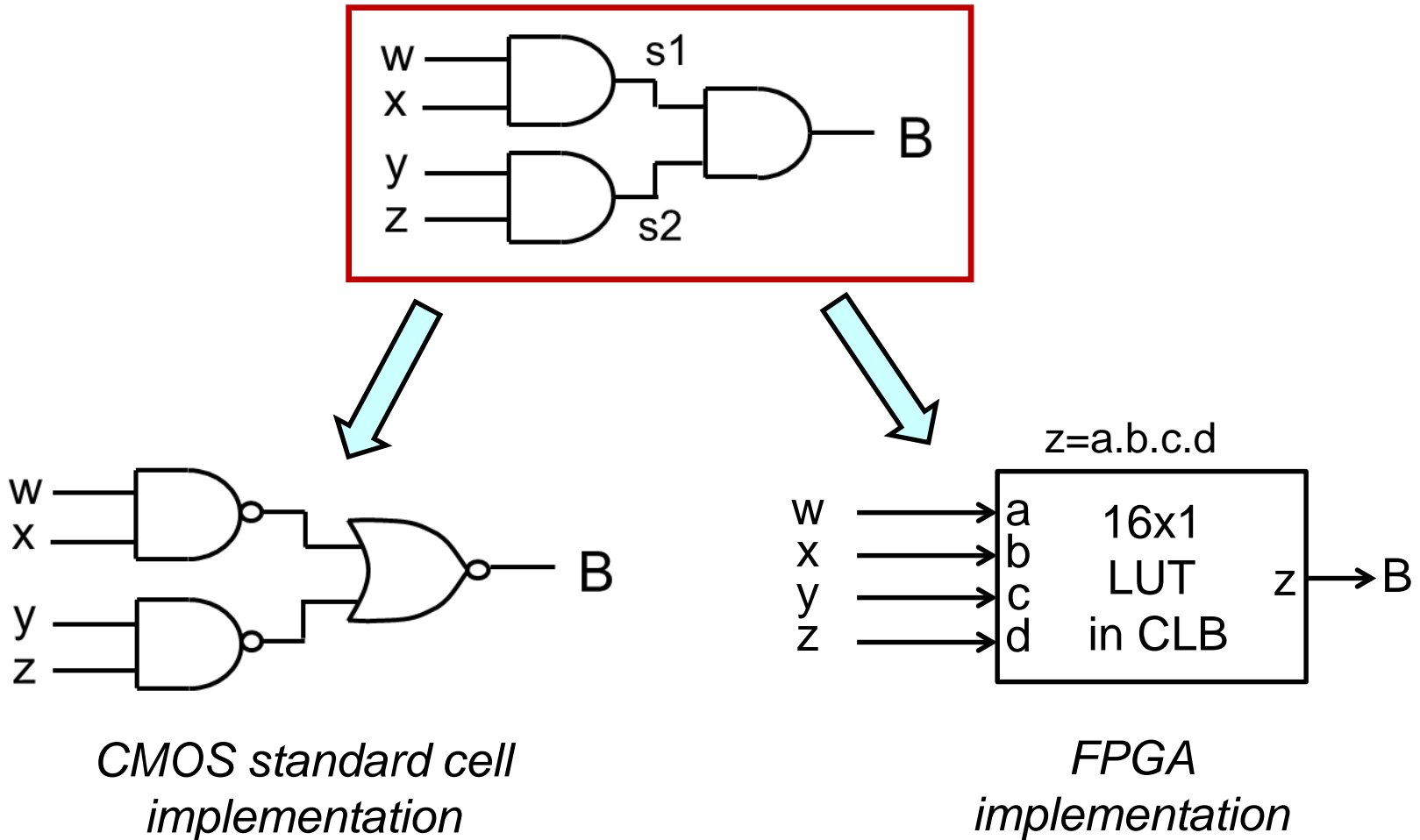
# Logical Grouping Modified by Mapping

- RTL structure may be considerably modified by technology mapping and optimization:



 
# Inference from Conditional Signal Assignment

```
architecture cond_sa of mux is
begin
  z <= a and b when sel='0' else
    a or b;
end cond_sa;
```



*gate-level RTL*

 


*FPGA implementation*
 
# Incomplete Assignment Implies Latch

- What happens if there are combinations of inputs that do not result in an assignment?

```
architecture cond_sa of mux is
begin
    z <= a and b when sel='1';
end cond_sa;
```



- A latch is inferred to cover the case  $sel \neq '0'$ 
  - This is now a sequential circuit – is that what we intended?
- We may not care what the result is when  $sel \neq '0'$
- Result is unnecessary, hazardous hardware
  - If we really wanted sequential operation, better to use flip-flop
- If combinational circuit is intention, make sure output is always assigned a value by using a final *else* clause


# Conditional Maintains Priority Order

- This is great for priority encoder, but what about multiplexer where all conditions are mutually exclusive?

architecture behave of mux4 is begin

```
z <= in0 when sel="00" else  
in1 when sel="01" else  
in2 when sel="10" else  
in3 when sel="11" else  
'0';
```

end behave;

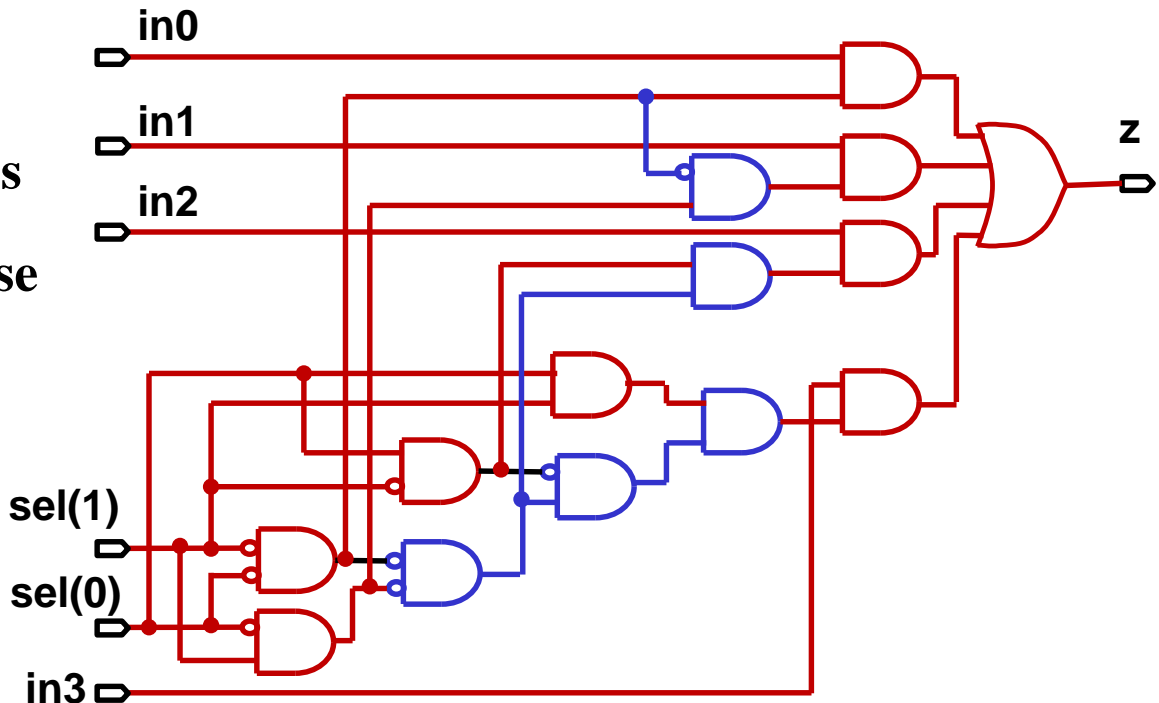


- Only red gates are needed to implement multiplexer
- Blue gates are inferred to maintain priority coding
- Not needed because the clauses are mutually exclusive


 
# Selected Signal Assignment

- SSA is better construct for building a multiplexer
  - No longer implied priority order
  - Clauses are required to be mutually exclusive
  - No redundant gates

```
architecture SSA of mux4 is
begin
  with sel select
    z <= in0 when "00" ,
         in1 when "01" ,
         in2 when "10" ,
         in3 when "11"
         'X' when others;
end SSA;
```




# Inferring Logic from Processes and Variables

- Simple variable assignment statements generate combinational logic
- Sensitivity list is usually ignored by synthesis compiler

```
entity syn_y is  
port ( x,y,z: in std_logic;  
       res: out std_logic);  
end entity syn_v;
```
 
```
architecture behav of syn_v is  
begin  
pr1: process (x,y)  
    variable v1,v2: std_logic;  
    begin  
        v1 := x and y;  
        v2 := v1 xor z;  
        res <= v1 nand v2;  
    end process;  
end behav;
```



# If-then-else Statements

- Like conditional assignment statements, if-then-else statements will generate latches *unless every “output signal” of the statement is assigned a value each time the process executes*
  - One branch of the if-then-else clause must always be taken AND
  - A signal assigned a value in one branch must be assigned a value in all branches.

architecture behav of syn\_if is

**begin**

pr1: **process** (x,y,z,sel)

**variable** v1: std\_logic;

**begin**

**if** sel='1' **then**


            v1 := x **xor** y;

            w <= v1 **and** z;

**end if**;


**end process**;

**end behav**;

 
 
# If-then-else Statements

```
architecture behav of syn_if is
begin
pr1: process (x,y,z,sel)
  variable v1: std_logic;
  begin
    if sel='1' then
      v1 := x xor y;
      w <= v1 and z;
      p <= V1;
    else
      w<=0;
    end if;
  end process;
end behav;
```




# Avoiding latches by “initialization”

- Can ensure that a signal is always assigned in an if-then-else clause by including a final else clause that assigns a default value to all “output signals” of the statement
- Another alternative is to **set a signal to a default value** within the process but before the if-then-else statement:

**architecture** behav of syn\_if is  
**begin**

 
```
pr1: process (x,y,z,sel)
  variable v1: std_logic;
  begin
    w <= '0';
    if sel='1' then
      v1 := x xor y;
      w <= v1 and z;
    end if;
  end process;
end behav;
```


 
# Variables and Inferred Latches

- Can a variable be used in a manner that implies a latch?
- Yes, if in a single active pass through the process a variable is **used before it is assigned**:

```
architecture behav2 of syn_if is
begin
  pr1: process (x,y,z,sel)
    variable v1: std_logic;
  begin
    w <= '0';
    if sel='1' then
      w <= v1 and z;
      v1 := x xor y;
    end if;
  end process;
end behav2;
```




# Case Statement

- Case statement is ideally suited for implementing multiplexers
  - all clauses must be mutually exclusive
  - no implied priority between clauses (unlike if-then-else)
  - no redundant logic
- Need to obey same rules to avoid latches
  - (a) One branch of the case statement must always be true AND
  - (b) If a signal is assigned a value in one branch of a case statement, it must be assigned a value no matter which branch is taken.
 
# 4 input multiplexer

```
architecture behav of syn_mux is
begin
pr1: process (in0,in1,in2,in3,sel)
begin
case sel is
when "00" => z <= in0;
when "01" => z <= in1;
when "10" => z <= in2;
when "11" => z <= in3;
end case;
end process;
end behav2;
```






# Sequential Circuits

- Any moderately complex digital system requires the use of sequential circuits, e.g. to
  - identify and modify current state of system
  - store and hold data
  - identify sequences of inputs
  - generate sequences of outputs
- If and case statements and conditional signal assignments can be used to infer latches
- Latches are not preferred means of generating sequential circuits.
  - A latch is transparent when LE is high – can lead to unintended asynchronous sequential behavior when a result is fed back to an input
  - Latches are prone to generate race conditions
  - Circuits with latches are difficult to verify timing
  - Circuits with latches are difficult to test

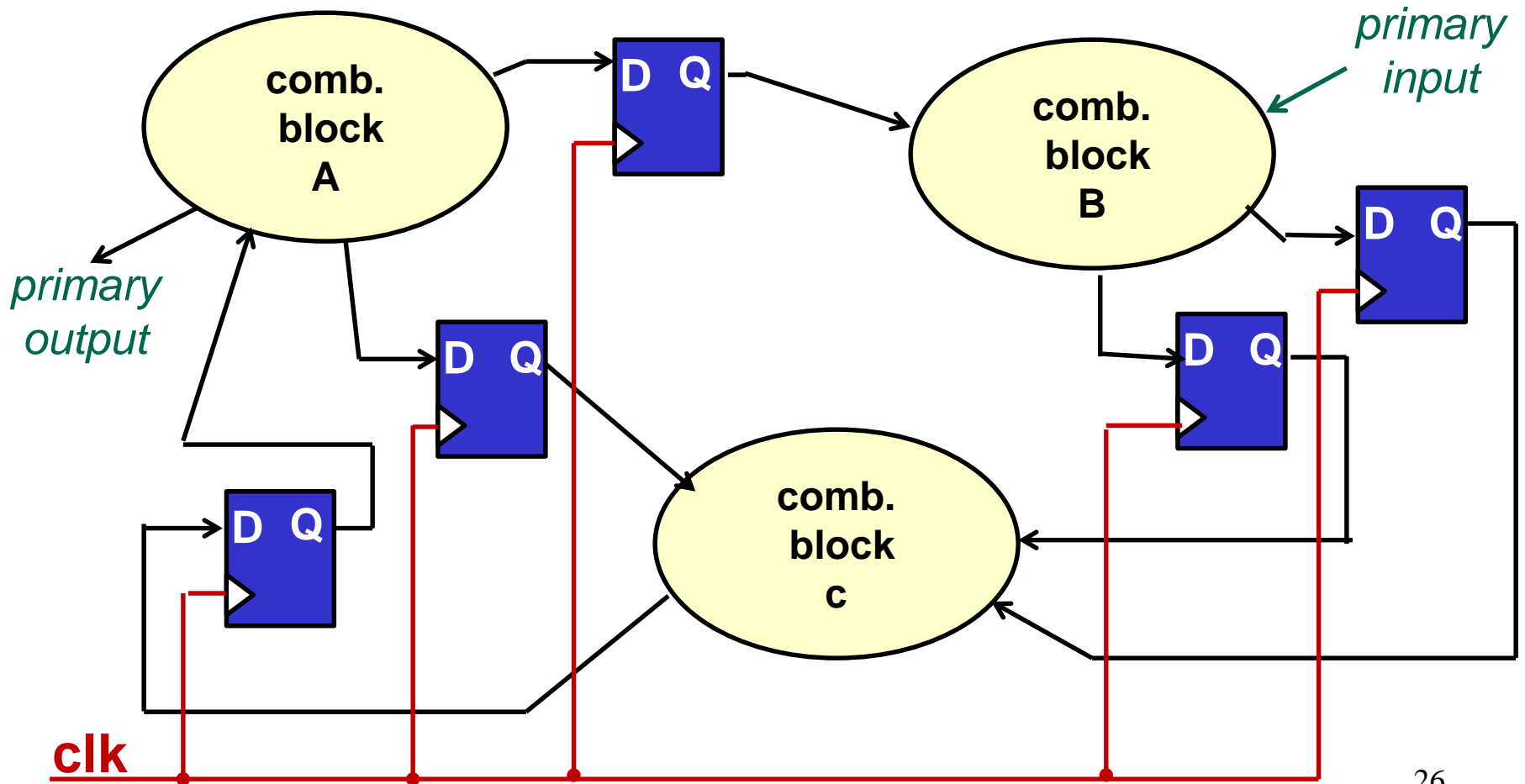
# Synchronous (Single Clock) Digital Design

- Preferred design style is combinational circuit modules connected via positive (negative) edge-triggered flip-flops that all use a common clock.



 
# Finite State Machine

- Single clock synchronous system can be modeled as a single combinational block and a multi-bit register


 
# Advantages of single clock synchronous

- Edge triggered D flip-flops are never transparent
  - no unintended asynchronous sequential circuits
- Timing can be analyzed by:
  - determining all combinational delays
  - just add them up
  - checking flip-flop setup and hold times
- No race conditions
  - only time signal values matter is on clock edge
- Easy to test
- Most real systems, however, cannot be designed using a single clock
  - different timing constraints on various I/O interfaces
  - clock delays across chip
  - goal is to make the single clock modules as large as possible<sup>28</sup>




# D Flip-flop

- Edge triggered D flip-flops are preferred sequential component
- Within a process, positive edge triggered operation is inferred using:

```
if rising_edge (clk) then           -- only with std_logic type  
    if clk'event and clk='1' then
```

- For example:
 
```
architecture RTL of FFS is  
begin  
p0: process (a,b,clk)  
    begin  
        if rising_edge (clk) then  
            z <= a xor b;  
        end if;  
    end process;  
end RTL;
```




# Inferring D Flip-flop with Asynchronous Reset

- Asynchronous reset takes precedence over clock
- Flip-flop can also include asynchronous set

architecture RTL of ARFF is  
begin
 
```
p0: process (a, b, resn, clk)
  begin
    if resn='0' then
      z <= '0';
    elsif rising_edge (clk) then
      z <= a xor b;
    end if;
  end process;
end RTL;
```



# Inferring D Flip-flop with Synchronous Reset

- Synchronous reset waits for clock
- Flip-flop can also include synchronous set

architecture RTL of ARFF is

begin

p0: process (a, b, resn, clk)

begin

if rising\_edge (clk) then

if resn='0' then

z <= '0';

else


z <= a xor b;

end if;

end if;

end process;

end RTL;

 

# Example: 4-bit synchronous counter


```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity count4 is
port( clk, reset: in std_logic;
      count: out std_logic_vector (3 downto 0));
end entity count4;

architecture RTL of count4 is
begin
p0: process (clk, reset)
variable vcount: std_logic_vector (3 downto 0);
begin
    if rising_edge (clk) then
        if reset='1' then
            vcount := "0000";
        else
            vcount := vcount+1;
        end if;
    end if;
    count <= vcount;
end process;
end RTL;
```



# Example: 4-bit synchronous counter


 


# Wait Statement

- Only one wait statement permitted per process
- Must be the first statement in the process
- Must be of the **wait until** form
  - cannot use **wait for** or **wait on** constructs
- Either of these will trigger execution on rising clock edge:
  - wait until** clk'event **and** clk='1';
  - wait until** rising\_edge(clk); -- only with std\_logic type
- A D flip-flop will be inferred for all signals assigned in the process
  - all signals are synchronously assigned in process
  
# Wait Statement - Example

```
architecture RTL of ARFF is
begin
  p0: process
  begin
    wait until rising_edge(clk);
    if resn='0' then
      z <= '0';
    else
      z <= a xor b;
    end if;
  end if;
end process;
end RTL;
```



# Loop Statements

- For loop is most commonly supported by synthesis compilers
- Iteration range should be known at compile time
- While statements are usually not supported because iteration range depends on a variable that may be data dependent.
- Compiler will unroll the loop, e.g.:

```
for k in 1 to 3 loop  
    shift_reg(k) <= shift_reg(k-1);  
end loop;
```


*will be replaced by:*

```
shift_reg(1) <= shift_reg(0);  
shift_reg(2) <= shift_reg(1);  
shift_reg(3) <= shift_reg(2);
```
 
# Functions


- Since:
  - functions are executed in zero time and
  - functions do not remember local variable values between calls
- Functions will typically infer combinational logic
- Function call is essentially replaced by in-line code

```
function parity (data: std_logic_vector)
  return std_logic is
  variable par: std_logic := '0';
begin
  for i in data'range loop
    par := par xor data(i);
  end loop;
  return (par);
end function parity;
```



↓ *optimized*
 
```
signal a: std_logic_vector (3 downto 0);
begin
  z <= parity (a);
```




# Procedures

- Like functions, procedures do not remember local variable values between calls
- Procedures, however, do not necessarily execute in zero time
- And procedures may assign new events to signals in parameter list
- Like function, think of procedure calls as substituting the procedure as inline code in the calling process or architecture
- Can include a **wait** statement, but then cannot be called from a process
  - Generally avoid wait statements in a procedure
  - Synchronous behavior can be inferred using if-then-else
- If procedure is called from a process with **wait** statement, flip-flops will be inferred for all signals assigned in procedure
 
# Tri-state Gates

- A tri-state gate is inferred if the output value is conditionally set to **high impedance Z**



| din | en | dout |
|-----|----|------|
| 0   | 1  | 0    |
| 1   | 1  | 1    |
| X   | 0  | Z    |

# Examples of Tri-state Gates

architecture RTL of STATE3 is

**begin**

**seq0 : process** (Din, EN)

**begin**

**if** (EN = '1') **then**

Dout(0) <= Din(0) **xor** Din(1);

**else** DOUT(0) <= 'Z';

**end if;**

**end process;**

**seq1 : process** (EN, Din)

**begin**

**case** EN is

**when** '1' => Dout(1) <= Din(2) **nor** Din(3);

**when others** => Dout(1) <= 'Z';

**end case;**

**end process;**


Dout(2) <= Din(1) **nand** Din(2) **when** EN = '1' **else** 'Z';

**with** EN **select**

Dout(3) <= Din (3) **when** '1',

'Z' **when others;**

**end RTL;**

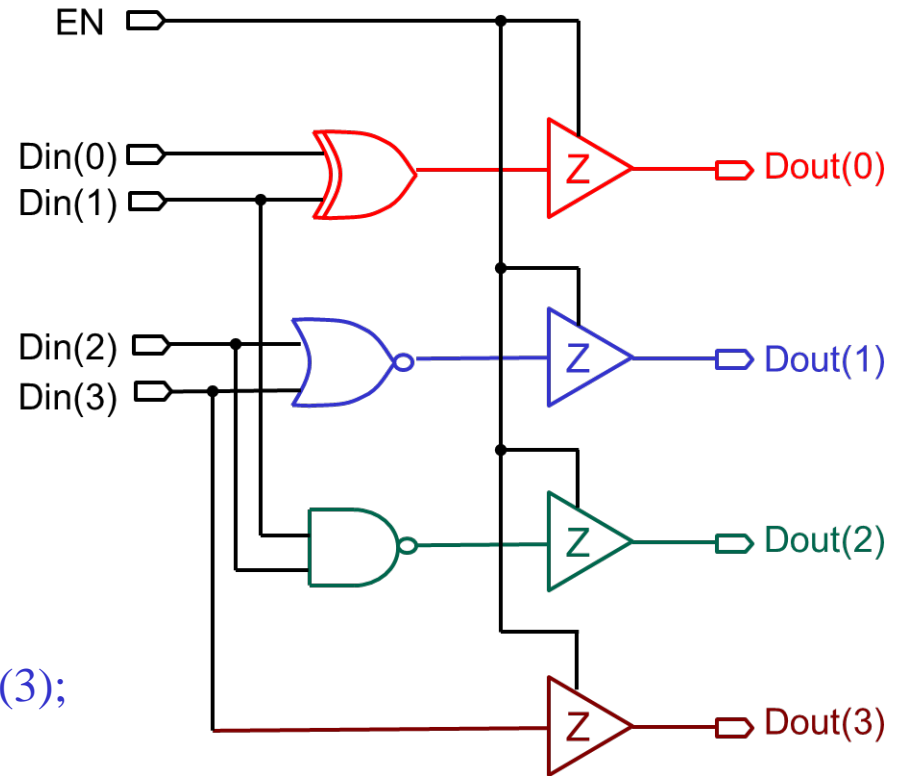



# Think of the Hardware Cost

- Comparison operators like  $=, >, <$  require comparator circuits
- Arithmetic operators like  $+, -, *$  imply adder, subtractor, and multiplier
- Multiplication and division by powers of 2 can be implemented using an arithmetic shift
- Multiplication by simple constants can be accomplished with explicit shift & add (e.g. multiply by 3)
- Order of logic and arithmetic operations:

# Think of the Hardware Cost

- Compare the following:

```
architecture RTL of modX is
signal A1, B1: unsigned(15 downto 0);
begin
  A1 <= A - 1;
  B1 <= B - 1;
seq: process
  begin
    wait until clk;
    case SEL is
      when '0' => DOUT <= A1;
      when '1' => DOUT <= B1;
    end case;
  end process;
end RTL;
```

```
architecture RTL of modX is
begin
seq: process
  variable v1: unsigned (15 downto 0);
  begin
    wait until clk;
    case SEL is
      when '0' => v1:=A;
      when '1' => v1:=B;
    end case;
    DOUT <= v1 - 1;
  end process;
end RTL;
```

# Example: Inferring Synthesis

- Draw the logic inferred by the following VHDL code:

```
entity abc is  
port (  
    A,B, clk, reset: IN bit;  
    C: OUT bit  
);  
end abc;
```

```
architecture RTL of abc is  
signal W, X, Y, Z;  
begin  
    W <= X xor Z;  
    p0: process (clk, A, B, reset)  
    begin  
        X <= '0';  
        if clk='1' then  
            X <= A;  
            Z <= A and B;  
        end if;  
        if reset='0' then  
            Y <= '0';  
        elsif clk'event and clk='1' then  
            Y <= A nor B;  
        end if;  
    end process;  
    C <= W nand Y;  
end RTL;
```

# Summary – Guidelines for Synthesis

- (1) While loop is generally not supported
- (2) All for loops must have statically determined loop ranges
- (3) To avoid a latch being inferred in a conditional CSA, every execution of the statement must assign a value to the target signal
- (4) To avoid a latch being inferred for a signal in a process, every executable path through the process must assign a value to that signal (assign default values before conditionals)
- (5) Using a variable in a process before it is assigned will infer a latch for that variable
- (6) Do not specify initial values for signals
- (7) Include all signals in process sensitivity list to avoid mismatch between pre- and post-synthesis simulation
- (8) All code should infer hardware structure – avoid “algorithmic” descriptions of hardware

# Summary – Guidelines for Synthesis

- 9) If possible, specify data ranges explicitly in declarations
- 10) Minimize signal assignment within a process – use variables
- 11) If you wish to use both combinational and sequential logic in a process, use if-then statements to infer flip-flops rather than wait statement.
- 12) When possible, move common complex operations out of the branches of conditional code and place them after the conditional code. This will generally lead to less hardware
- 13) Use a case statement rather than if-then-else if clauses are mutually exclusive – avoids redundant priority logic
- 14) Avoid level sensitive latches if they are not part of the target technology library