

CPE 487: Digital System Design

Spring 2018

Lecture 2





Digital Logic Basics

Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology


Hoboken, NJ 07030

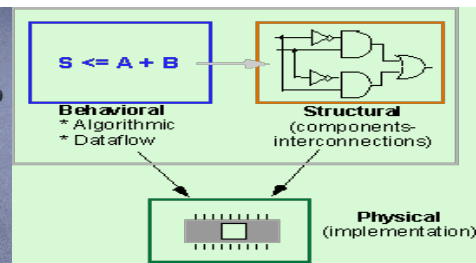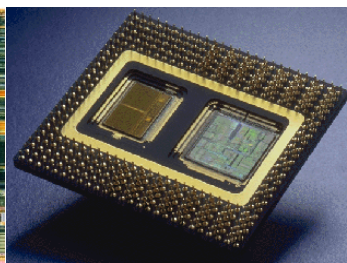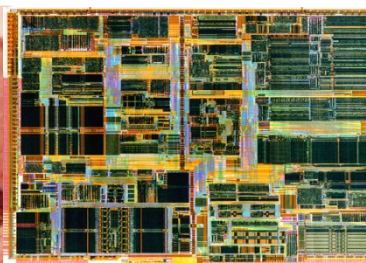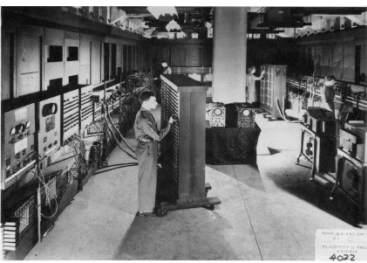

Digital Abstraction

- Most physical variables are **continuous**

 - voltage on a wire
- frequency of an oscillation
- position of a mass




- Computation on continuous variables subject to noise and distortion

- any computation will have finite error
- errors will accumulate

- Digital abstraction considers **discrete subset** of values


 
- output can be “restored” to correct value
- error free (with very high probability)



Digital Discipline: Binary Values

- Early computing engines used multi-value digital variables
 - Babbage engine used gears with 10 different positions
 - Simplified base₁₀ arithmetic
- Very difficult to build electronic circuits that restore to multiple (>2) discrete values
- Very easy to build circuits that restore to two values
- Use two discrete (binary) values: **0** and **1**

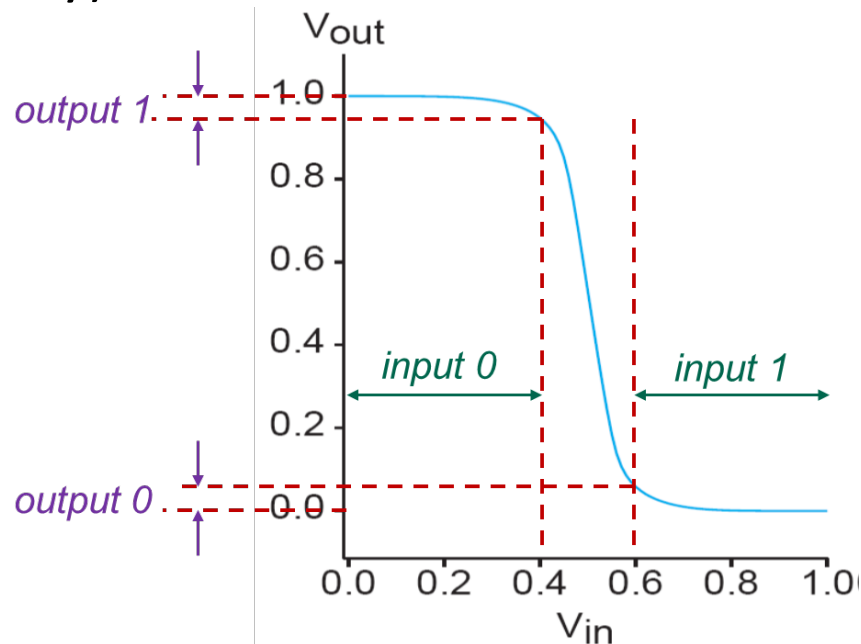 Transfer function of a simple CMOS inverter:



Digital Discipline: Binary Values

- Binary signals can be used to represent logical values:
 - **0** = FALSE **1** = TRUE
- Binary signals can be used to represent numerical values:
 - using base₂ representation
 - each binary signal represents one binary digit (**bit**)
- Binary signals can be used to represent any other variable that can only take on one of two different values
 - e.g. black/white, on/off, up/down
- In digital electronic circuits:
 - **0** is usually low voltage (ground, VSS, 0 volts)
 - **1** is usually high voltage (power supply, VDD, 3.3 volts)
- Beauty of (binary) digital abstraction is that the designer does not need to know the (physical) implementation details
 - can just focus on **0**'s and **1**'s

Formal (Philosopher's) Logic

A: All dogs are warm blooded

B: Molly is a dog

C: Molly is warm blooded

A	B	C
T	T	T
T	F	?
F	T	?
F	F	?

*If (A is true) **and** if (B is true), **then** (C is true)*

What if B is not true. Does that make C false?

e.g. What if Molly is a cat?

Formal logic does not address cases not explicitly covered in the logic statement

Digital (Boolean) Logic

In digital logic, there is always an implied *else* clause

*If (A is true) **and** if (B is true),
then (C is true); **else** (C is false)*

A: If you have come to a complete stop

B: There is no traffic coming

C: You may proceed

*If (A is false) **or** if (B is false),
then (C is false); else (C is true)*


In digital logic, usually use '1' for true, '0' for false

A	B	C
T	T	T
T	F	F
F	T	F
F	F	F

A	B	C
1	1	1
1	0	0
0	1	0
0	0	0

AND gate

logic symbol

 

truth table

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Boolean equation


$$C = A * B$$

or $C = A.B$

When more than two inputs, the output equals '1' *only* when all inputs are equal to '1'

OR gate

logic symbol

 

Boolean equation

$$C = A + B$$


truth table

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

When more than two inputs, the output equals '1'
when any input is equal to '1'

Inverter or NOT gate

logic symbol

 

truth table

A	Z
0	1
1	0


Boolean equation

$$Z = \overline{A}$$


or $Z = A'$

NAND gate

logic symbol

 

equivalent to:

 

Boolean equation

$$C = \overline{A \cdot B}$$

or $C = \overline{A \cdot B}$


When more than two inputs, the output equals '0' *only* when all inputs are equal to '1'

truth table


A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

NOR gate

logic symbol

 

equivalent to:

 

Boolean equation

$$C = \overline{A+B}$$


truth table

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

When more than two inputs, the output equals '0' *when any* input is equal to '1'


XOR and XNOR gate

XOR symbol

 

$$C = A \oplus B$$

XNOR symbol

 


$$D = \overline{A \oplus B}$$

XOR/XNOR truth table

A	B	C	D
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

When more than two inputs, the output of XOR equals '1' *only when an odd number of inputs are equal to '1'*

Creating More Complex Logic Functions

 

$$Z = [(A \cdot B \cdot C) + D] + [D \cdot \overline{(E + F)}]$$

Some Useful Formulae

$$A + '0' =$$

$$A + '1' =$$

$$A + A =$$

$$A + \overline{A} =$$

$$A \oplus '0' =$$

$$A \oplus '1' =$$

$$A \oplus A =$$

$$A \oplus \overline{A} =$$

$$A \cdot '0' =$$

$$A \cdot '1' =$$

$$A \cdot A =$$

$$A \cdot \overline{A} =$$

$$A \oplus B = (A \cdot \overline{B}) + (\overline{A} \cdot B)$$

$$\overline{A \oplus B} = (A \cdot B) + (\overline{A} \cdot \overline{B})$$

Some Useful Formulae

$$A + '0' = A$$

$$A + '1' = '1'$$

$$A + A = A$$

$$A + \overline{A} = '1'$$

$$A \oplus '0' = A$$

$$A \oplus '1' = \overline{A}$$

$$A \oplus A = '0'$$

$$A \oplus \overline{A} = '1'$$

$$A \cdot '0' = '0'$$

$$A \cdot '1' = A$$

$$A \cdot A = A$$


$$A \cdot \overline{A} = '0'$$

$$A \oplus B = (A \cdot \overline{B}) + (\overline{A} \cdot B)$$


$$\overline{A \oplus B} = (A \cdot B) + (\overline{A} \cdot \overline{B})$$

DeMorgan's Theorem
 
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



 
$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



1. Change AND to OR (OR to AND)
2. Invert all inputs
3. Invert output


Example: AOI22

- $Y = A.B + C.D$

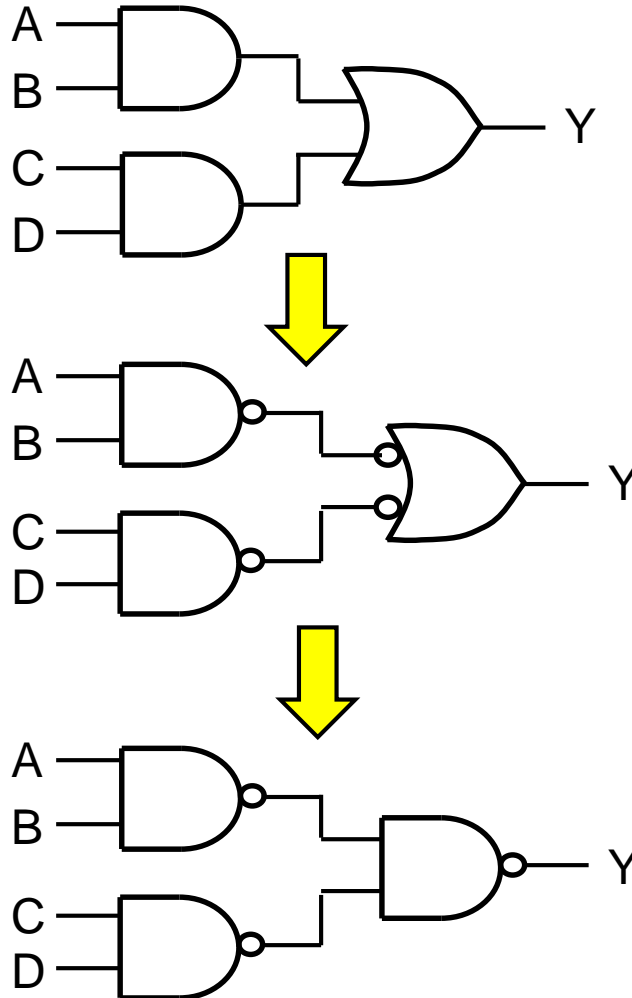


Multiplexer

- $Z = \overline{S}.A + S.B$

 

S	Z
0	A
1	B

 


S	A	B	Z
0	0	-	0
0	1	-	1
1	-	0	0
1	-	1	1

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

4-input Multiplexer

 - $$Z = \overline{S_0} \cdot \overline{S_1} \cdot I_0 + S_0 \cdot \overline{S_1} \cdot I_1 + \overline{S_0} \cdot S_1 \cdot I_2 + S_0 \cdot S_1 \cdot I_3$$



S₁	S₀	Z
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃


- Typically, an 2^N -way multiplexer will use N *select* signals to choose between one of 2^N inputs

Combinational vs. Sequential Logic

- A combinational circuit (logic) is one in which the output depends only on the current value of the inputs
 - All of the logic gates we have described so far (AND, NOR, XOR, multiplexer etc.) are combinational
 - If you know the inputs you know the outputs
- A sequential circuit (logic) is one in which the output depends on the current value and previous values of the inputs
 - Output depends on the sequence of applied inputs
 - Sequential circuits include some form of memory of previous inputs that modify output values
 - We often call these remembered values the state of the circuit or system.
 - All sequential circuits include some form of feedback loop to feed the remembered state back into the inputs of the circuit.

Memory – the cross coupled inverter

 
- Almost all form of digital memory are built around the idea of having two inverters (NOT gates) connected in a feedback loop.



- Positive feedback drives circuit into one of two stable states
- Either: $(Y=1, Z=0)$ *OR* $(Y=0, Z=1)$
 - Circuit will hold state indefinitely
- How do we change the state?

RS Latch

- Simple “writable” storage element

 



Rb	Sb	Q
0	1	0
1	0	1
1	1	<i>no change</i>
0	0	<i>illegal</i>

- Normally, S_b and R_b are both 1
- When $S_b=0$, Q is set to 1
- When $R_b=0$, Q is reset to 0


D Latch

- When Gate = 1, latch is transparent
- D flows through to Q like a buffer
- When gate = 0, the latch is opaque
- Q holds its old value independent of D
- a.k.a. transparent latch or level-sensitive latch

D	Gate	Q
0	1	0
1	1	1
0	0	<i>no change</i>
1	0	<i>no change</i>

  


D Flip-flop

 

clk	D	Q
0	X	no change
1	X	no change
↑	1	1
↑	0	0

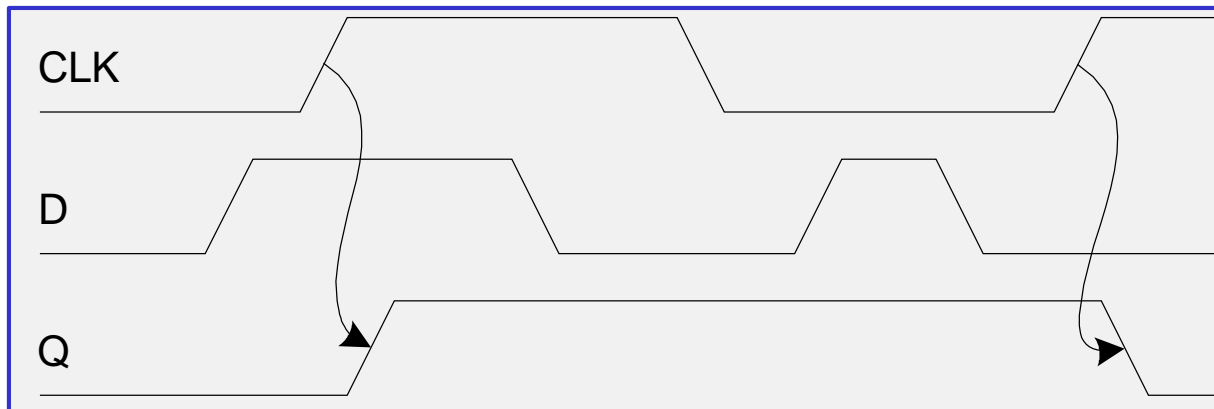- When CLK rises, D is copied to Q
- At all other times, Q holds its value
- a.k.a. edge-triggered flip-flop, master-slave flip-flop



Number Systems

Decimal (base₁₀)

$$A = \sum_{i=0}^{n-1} a_i \cdot 10^i$$

10^2 10^1 10^0

1 **5** **7**

$$= (1 \times 100) + (5 \times 10) + (7 \times 1)$$

Binary (base₂)

$$A = \sum_{i=0}^{n-1} a_i \cdot 2^i$$

2^7 2^6 2^5 2^4 2^3 2^2 2^1 2^0

1 **0** **0** **1** **1** **1** **0** **1**

$$= 128 + 0 + 0 + 16 + 8 + 4 + 0 + 1 = 157_{10}$$

Powers of 2

- $2^0 = 1$
- $2^1 = 2$
- $2^2 = 4$
- $2^3 = 8$
- $2^4 = 16$
- $2^5 = 32$
- $2^6 = 64$
- $2^7 = 128$
- $2^8 = 256$
- $2^9 = 512$
- $2^{10} = 1024$
- $2^{11} = 2048$
- $2^{12} = 4096$
- $2^{13} = 8192$
- $2^{14} = 16384$
- $2^{15} = 32768$
- $2^{16} = 65536$
- handy to memorize up to 2^{10}

Range of Binary Numbers

- N -digit decimal number
 - How many values?
 - Range?
 - Example: 3-digit decimal number:

- N -bit binary number
 - How many values?
 - Range:
 - Example: 3-bit binary number:

Hexadecimal Numbers

- For humans, its clumsy to always work in binary
 - just too many bits!
- Divide a binary number into 4-bit groupings and represent each 4-bits by a single hexadecimal (base₁₆) digit.

Binary:	0010	1001	0101	0111
Hex:	2	9	5	7

- But, in hexadecimal, each digit can have a value of 0 – 15₁₀ !!
- We need new symbols to represent the values 10₁₀ – 15₁₀
- Use symbols A, B, C, D, E and F

Hexadecimal Numbers

Hex Digit	Decimal Equivalent	Binary Equivalent
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

- For example:

$$4AF_{16} =$$

$$0100\ 1010\ 1111_2$$

$$= (4 \times 256)$$


$$+ (10 \times 16)$$

$$+ (15 \times 1)$$


$$= 1199_{10}$$

Bits, Bytes and Nibbles...


- Bits:
(8-bit binary)

 

- Bytes & Nibbles:
(8-bit binary)

 

- Bytes:
(32-bit hex)

 

Addition

- Decimal:

$$\begin{array}{r} 3734 \\ + 5168 \\ \hline \end{array}$$

- Binary:

$$\begin{array}{r} 1011 \\ + 0011 \\ \hline \end{array}$$


- Hex:

$$\begin{array}{r} 1A37 \\ + 09F6 \\ \hline \end{array}$$

Overflow

- Note that if we add two n-bit numbers, we will (in general) get an (n+1) bit result:

$$\begin{array}{r} 1\ 1\ 1 \quad \text{carries} \\ 1\ 0\ 1\ 0 \\ + \quad 0\ 1\ 1\ 1 \\ \hline 1\ 0\ 0\ 0\ 1 \end{array}$$

overflow 

Signed Binary Representation

How do we deal with negative numbers?

Two common approaches:

- Sign-magnitude representation
- Two's complement representation

Sign-Magnitude Representation

- One sign bit plus n-1 magnitude bits
- MSBit is the sign bit:
 - MSB=0 means positive number
 - MSB=1 means negative number

$$A = (-1)^{a^{n-1}} \times \sum_{i=0}^{n-2} a_i \cdot 2^i$$

- *for example, for n=8:*

0 0 0 1 0 1 1 1

$$= +1 \times (0 + 0 + 16 + 0 + 4 + 2 + 1) = 23$$

1 0 0 1 0 1 1 1

$$= -1 \times (0 + 0 + 16 + 0 + 4 + 2 + 1) = -23$$

- n-bit sign-magnitude number can take on values $-(2^{n-1}-1)$ to $(2^{n-1}-1)$

Problems with Sign-Magnitude

1. Addition doesn't work

- for example, 4-bit addition of (-5) and $(+2)$

$$\begin{array}{r} 1\ 1\ 0\ 1 \\ +\ 0\ 0\ 1\ 0 \\ \hline 1\ 1\ 1\ 1 \end{array} = -7_{10} \text{ (incorrect)}$$

2. Two representations of zero (± 0):

0 0 0 0

1 0 0 0

Two's Complement Representation

- MSBit has value (-2^{n-1}) :

$$A = -(a_{n-1} \cdot 2^{n-1}) + \sum_{i=0}^{n-2} a_i \cdot 2^i$$

- for example, $n=8$:

$$2^7 \quad 2^6 \quad 2^5 \quad 2^4 \quad 2^3 \quad 2^2 \quad 2^1 \quad 2^0$$

$$0 \quad 0 \quad 0 \quad 1 \quad 0 \quad 1 \quad 1 \quad 1$$

$$= 0 + 0 + 0 + 16 + 0 + 4 + 2 + 1 = 23$$

$$1 \quad 1 \quad 1 \quad 0 \quad 1 \quad 0 \quad 0 \quad 1$$

$$= -128 + 64 + 32 + 0 + 8 + 0 + 0 + 1 = -23$$

- n -bit two's complement number can take on values (-2^{n-1}) to $(2^{n-1}-1)$

Two's Complement

- To form two's complement (i.e. flip the sign) of number A, *either*
- Working from LSB to MSB, complement (invert) all bits after (to the left of) first '1':
 - e.g. $A = 0101$ ($= 5$)
complementing all bits to left of first '1' (occurs at bit 0):
 - $A = 1011$ ($= -5$)

OR

- Invert all bits in A and add 1:
 - $A = \overline{A} + 1 = 1010 + 1 = 1011$ ($= -5$)


Convenience of Two's Complement

1. MSB still indicates sign

2. Addition *does* work

$$\begin{array}{r} 1\ 0\ 1\ 1 \\ + 0\ 0\ 1\ 0 \\ \hline 1\ 1\ 0\ 1 \end{array} \quad \begin{array}{r} -5_{10} \\ + 2_{10} \\ \hline -3_{10} \text{ (correct!)} \end{array}$$

$$\begin{array}{r} 1\ 0\ 1\ 1 \\ + 0\ 1\ 1\ 1 \\ \hline 1\ 0\ 0\ 1\ 0 \end{array} \quad \begin{array}{r} -5_{10} \\ + 7_{10} \\ \hline +2_{10} \text{ (correct!)} \end{array}$$


 note: throw away
the "overflow" bit

3. Only one representation of zero: 0 0 0 0


Busses

- Frequently useful to group a number of signals into a group as a bus:


– e.g. A is a 16-bit bus:

 

– represented as

 

or

 

- Bus may carry a binary value (with a LSB and a MSB)
- Or just a collection of non-numerically related bits
 - e.g. binary instruction

Registers

- When we want to “remember” an N-bit value...
 - may be numerical value, instruction, code, address etc.
- We often group N D-flip-flops together to capture and store the value on the rising edge of a common clock
- We call this an N-bit **register**
 - e.g. 16-bit register

