

CPE 487: Digital System Design

Spring 2018

Lecture 5






Dataflow Modeling

Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology

Hoboken, NJ 07030

     

Concurrent Signal Assignment


- Simple CSA's execute whenever an event occurs on a signal on the RHS of the assignment statement

$z \leq (a \text{ and } (\text{not } b)) \text{ xor } (c \text{ or } (a \text{ and } (\text{not } d))) \text{ after } 3 \text{ ns};$

target-signal \leq *waveform-elements*;

- Useful for describing gate level combinational logic
 - (when output is a function of current input values only)
- Not suited for modeling at higher levels of abstraction
- Do not capture sequential logic behavior
 - (when output is a function of current & previous input values)

4-way 8-bit Multiplexer

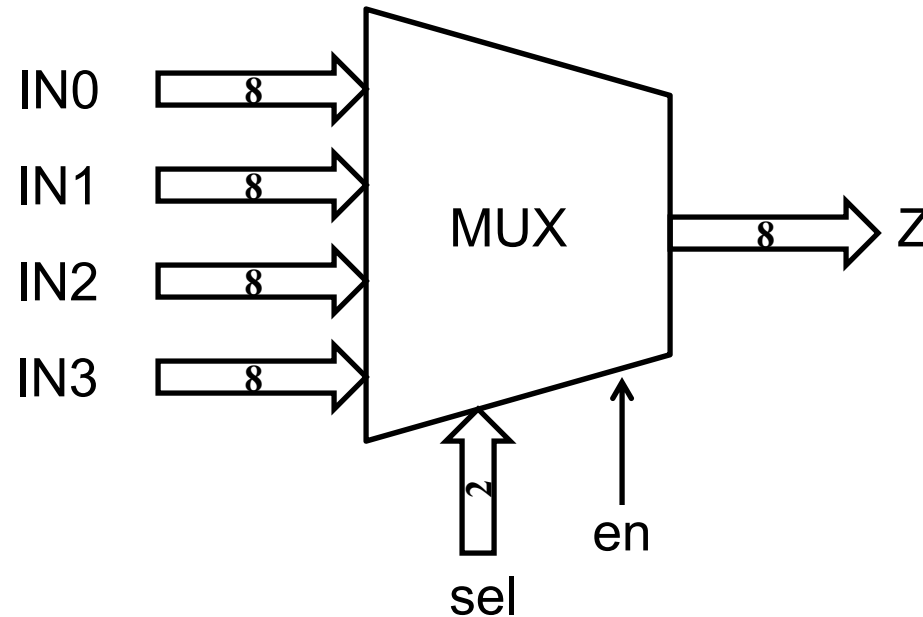

- Using single bit assignment statements, this would require 54 assignment statements!
- Even using 8-bit vectors (`std_logic_vector`) would require 12 statements
- Simplify using conditional expressions

Conditional Signal Assignment Statement

- Conditional signal assignment statement selects different values for the target signal based on the various specified conditions – it is like an **if-then-else** statement.


```
target-signal <= [waveform-elements when condition else]  
                [waveform-elements when condition else]  
                ...  
                [waveform-elements when condition else]  
                [waveform-elements];
```

- Will be executed whenever an event occurs on a signal used in any of the waveform expressions, or in any of the conditions.
- Only the first clause found to be true is executed
 - Order of these clauses matters!


4-way 8-bit Multiplexer

```
library IEEE;  
use IEEE.std_logic_1164.all;  
  
entity mux4 is  
    port ( IN0, IN1, IN2, IN3: in std_logic_vector (7 downto 0);  
          sel: in std_logic_vector (1 downto 0);  
          en: in std_logic;  
          Z: out std_logic_vector (7 downto 0));  
end entity mux4;
```

 
```
architecture behavioral of mux4 is  
begin  
    Z <= "00000000" after 5 ns when en='0' else  
        IN0 after 5 ns when sel="00" else  
        IN1 after 5 ns when sel="01" else  
        IN2 after 5 ns when sel="10" else  
        IN3 after 5 ns when sel="11" else  
        "XXXXXXXX" after 5 ns;  
end architecture behavioral;
```



1-bit Latch

 


din	gate	Q
0	1	0
1	1	1
0	0	<i>no change</i>
1	0	<i>no change</i>

 

- Sequential circuit
- Gate level structure describes a possible implementation but does not explicitly capture behavior

1-bit Latch using Conditional Assignment

 

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
entity latch is  
    port (din, gate: in std_logic;  
          Q: out std_logic);  
end entity latch;
```

```
architecture lat_1 of latch is  
begin  
    Q <= din after 3 ns when gate='1';  
end architecture lat_1;
```

- There are combinations of inputs which will not trigger execution \Rightarrow memory of previous state

Selected Signal Assignment Statement

- Alternative form of conditional assignment
- Selects different values for a target signal based on the value of a select expression.
 - more like a **case** statement.

with *expression* **select**

target-signal <= *waveform-elements* **when** *choices*,
waveform-elements **when** *choices*,

...

[*waveform-elements* **when** *others*];

- Executed when event occurs on any signal in the select expression or on any signal used in any waveform expression.
- Choices must be mutually exclusive
 - all choices are evaluated – order does not matter

Select Signal Assignment: Byte Selector

- Select a specified byte from 32-bit word:

```
library IEEE;
use IEEE.std_logic_1164.all;


entity bytesel is
    port ( din: in std_logic_vector (31 downto 0);
          badd: in std_logic_vector (1 downto 0);
          byte_out: out std_logic_vector (7 downto 0));
end entity bytesel;
```

```
architecture dataflow of bytesel is
begin
```

```
    with badd select
```

```
        byte_out <= din(7 downto 0) after 3 ns when "00",
                din(15 downto 8) after 3 ns when "01",
                din(23 downto 16) after 3 ns when "10",
                din(31 downto 24) after 3 ns when "11",
                "XXXXXXXX" after 3 ns when others;
```

```
end architecture dataflow;
```

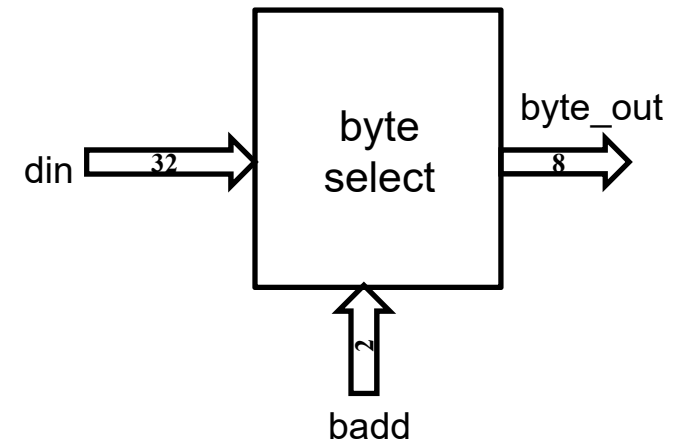

Sidebar: Concatenation Operator

- **&** operator can be used to concatenate a j-bit word and a k-bit word to produce a (j+k) bit word.
- For example:

if a= "0010" and b="1010" and of type std_logic_vector(3 downto 0):

a & b = "00101010"


a & b & a = "001010100010"

a(3 downto 2) & "01" =

b(3) & a(1 downto 0) =

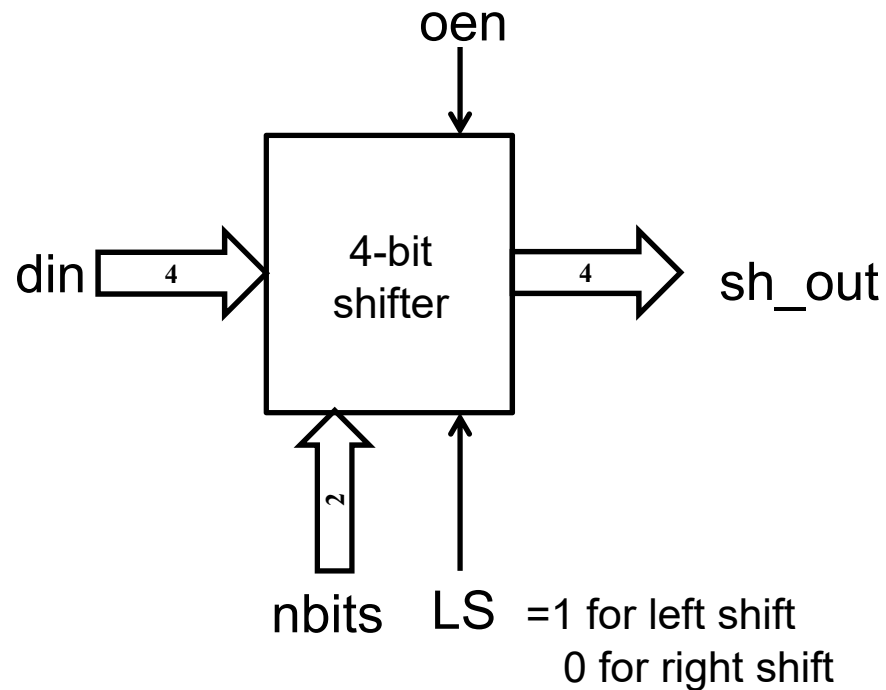Example: 4-bit Logical Shifter

- Use Conditional Signal Assignment to describe a circuit that logically shifts a 4-bit word 0-3 bits to the right or left. Include tri-state output.




Inertial Delay

- By default, gate delays are considered inertial
 - due to intrinsic speed limitation of device
- What happens if a gate sees a very short pulse at its input?
- Inertial delay will filter out pulses shorter than the specified gate delay
 - Default rejection window = gate delay

out1 <= input **or '0' after 8 ns.**

out2 <= input **or '0' after 2 ns.**

 

Inertial Delay with Rejection Window

- We can override default rejection window:

```
z <= reject 3ns inertial (x xor y) after 5ns;
```

- This gate has a delay of 5ns, but will only reject input pulses shorter than 3 ns.
- Inertial delay will also reject output pulses shorter than the reject window.
- For example, using xor gate (above) with following inputs:

```
x <= '0', '1' after 10ns, '0' after 20ns;
```


```
y <= '0', '1' after 12ns, '0' after 18ns;
```

generates no output on z

Transport Delay

- Signals also experience delays through wires
 - Wires can change state very quickly (fast rise & fall time)
 - If wire is long, transport delay can be much greater than the wire rise/fall time.
 - Even a very long wire, may transmit very short pulses (with an appropriate delay)
- Transport delay does not filter out short pulses:



`sum <= transport (x xor y) after 10ns;`

 

Inertial + Transport Delay

```
library IEEE;
use IEEE.std_logic_1164.all;
entity half_adder is
port(a, b: in std_logic;
      sum, carry: out std_logic);
end entity half_adder;

  architecture transport_delay of half_adder is
signal s1, s2: std_logic:= '0';
begin
s1 <= (a xor b) after 2 ns;
s2 <= (a and b) after 2 ns;
sum <= transport s1 after 4 ns;
carry <= transport s2 after 4 ns;
end architecture transport_delay;
```



- Allows us to independently model gate (inertial) and wire (transport) delays



Dataflow Delays

- Dataflow describes process of events flowing from one device to another

$b \leq \text{not } a \text{ after } 2 \text{ ns};$

$c \leq \text{not } b \text{ after } 2 \text{ ns};$

 
 
$d \leq \text{not } c \text{ after } 2 \text{ ns};$



Zero Delays

- What happens when delays are zero?

 
 
e.g.: $b \leq \text{not } a$ after 0 ns; *or* $b \leq \text{not } a$;
 $c \leq \text{not } b$;
 $d \leq \text{not } c$;



- Are these events really happening in zero time?
- What impact does this have on concurrency?

Delta Delays

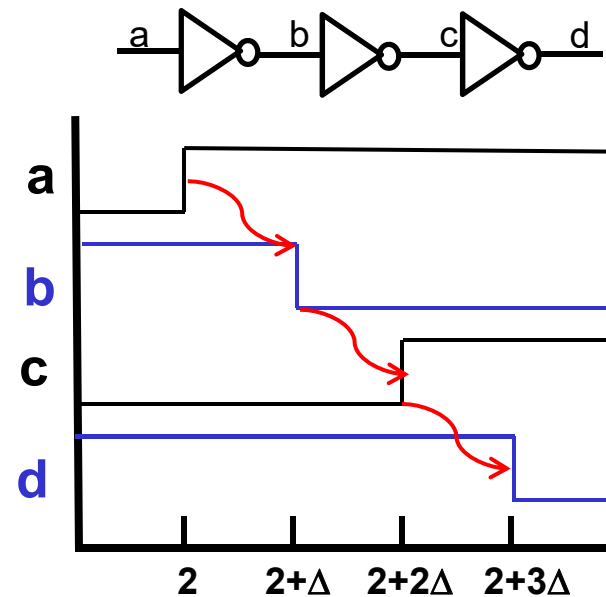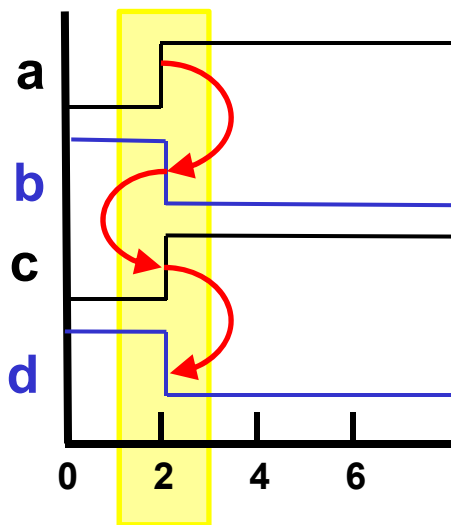- When no delay is specified, simulator adds small (delta) delay Δ when scheduling the output event
- Δ is smaller than any physical delay
 - infinitesimally small but non-zero



- This maintains correct data flow and ensures events processed in correct order
 - without introducing physical delay


Signal Delays - Summary

- VHDL signals do not change instantaneously.
- A scheduled change for a VHDL signal never occurs at the present time but is always delayed until some future time.
 - this is the basis of concurrency
 - execution of one CSA cannot affect the execution of another CSA at the present time
- The future time at which the change is to take affect can be explicitly stated. If no time is specified for a signal change, the default future time is the present time plus an infinitesimally small time called **delta time**.

 Example: Ring Oscillator

- What will happen if the output of the inverter chain is fed back to the input?

$b \leq \text{not } d \text{ after } 2 \text{ ns};$
 $c \leq \text{not } b \text{ after } 2 \text{ ns};$
 $d \leq \text{not } c \text{ after } 2 \text{ ns};$




- What will happen if no delay is specified?

Multiple Drivers

- Each concurrent signal assignment statement creates a driver for the signal being assigned
- Can there be more than one driver for a signal?
 - depends on the type of the signal

`z <= a and b after 10 ns;`

`z <= not c after 5 ns;`

 


- With standard (unresolved) types (e.g. bit, std_ulogic, integer), this is illegal and will cause either a compiler or a run-time error
- With **resolved** types (e.g. std_logic, std_logic_vector) a resolution function is invoked to determine correct result (more on this later).

Std_logic Resolution Table

	U	X	0	1	Z	W	L	H	-
uninitialized	U	U	U	U	U	U	U	U	U
unknown	X	U	X	X	X	X	X	X	X
forcing '0'	0	U	X	0	X	0	0	0	X
forcing '1'	1	U	X	X	1	1	1	1	X
high impedance	Z	U	X	0	1	Z	W	L	H
weak unknown	W	U	X	0	1	W	W	W	X
weak '0'	L	U	X	0	1	L	W	L	X
weak '1'	H	U	X	0	1	H	W	W	X
don't care	-	U	X	X	X	X	X	X	X


Multiple Driver Examples

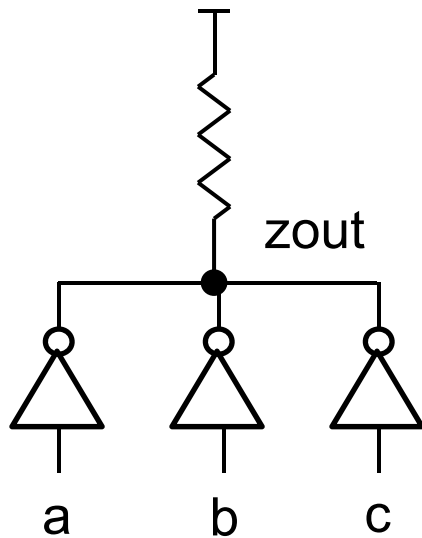

“wired NOR”

signal zout has 4 drivers
(3 open-drain buffers plus a resistor)

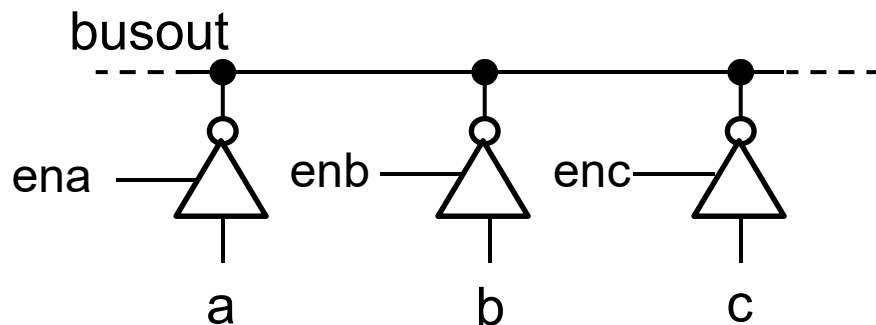buffers output '0' or 'Z'
resistor outputs 'H'



tri-state bus

each buffer outputs '0', '1' or 'Z'
(only one driver active at a time)

Concurrent Assertion Statement

- During simulation and debugging it is useful to be able to check and report on signal values, e.g:
 - Illegal combination of inputs
 - setup or hold time violations
 - unexpected condition
- Assert statement provides mechanism for testing state of system and reporting results on simulator console

```
assert boolean-expression  
[report string-expression]  
[severity expression];
```

- If the value of the *boolean-expression* is false, the report message is printed along with the severity level
 - executed when event occurs on any signal in *boolean-expression*

Severity Levels

- Implementation dependent
- Common values:
 - NOTE
 - WARNING
 - ERROR
 - FAILURE (*this level will abort Xilinx Isim simulator*)

for example:

```
assert (a=b) or (a=c)  
[report “a is not equal to b or c”]  
[severity WARNING];
```

Example: RS Latch


```
entity rsff is
port(rb, sb: in std_logic;
      Q:out std_logic);
end entity rsff;

architecture rsa1 of rsff is
begin
    assert rb='1'
    report "reset initiated"
    severity NOTE;

    assert (rb='1') or (sb='1')
    report "rb and sb both zero"
    severity ERROR;


    Q <= '1' when sb='0' else
        '0' when rb='0';

end architecture rsa1;
```

 

rb	sb	Q
0	1	0
1	0	1
1	1	<i>no change</i>
0	0	<i>illegal</i>

RS Latch: Simulation Output

 

Console

```
# run 1000 ns  
Simulator is doing circuit initialization process.  
Finished circuit initialization process.  
at 10 ns: Note: reset initiated (/rs_assert_tb/uut/).  
at 30 ns: Note: reset initiated (/rs_assert_tb/uut/).  
at 33 ns: Error: Both r and s are zero  
ISim> |
```