

Lecture 6





Behavioral Modeling: Processes

Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology


Hoboken, NJ 07030

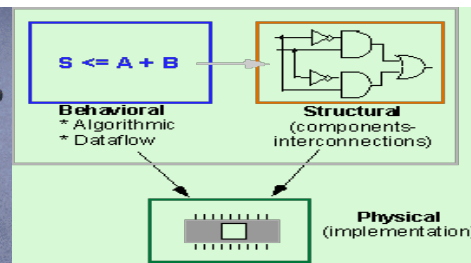  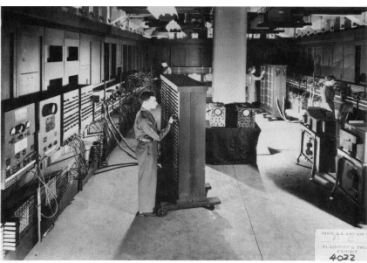

Higher Levels of Abstraction

- Conditional CSA's allow us to move from the gate level to the register transfer level (registers, multiplexers, adders etc.)
- Impractical for higher levels of abstraction where we want to focus on high level function rather than structural implementation.
- For example:
 - 16-bit microprocessor ??
 - or maybe something simpler like a
 - 9-stage, 16 bit FIR filter ??

FIR Filter

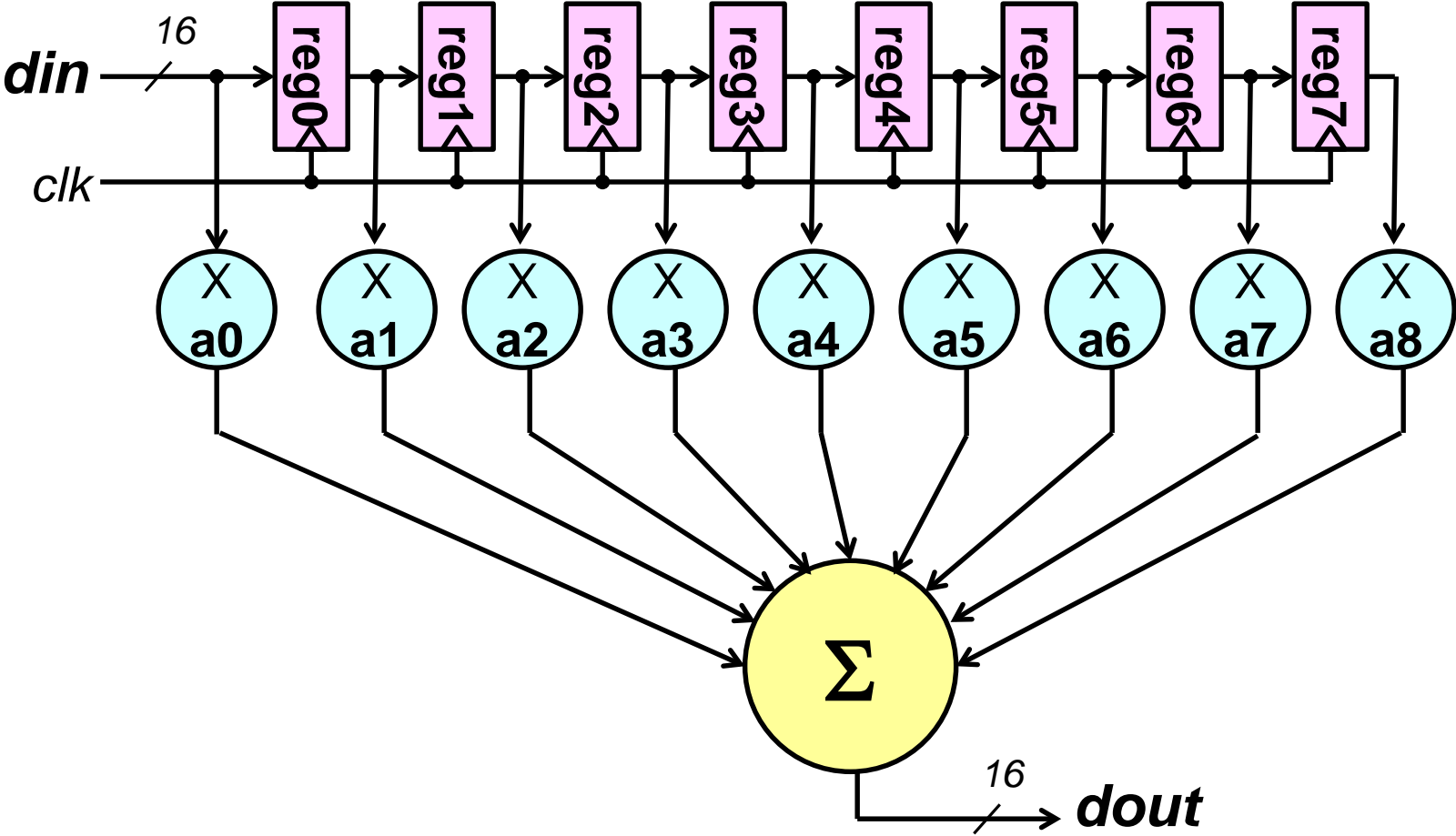

Process Construct

- Sequentially executed block of code
 - much like conventional programming languages
 - executes in zero time
- Supports **variables** as well as **signals**
- Powerful control flow constructs
- More control over when assignments are executed

Process Example

entity NANDXOR is

port (

A, B : **in** std_logic;

C : **in** std_logic;

D : **out** std_logic);

end NANDXOR;

architecture RTL of NANDXOR is

signal T : std_logic;

begin

p0 : T <= A **nand** B **after** 2 ns;


p1 : **process** (T, C)

begin

D <= T **xor** C **after** 3 ns;

end process p1;


end RTL;

 

Sensitivity List

p1 : process (T, C)

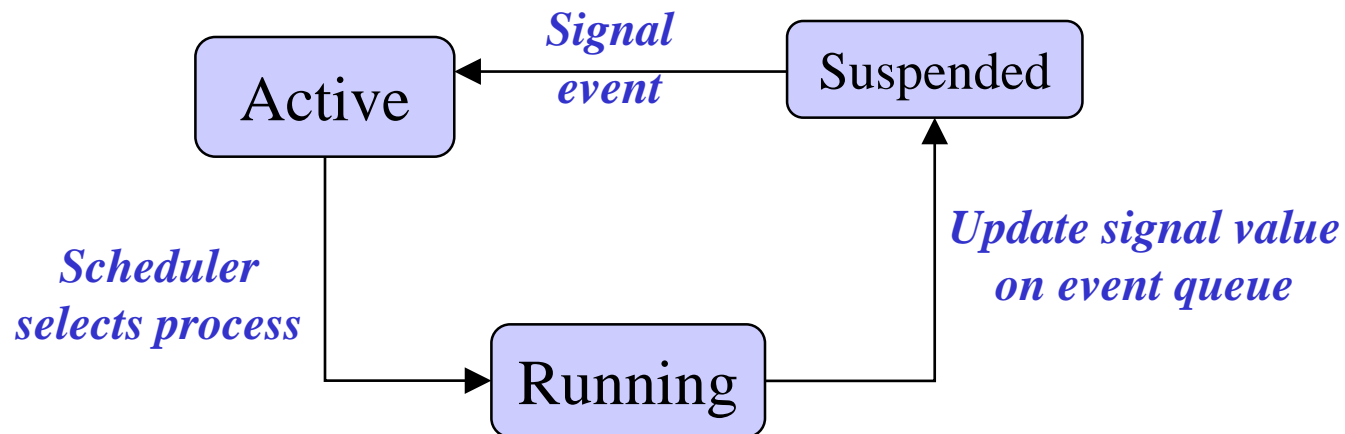- (T,C) is the process sensitivity list of process p1
- A process is executed whenever an event occurs on any signal in the sensitivity list
- Statements in the process are executed sequentially
- Process is then suspended until an event occurs on one of signals in process sensitivity list



Concurrent Signal Assignment or Process?

```
p1 : process (T, C)
  begin
    D <= T xor C after 3 ns;
  end process p1;
```

or

```
p1 : D <= T xor C after 3ns;
```

- These two representations are equivalent!
- CSA's are implemented as processes
- A CSA is a short-hand method of defining a process that schedules events on only one output signal
- Each process can be thought of as a concurrent assignment that can:
 - do complex sequential processing to calculate a result
 - schedule events on more than one signal

Process Programming – If then Else


- An if statement selects a sequence of statements for execution based on the value of a condition (Boolean value).

```
if boolean-expression then  
    sequential-statements  
{ elsif boolean-expression then  
    sequential-statements }  
[else  
    sequential-statement ]  
end if;
```


- Only first clause (boolean expression) found to be true is executed – order of these clauses matters
- Note that **elsif** is one word but **end if** is two words

 Example 8-bit comparator

```
entity cmp_8 is  
  port (  
    a,b: in std_logic_vector (7 downto 0);  
    en: in std_logic;  
    eq: out std_logic);  
end cmp_8;  
architecture behavior of cmp_8 is  
begin  
  cmp_proc : process (a,b,en)  
  begin  
    if en='0' then  
      eq <= '0' after 4 ns;  
    elsif a=b then  
      eq <= '1' after 7 ns;  
    else  
      eq <= '0' after 7 ns;  
    end if;  
  end process cmp_proc;  
end behavior;
```



D Flip-Flop

 

\bar{S}	\bar{R}	clk	D	Q	\bar{Q}
0	1	X	X	1	0
1	0	X	X	0	1
1	1	↑	1	1	0
1	1	↑	0	0	1
0	0	X	X	?	?

- Rising edge triggered sequential circuit
- D flip-flop captures value of D when clk goes from '0' to '1'
- S and R are asynchronous over-riding set and reset
- In order to model, we need to know on which input an event has occurred


Sidebar: Attributes

- Attributes return information about a signal, e.g.:

Attribute	Function
signal_name' event	returns the Boolean value <i>True</i> if an event on the signal occurred at current time, otherwise returns value <i>False</i>
signal_name' active	returns the Boolean value <i>True</i> there has been a transaction (assignment) on the signal at the current time, otherwise returns the value <i>False</i>
signal_name' last_event	returns the time elapsed since the last event on the signal
signal_name' last_active	returns the time elapsed since the last transaction on the signal
signal_name' last_value	returns the value of the signal before the last event occurred on the signal
signal_name' delayed(T)	returns a signal that is the delayed version (by time T) of the original one. [T is optional, default Δ]
signal_name' stable(T)	returns the Boolean value <i>True</i> if no event has occurred on the signal during the interval T, otherwise returns <i>False</i> . [T is optional, default Δ]
signal_name' quiet(T)	returns the Boolean value <i>True</i> if no transaction has occurred on the signal during the interval T, otherwise returns <i>False</i> . [T is optional, default Δ]

Sidebar: Attribute Examples

 $dx \leq$ '0' after 0ns, '1' after 5ns, '0' after 10ns, '0' after 15ns, '1' after 20ns, '0' after 30ns;



dx' event

has the value TRUE at t=10ns

dx' event

has the value FALSE at t=15ns

dx' active

has the value TRUE at t=15ns

dx' last_event

has the value 5ns at t=15ns

dx' last_value

has the value '1' at t=15ns

dx' delayed(8ns)

has the value '1' at t=15ns

dx' stable(8ns)

has the value FALSE at t=15ns

dx' stable(2ns)


has the value TRUE at t=15ns

dx' delayed(8ns)'event

has the value TRUE only at times 13, 18, 28, and 38ns.

 Example: D Flip-Flop

```
entity Dff is
  port (
    clk,D,Rb,Sb: in std_logic;
    Q,Qb: out std_logic);
end entity Dff;
```



```
architecture DA1 of Dff is
begin
  ff_proc: process (clk,Rb,Sb)
  begin
    if Rb='0' then
      Q<='0' after 5ns;
      Qb<='1' after 5ns;
    elsif Sb='0' then
      Q<='1' after 5ns;
      Qb<='0' after 5ns;
    elsif clk'event and clk='1' then
      Q<=D after 7 ns;
      Qb<= not D after 7 ns;
    end if;
  end process ff_proc;
end architecture DA1;
```

Process Programming: Case Statement

- A case statement selects one of several branches for execution based on the value of expression

case *expression* **is**

when *choices* => *sequential-statements*

when *choices* => *sequential-statements*

-- can have any number of branches

[**when others** => *sequential-statements*]

end case;


- The set of *choices* must be mutually exclusive and cover all possible values of the *expression*.
 - Because choices must be mutually exclusive, order of clauses does not matter

Example: 4-way 8-bit multiplexer

```
entity mux4 is
  port ( IN0, IN1, IN2, IN3: in std_logic_vector (7 downto 0);
        sel: in std_logic_vector (1 downto 0);
        en: in std_logic;
        Z: out std_logic_vector (7 downto 0));
end entity mux4;
```

```
architecture using_case of mux4 is
begin
```

```
  P1: process (IN0,IN1,IN2,IN3,sel,en)
  begin
    if en='0' then
      Z<= x"00" after 5ns;
    else
      case sel is
        when "00" => Z<= IN0 after 5ns;
        when "01 "=> Z<= IN1 after 5ns;
        when "10" => Z<= IN2 after 5ns;
        when "11" => Z<= IN3 after 5ns;
        when others => Z<="XXXXXXXX" after 5ns;
      end case;
    end if;
  end process;
end architecture using_case;
```

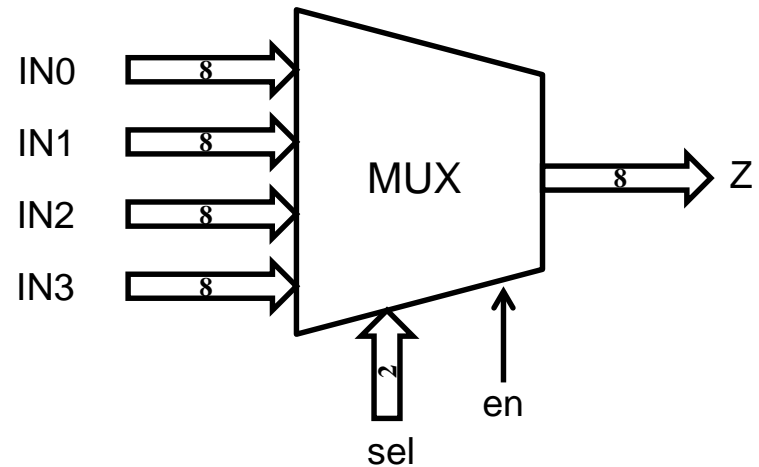

Sidebar: Bit String Literals

- Special forms of string literals that are used to represent binary, octal, or hexadecimal numeric data values. The numerical value is given in double quotes (") and the representation is specified by a character preceding the quoted value.
- The underscore character can be used for convenience and clarity - it does not change the represented value. For example:
 - Binary data: **B**"0110_1101_1111_0010"
 - Octal data: **O**"16_67_62".
 - Hexadecimal data: **X**"6DF2"
 - Binary data: "0010110111110010"
- Note that binary is assumed when no base specified, but underscore cannot be used in this case.

Null Statement

- The null statement is used to explicitly say “do nothing”

Null;

- Particularly useful in case statement when no action is required in response to one of the choices. For example:

```
case sel is  
when “00” =>      Z<= IN0 after 5ns;  
when “01 ”=>     Z<= IN1 after 5ns;  
when “10” =>     Z<= IN2 after 5ns;  
when “11” =>     Null;  
end case;
```

Process Programming: Loop Statement


- The loop statement is used to iterate through a set of sequential statements.

```
[loop-label : ] iteration-scheme loop  
    sequential-statements  
end loop [loop-label];
```

Three types of iteration scheme:

1. **for** *identifier* **in** *range*
2. **while** *boolean-expression*
3. No iteration scheme specified

 Example: 8-stage, 16-bit register pipeline



entity pipe8 is

```
port ( din:in std_logic_vector(15 downto 0);  
      clk:in std_logic;  
      dout:out std_logic_vector(15 downto 0));
```

end entity pipe8;

architecture pipe_be of pipe8 is

```
type sig8x16 is array (0 to 7) of std_logic_vector(15 downto 0);
```

```
signal regfile: sig8x16;
```

begin

```
rproc: process (clk) is
```

```
begin
```

```
  if clk='1' then
```

```
    regfile(0)<=din after 5ns;
```

```
    for i in 1 to 7 loop
```

```
      regfile(i)<=regfile(i-1) after 5ns;
```

```
    end loop;
```

```
  end if;
```

```
end process;
```

```
dout<=regfile(7);
```

```
end architecture pipe_be;
```


Loop Statement: For Iteration

```
[loop-label : ] for index in range loop  
    sequential-statements  
end loop [loop-label];
```

- *index* is implicitly declared in the loop statement
- *index* is local to the loop and read-only
- Loop statement is most powerful when used with **variables** (next lecture)

Multiple Processes: Single-bit ALU

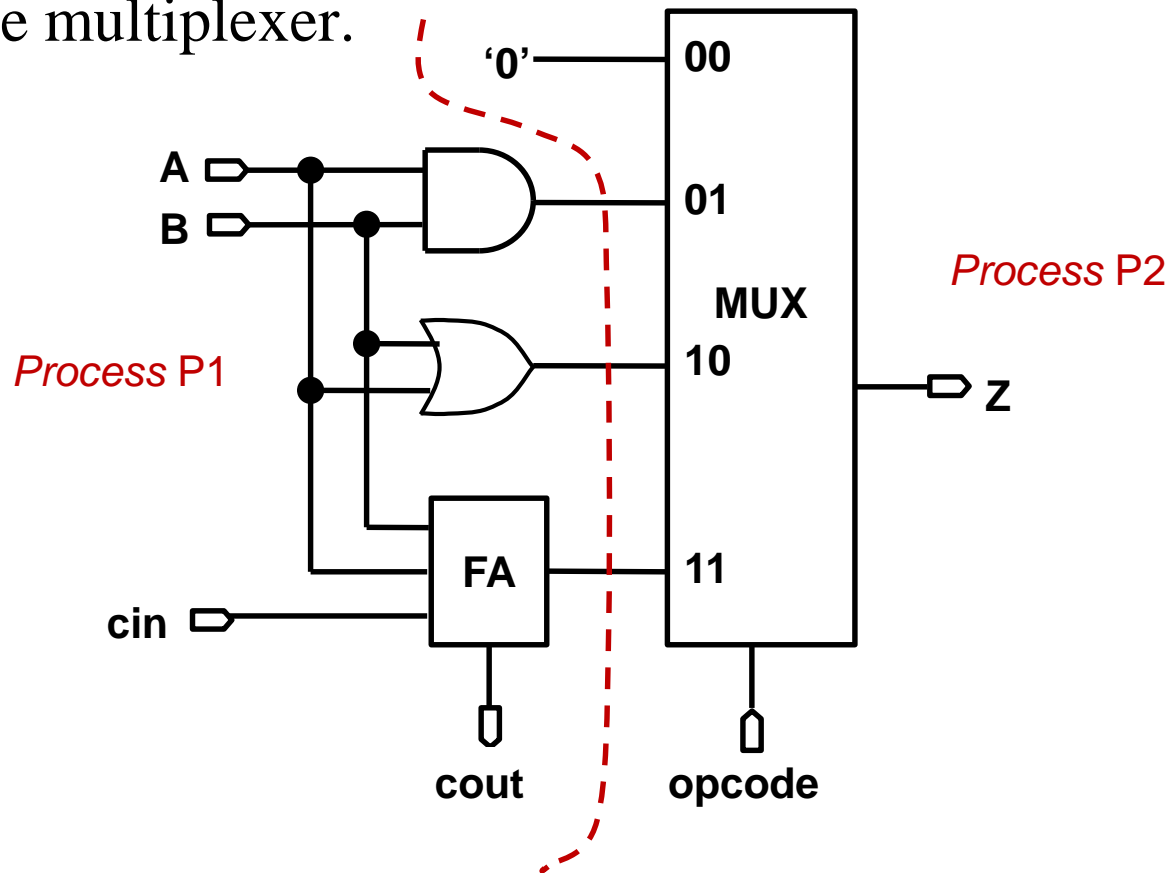Model a single-bit ALU that has four functions: ZERO, AND, OR and ADD selected by a two-bit input opcode. Use two processes: one to describe the basic operations and one to describe the multiplexer.



Example: Register File

Model a register file with sixteen registers, where each register is 32 bits. Implement the register file with two processes: one process reads the register file, while another writes the register file.

The register file has 32-bit `din` and `dout` ports and a 4-bit address port. The read operation should be asynchronous. The write operation should be synchronous, occurring on the rising edge of a write signal.

An enable signal allows expansion of the register file to a larger address range. When the enable signal is 0, `dout` is tri-state (high impedance) and write operations are inhibited.

