

CPE 487: Digital System Design

Spring 2018

Lecture 8





Structural Modeling

Bryan Ackland

Department of Electrical and Computer Engineering

Stevens Institute of Technology

Hoboken, NJ 07030

  
 
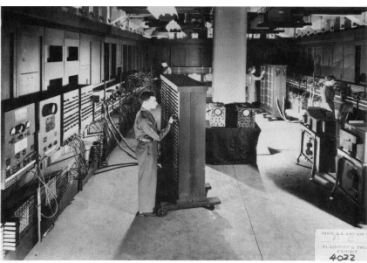


Abstraction & Hierarchy



- In order to create detailed model of a complex system, we need to use abstraction & hierarchy
- Behavioral modeling provides abstraction
 - so far all our models have been described as one **entity**
- Structural modeling supports hierarchy & re-use
- Structural modeling describes physical connection between subsystems whose behavior and/or structure has already been defined
- Structural modeling supports designer directed partitioning of a system
 - important in synthesis
- Structural modeling facilitates sharing and re-use of designs

Building a Structural Hierarchy

- Design a set of components

   

 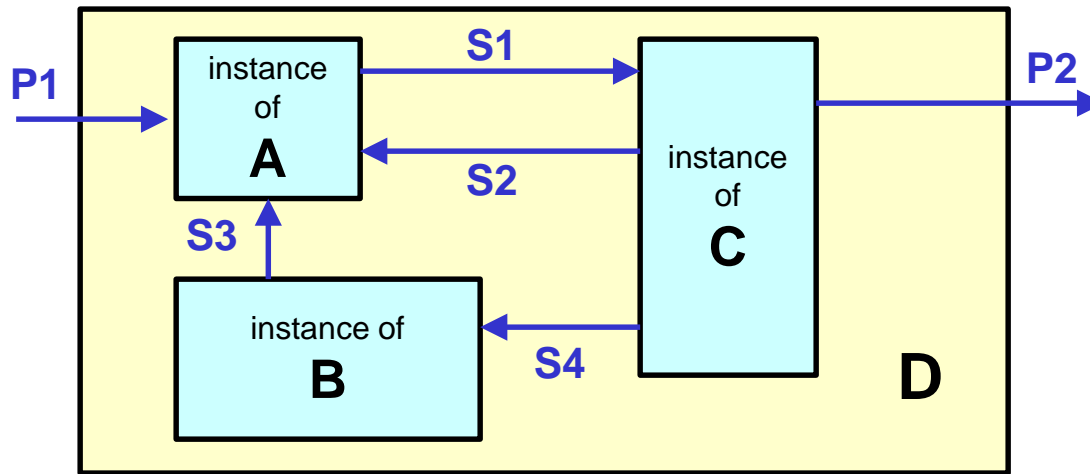- Instantiate these components in a new (higher level) component



- Connect components together with signals

Modeling a Structural Hierarchy

entity D is

```
port(P1:in bit;  
      P2:out bit);  
end entity D;
```

architecture structural of D is

```
component A is  
port(a1,a2,a3:in bit;  
      a4:out bit);  
end component A;
```

```
component B is  
port(b1:in bit;  
      b2:out bit);  
end component B;
```

```
component C is  
port(c1:in bit;  
      c2,c3,c4:out bit);  
end component C;
```

```
signal s1,s2,s3,s4: bit;
```


```
begin
```

```
Inst1: A port map (a1=>P1,  
                  a2=>S2, a3=>S3,  
                  a4=>S1);
```

```
Inst2: B port map (b1=>S4,  
                  b2=>S3);
```

```
Inst3: C port map (c1=>S1,  
                  c2=>S2, c3=>S4,  
                  c4=>P2);
```

```
end architecture structural;
```

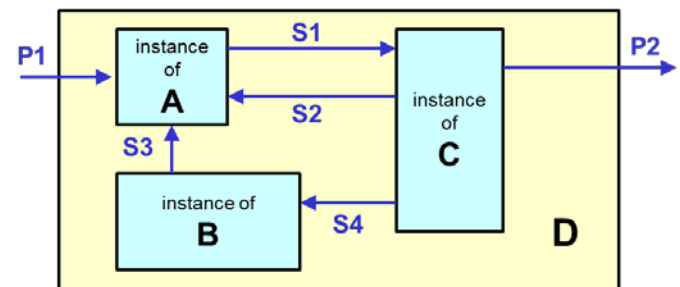

Elements of a Structural Model

1. Ensure you have a behavioral or structural description of each component in the **system**
 - i.e., you have a correct entity-architecture description of each component defined elsewhere (in this or another VHDL file or a package)

2. In architecture of **system**:

architecture arch_name **of** entity_name **is**

-- declare various components

-- declare signals that will interconnect instantiated components

begin

-- instantiate one or more instances of each component using

-- port map to connect component ports to system ports & signals

end architecture arch_name;

Component Declaration

- A component declaration declares the name and the interface of a component.
- It appears in the declarations part of an architecture part, or in a package declaration.

```
component component-name [is
    [port (list-of-interface-ports);]
end component [component-name];
```

- component name and port names & types must match those in original entity description

```
component flipflop
    port(D : IN std_logic;
        clk : IN std_logic;
        Q ,Qb: OUT std_logic);
end component;
```



```
entity flipflop is
    port(D : IN std_logic;
        clk : IN std_logic;
        Q ,Qb: OUT std_logic);
end entity;
```

Component Instantiation


- Defines and labels a specific instance of a declared subcomponent.
- Associates the ports of the entity & the signals of the architecture with the ports of the subcomponent.

Component-label : component-name [**port map**
(association-list)];

- Association-list associates signals in the entity, called **actuals**, with the ports of a component, called **formals**.
(*formal1=>actual1, formal2=>actual2,...*) *--etc.*
- An actual may be the keyword **open** to indicate a port that is not connected.

FF1: flipflop **port map** (clk=>ckin, D=>d3, Q=>dout, Qb=>**open**);

Example: 6-element shift register

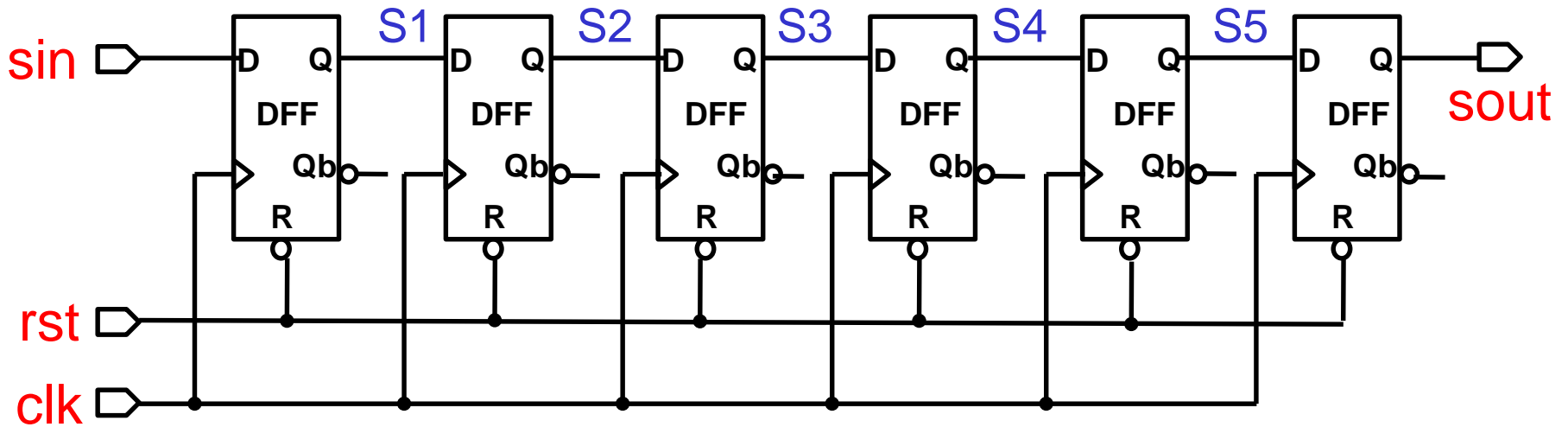

SR6

6-bit SR: DFF component model

entity DFF is

port (

R, ck, D : in std_logic;

Q, Qb : out std_logic);

end DFF;

architecture behave of DFF is

begin

dfp: process (R, ck)

begin

if (R = '0') then

Q <= '0';

Qb <= '1';

elsif (ck'event and ck = '1') then


Q <= D;

Qb <= not D;

end if;

end process;

end behave;

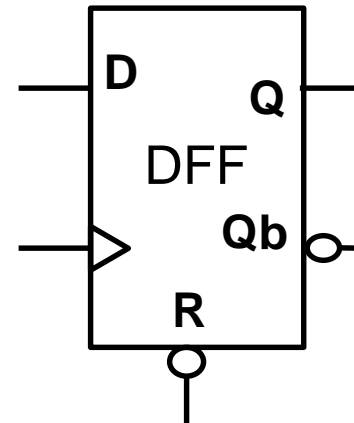

6-bit SR: SR6 declarations

```
entity SR6 is  
  port (  
    rst, clk, si: in std_logic;  
    so: out std_logic);  
end SR6;
```

```
architecture RTL of SR6 is  
  component DFF  
    port (  
      R, ck, D : in std_logic;  
      Q, Qb:out std_logic);  
  end component;
```

```
signal s1,s2,s3,s4,s5: std_logic;
```


```
begin
```



6-bit SR: SR6 declarations

```
bit0 : DFF port map (R => rst, ck => clk, D=>sin, Q=>S1, Qb=>open);  
bit1 : DFF port map (R => rst, ck => clk, D=>S1, Q=>S2, Qb=>open);  
bit2 : DFF port map (R => rst, ck => clk, D=>S2, Q=>S3, Qb=>open);  
bit3 : DFF port map (R => rst, ck => clk, D=>S3, Q=>S4, Qb=>open);  
bit4 : DFF port map (R => rst, ck => clk, D=>S4, Q=>S5, Qb=>open);  
bit5 : DFF port map (R => rst, ck => clk, D=>S5, Q=>sout, Qb=>open);
```

end architecture RTL;

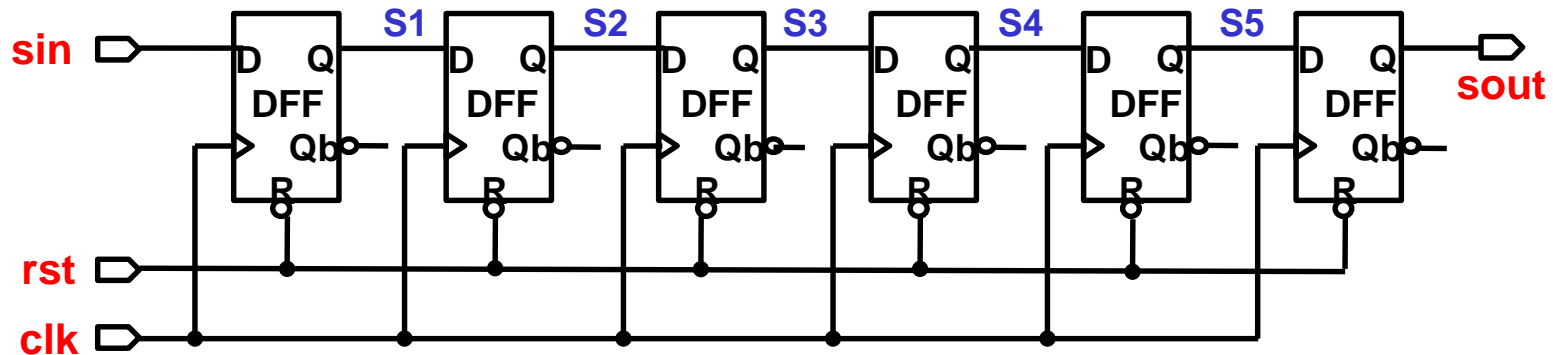

Named & Positional Association

- In previous example, we used **named association**
 - allows associations to be made in any order

(formal1=>actual1, formal2=>actual2,...) --etc.

- Positional association only names actuals in the same order as the formals were listed in the component declaration
 - like order based subroutine parameter passing in conventional programming languages

(actual1, actual2, actual3...) --etc.

- less verbose, but more prone to error

Named & Positional Association

- Component declaration:

```
component DFF port (  
R, ck, D : in std_logic;  
Q, Qb:out std_logic);  
end component;
```

- Component instantiation – named association

```
bit0: DFF port map (ck=>clk, R=>rst, D=>sin, Q=>S1, Qb=>open);
```

- Component instantiation – positional association

```
bit0: DFF port map (rst, clk, sin, S1, open);
```

Signals used in Port Map

- **Actual** signals used in port map can be:
 - scalars
 - vectors
 - array elements
 - literals

INST6B : CHILD6 port map (
 INP (2 downto 0) => QB (4 downto 2),
 INP (3) => reset,
 INP (4) => QB(0),
 outp => SET,
 enable=>'1',
 A(0 to 5)=> O"35";

Sidebar: Array Attributes

- In addition to signal attributes, there are array attributes that return index range information

array'left	returns the left bound of the array index
array'right	returns the right bound of the array index
array'high	returns the upper bound of the array index
array'low	returns the lower bound of the array index
array'length	returns the number of elements in the array
array'range	returns the index range of the array
array'ascending	returns TRUE if array uses ascending index
array'descending	returns TRUE if array uses descending index

Examples of Array Attributes

signal abc: std_logic_vector (7 **downto** 2);

abc'left	returns 7
abc'right	returns 2
abc'high	returns 7
abc'low	returns 2
abc'length	returns 6
abc'range	returns 7 downto 2
abc'ascending	returns FALSE
abc'descending	returns TRUE

Unconstrained Ports

- A component entity may be defined with an input or output port that is an array type with no specification of index constraints:

```
entity mbit_and is  
  Port (din:in std_logic_vector;  
         z:out std_logic);  
end mbit_and;
```

```
architecture mba of mbit_and is  
begin  
  p1:process(din)  
    variable av: std_logic;  
    begin  
      av:='1';  
      for i in din'low to din'high loop  
        if din(i)='0' then av:='0';  
      end if;  
    end loop;  
    z<=av;  
  end process;  
end mba;
```

Constraint Passing

- The index bounds are not determined (constrained) until the component is instantiated:

```
component mbit_and
  port( din : in std_logic_vector;
        z : out std_logic);
end component;

...
signal pbus : std_logic_vector(3 downto 0);
signal bb : std_logic;

...
begin
and1: mbit_and port map (din => pbus, z => bb);
```

Example: 4x4 Unsigned Multiply

- You are provided with two basic components: a 1-bit full adder and a 2-input and gate. Build a structural model of a 4x4 unsigned multiplier

```
entity fadd is  
  Port (a,b,cin: in std_logic;  
         sum,cout: out std_logic);  
end fadd;  
  
architecture gate of fadd is  
begin  
  sum <= a xor b xor cin after 5 ns;  
  cout <= (a and b) or (a and cin)  
         or (b and cin) after 5 ns;  
end gate;
```


```
entity and2 is  
  Port (a,b: in std_logic;  
        c: out std_logic);  
end and2;  
  
architecture gate of and2 is  
begin  
  c <= a and b after 3 ns;  
end gate;
```

Unsigned Multiply Operations

Multiplicand	>					X3	X2	X1	X0
Multiplier	>				x	Y3	Y2	Y1	Y0
1st partial product	>					Y0X3	Y0X2	Y0X1	Y0X0
2nd partial product	>				Y1X3	Y1X2	Y1X1	Y1X0	
3rd partial product	>			Y2X3	Y2X2	Y2X1	Y2X0		
4th partial product	>	+	Y3X3	Y3X2	Y3X1	Y3X0			
Final product	>	P7	P6	P5	P4	P3	P2	P1	P0

- Components operations are:
 - 4x1-bit multiplies
 - 4-bit additions

4x1 Unsigned Multiply

 

entity mpy4x1 **is**

Port(x: **in** std_logic_vector(3 **downto** 0));

y: **in** std_logic;

z: **out** std_logic_vector(3 **downto** 0));

end mpy4x1;

architecture struct of mpy4x1 **is**
component and2

port(a,b: **in** std_logic;

c: **out** std_logic);

end component;

begin

bit3: and2 **port map**(a=>x(3),
b=>y, c=>z(3));


bit2: and2 **port map**(a=>x(2),
b=>y, c=>z(2));

bit1: and2 **port map**(a=>x(1),
b=>y, c=>z(1));

bit0: and2 **port map**(a=>x(0),
b=>y, c=>z(0));

end struct;

4-bit adder

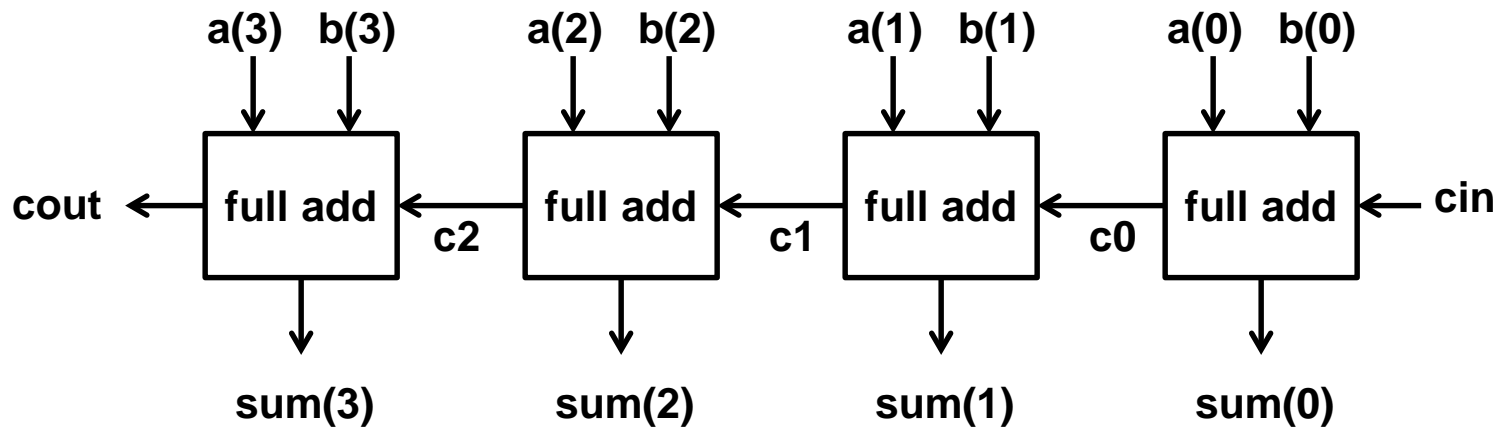

entity add4 is

```
Port( a, b: in std_logic_vector(3 downto 0);
```


```
cin: in std_logic;
```

```
sum: out std_logic_vector(3 downto 0);
```

```
cout: out std_logic);
```

```
end add4;
```

4-bit adder (cont.)

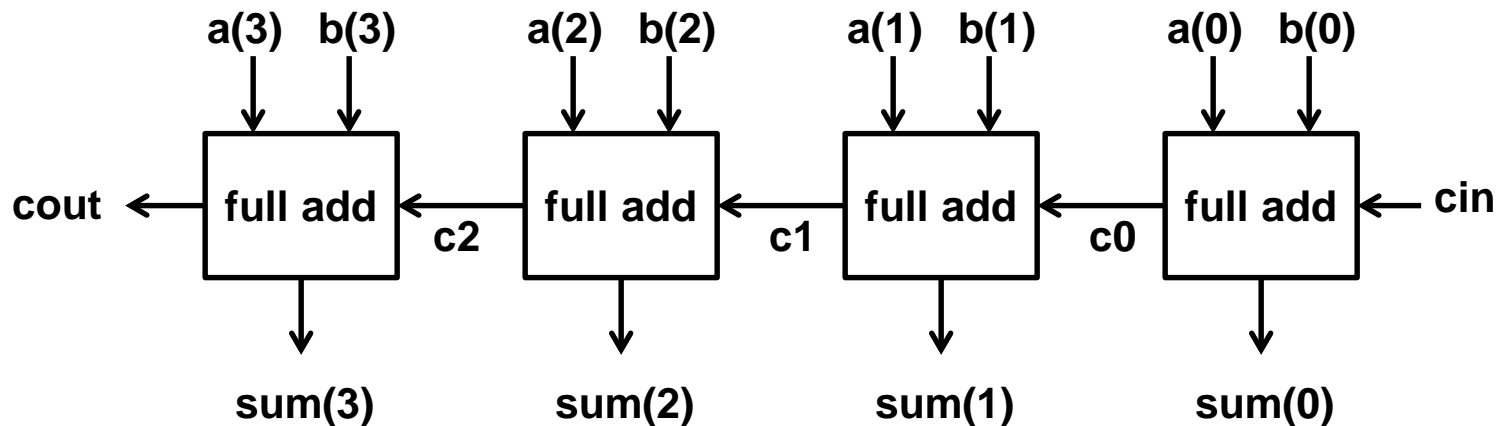

architecture struct of add4 is

```
signal c: std_logic_vector(2 downto 0);
```

```
component fadd
```

```
port( a, b, cin : in std_logic;
```

```
sum, cout :out std_logic);
```

```
end component;
```

```
begin
```

```
x0: fadd port map(a=>a(0), b=>b(0),  
cin=>cin, sum=>sum(0),cout=>c(0));
```


```
x1: fadd port map(a=>a(1), b=>b(1),  
cin=>c(0), sum=>sum(1),cout=>c(1));
```

```
x2: fadd port map(a=>a(2), b=>b(2),  
cin=>c(1), sum=>sum(2),cout=>c(2));
```

```
x3: fadd port map(a=>a(3), b=>b(3),  
cin=>c(2), sum=>sum(3),cout=>cout);
```

```
end struct;
```

4x4 multiplier – putting it all together

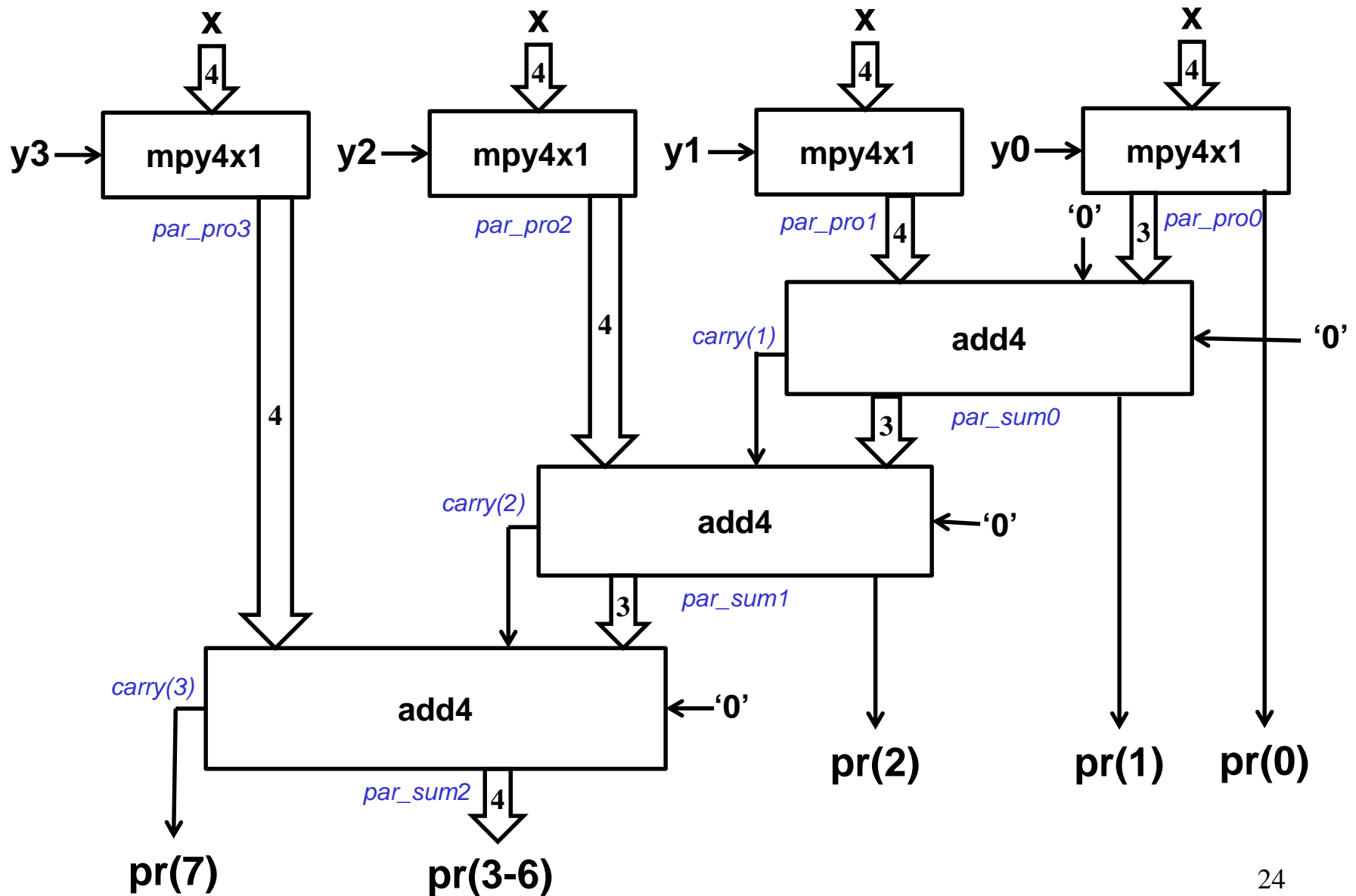

4x4 multiplier – entity

entity mult4x4 is

Port (x, y : **in** std_logic_vector(3 **downto** 0);

 pr : **out** std_logic_vector(7 **downto** 0));

end mult4x4;

4x4 multiplier – architecture declarations

architecture struct **of** mult4x4 **is**

signal par_pr0, par_pr1, par_pr2, par_pr3: std_logic_vector(3 **downto** 0);

signal par_sum1, par_sum2, par_sum3: std_logic_vector(3 **downto** 0);

signal carry: std_logic_vector(3 **downto** 1);

component mpy4x1 **is**

port(x : **in** std_logic_vector(3 **downto** 0);

 y : **in** std_logic;

 z : **out** std_logic_vector(3 **downto** 0));

end component;

component add4 **is**

port(a,b : **in** std_logic_vector(3 **downto** 0);

 cin : **in** std_logic;

 sum :**out** std_logic_vector(3 **downto** 0);

 cout : **out** std_logic);

end component;

4x4 multiplier – architecture instantiations

begin

```
mpy0: mpy4x1 port map(x => x, y => y(0), z => par_pr0);
```

```
mpy1: mpy4x1 port map(x => x, y => y(1), z => par_pr1);
```

```
mpy2: mpy4x1 port map(x => x, y => y(2), z => par_pr2);
```

```
mpy3: mpy4x1 port map(x => x, y => y(3), z => par_pr3);
```

```
subadd1: add4 port map(a => '0' & par_pr0(3 downto 1), b => par_pr1,  
    cin => '0', sum => par_sum1, cout => carry(1) );
```

```
subadd2: add4 port map(a => carry(1) & par_sum1(3 downto 1), b => par_pr2,  
    cin => '0', sum => par_sum2, cout => carry(2) );
```

```
subadd3: add4 port map(a => carry(2) & par_sum2(3 downto 1), b => par_pr3,  
    cin => '0', sum => par_sum3, cout => carry(3) );
```

```
z <= carry(3) & par_sum3 & par_sum2(0) & par_sum1(0) & par_pr0(0);
```

end struct;

Exploiting Regularity

- Models so far have captured hierarchy but not regularity
- Instantiating many copies of same component is tedious
 - Imagine a 64x64 bit multiplier!
- Take for example, 4-bit adder:

architecture struct of add4 is

```
signal c: std_logic_vector(2 downto 0);  
component fadd  
port( a, b, cin : in std_logic;  
      sum, cout : out std_logic);  
end component;
```

begin

```
x0: fadd port map(a=>a(0), b=>b(0),  
  cin=>cin, sum=>sum(0),cout=>c(0));  
x1: fadd port map(a=>a(1), b=>b(1),  
  cin=>c(0), sum=>sum(1),cout=>c(1));  
x2: fadd port map(a=>a(2), b=>b(2),  
  cin=>c(1), sum=>sum(2),cout=>c(2));  
x3: fadd port map(a=>a(3), b=>b(3),  
  cin=>c(2), sum=>sum(3),cout=>cout);  
end struct;
```

Generate Statement

- Allows us to generate an “array” of instantiations:

architecture struct of add4 is

-- **signal** c: std_logic_vector(2 **downto** 0);

component fadd

port(a, b, cin : **in** std_logic;

sum, cout :**out** std_logic);

end component;

signal carry: std_logic_vector(4 **downto** 0);

begin

carry(0)<=cin;

GADD: for k **in** 3 **downto** 0 **generate**

FA: fadd **port map**(a=>a(k), b=>b(k), cin=>carry(k),
sum=>sum(k),cout=>carry(k+1));

end generate GADD;

cout<=carry(4);

end struct;