

E246 Electronics & Instrumentation

Lecture 1: Introduction and Review of Basic Electronics



Course Personnel

Instructor:

Yi Guo

Office: Burchard 207

Office Hours: Tuesday & Thursday 2-3pm

Ph: (201) 216-5658

Email: yguo1@stevens.edu

Textbook

Essentials of Electrical and Computer Engineering, by David V. Kerns and J. David Irwin, Pearson Prentice Hall., ISBN 0-13-923970-7, 2004.

Reference Books

R. C. Dorf and J. A. Svoboda, *Introduction to Electric Circuits*, 6/e, John Wiley & Sons, 2004.

J. W. Nilsson and S. A. Riedel, *Electric Circuits*, 6/e, Prentice Hall, 2000.

G. Rizzoni, *Principles and Applications of Electrical Engineering*, 3/e, McGraw Hill, 2000.

Reference Books

- # Allan R. Hambley, Electronics, 2nd Ed. Prentice Hall, 2000
 - # Smith and Dorf, Circuits, Devices and Systems, 5th Ed. John Wiley & Sons, 1992.
 - # Bobrow, Fundamentals of Electrical Engineering, 2nd Ed. Oxford University Press, 1994.
 - # Horowitz and Hill, The Art of Electronics, 2nd Ed. Cambridge University Press, 1989.
-

Today's Plan

- # Introduction to Electrical Engineering
 - # Electric circuit variables
 - # Electric circuit elements: resistor, independent and dependent sources, voltmeters and ammeters, switches
 - # Kirchhoff's Law
 - # Sections in textbook: 1.1~1.2,2.1~2.3
-

The Subject

- # *Electrical engineering* is the profession concerned with systems that produce, transmit, and measure electric signals.
 - # It combines the physicist's models of natural phenomena with the mathematician's tools for manipulating those models to produce systems that meet practical needs.
-

Five Major Classifications of Electrical Systems

- # Communication systems
 - # Computer systems
 - # Control systems
 - # Power systems
 - # Signal-processing systems
-

Circuit Theory

- # An electric circuit is a *mathematical model* that approximates the behavior of an actual electrical system.
 - # The models, the mathematical techniques, and the language of circuit theory will form the intellectual framework for your future engineering endeavors.
-

Problem Solving Process


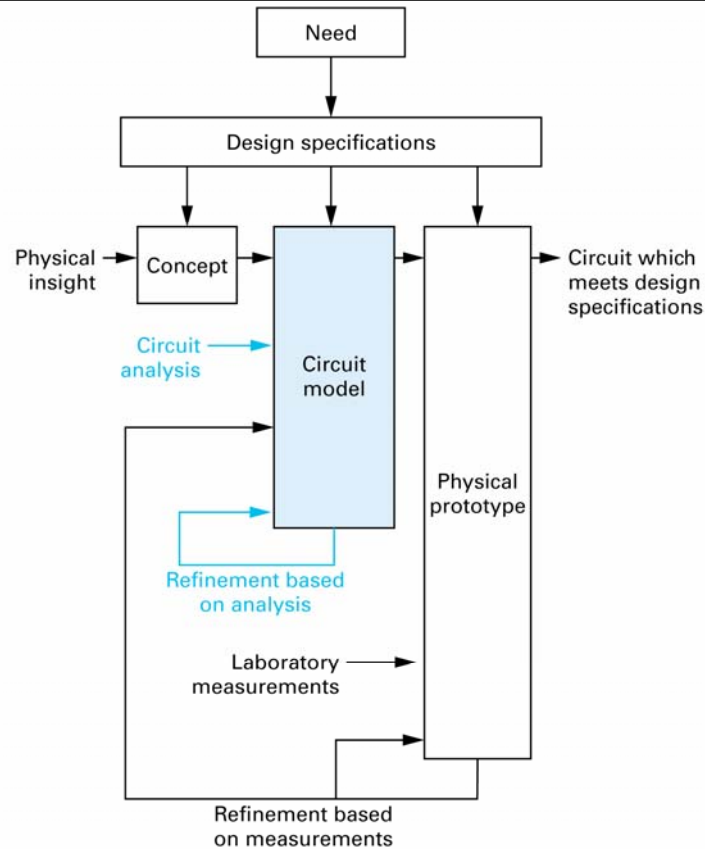


Figure 1.4 A conceptual model for electrical engineering design

What is Electric Circuit?


- # An electric circuit is an interconnection of *electrical elements* linked together in a *closed path* so that an *electric current* may flow continuously.

A simple circuit:

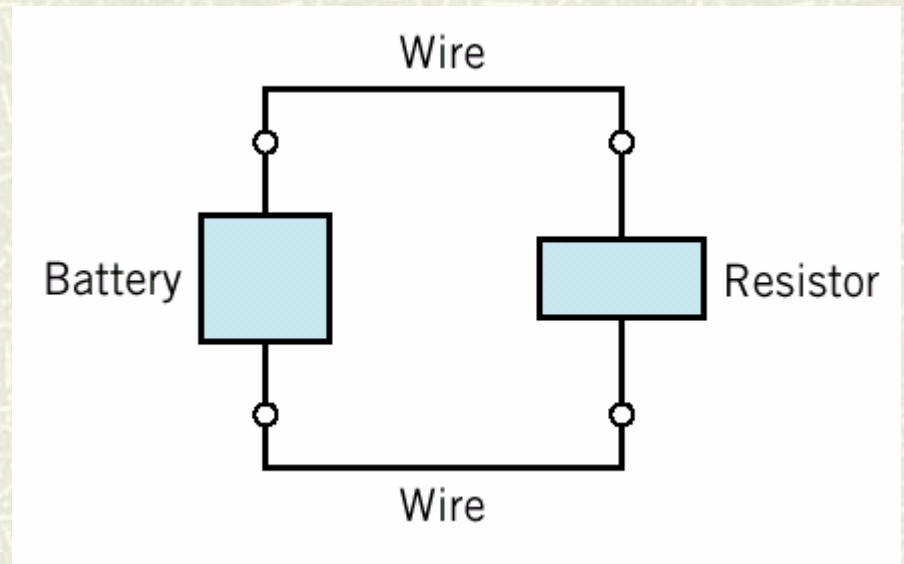

Basic Circuit Variables

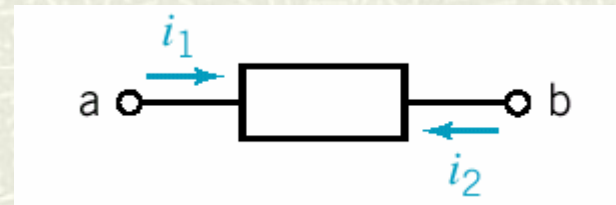
- # **Charge:** the quantity of electricity responsible for electric phenomena, denoted by q , Unit: Coulomb, C.
- # **Current:** the time rate of flow of electric charge past a given point, denoted by i .
 - Mathematical representation: $i = \frac{dq}{dt}$
 - Unit: ampere, A.



Current


■ Two different types:

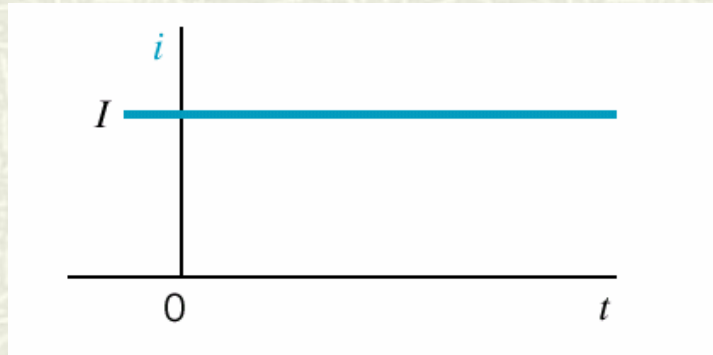- DC (direct current) is a current of *constant magnitude*



- AC (alternating current) is a time-varying current $i(t)$ that has a sinusoidal form).
-

Time-Varying Current

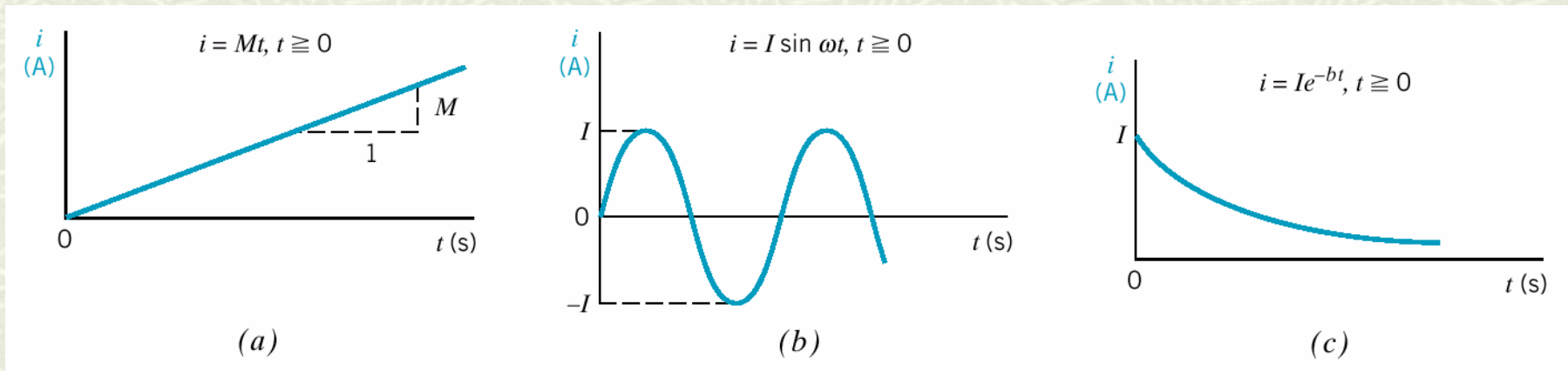


- (a) A ramp with a slope M .
- (b) A sinusoid.
- (c) An exponential. I is a constant. The current i is zero for $t < 0$.

Voltage


- # Definition: energy required to move a unit positive charge from the – terminal to the + terminal across an element.
- # Mathematical representation:

$$v = \frac{dw}{dq}$$

- # Unit: volt, V.

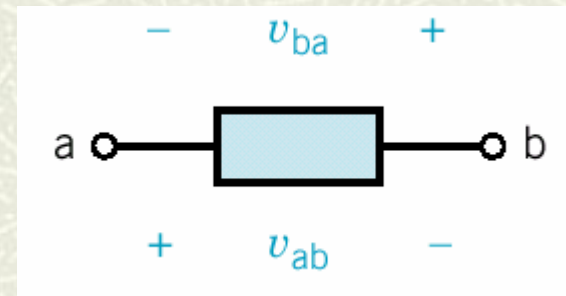

Voltage

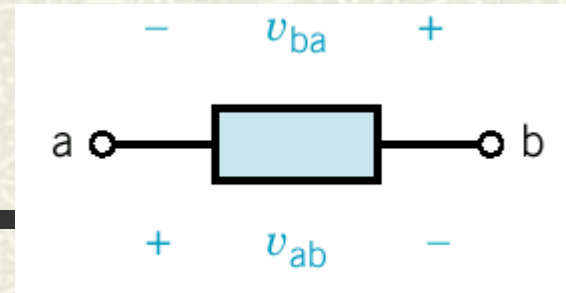

- # The direction of a voltage is given by its polarities:
 - The voltage v_{ab} is proportional to the work required to move a positive charge from terminal a to terminal b.
 - The voltage v_{ba} is proportional to the work required to move a positive charge from terminal b to terminal a.
- # v_{ab} is read as “the voltage at terminal a with respect to terminal b”; or, “the voltage drop from terminal a to terminal b”.

$$V_{ab} = -V_{ba}$$

Power


Definition: time rate of expending or absorbing energy.

Mathematical representation: $p = \frac{dw}{dt}$

Unit: watt, W.

Relation with current and voltage:

$$p = vi$$

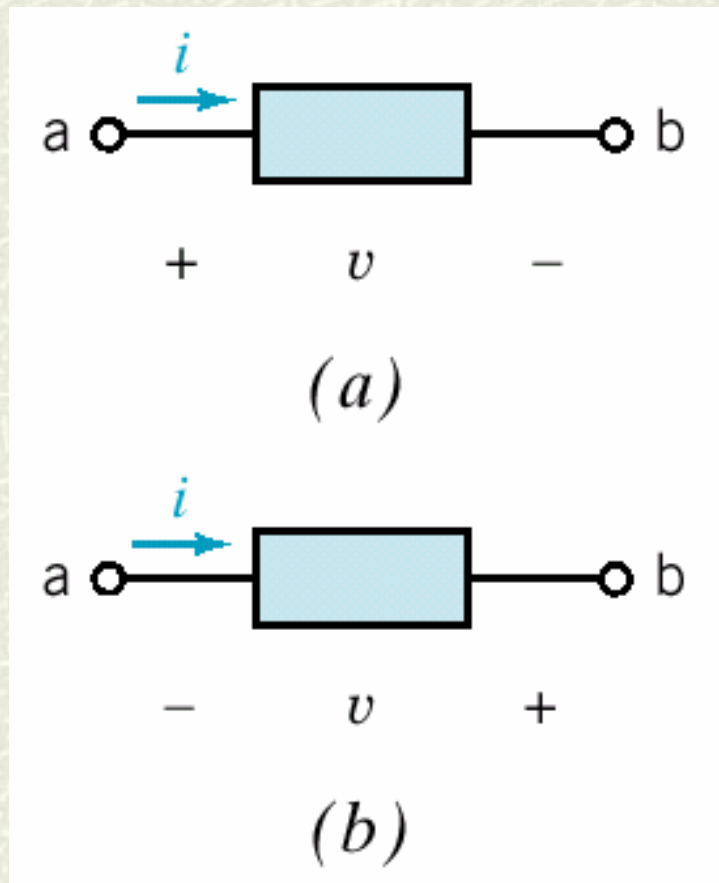

Passive convention: the assigned direction of the current is directed from the + terminal to the – terminal.

- a). Power *absorbed* (or *dissipated*) by the element, as v and i adhere to the passive convention.
- b). Power *supplied* (or *delivered*) by the element, as v and i do not adhere to the passive convention.

Concepts

‡ A **linear** elements satisfies the property of *superposition* and *homogeneity*.

IF $i_1 \rightarrow v_1$

$$i_2 \rightarrow v_2$$


THEN $i_1 + i_2 \rightarrow v_1 + v_2$

$$ki_1 \rightarrow kv_1$$

$$ki_2 \rightarrow kv_2$$


A **passive** element *absorbs* energy.

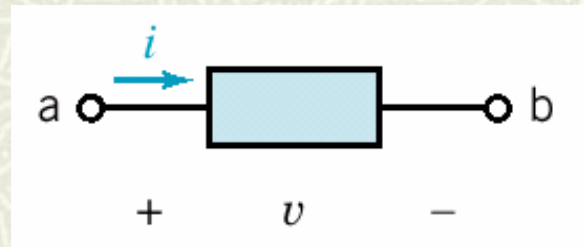
$$w = \int_{-\infty}^t v i d\tau \geq 0 \quad \text{for all } t.$$



An **active** element is capable of *supplying* energy.
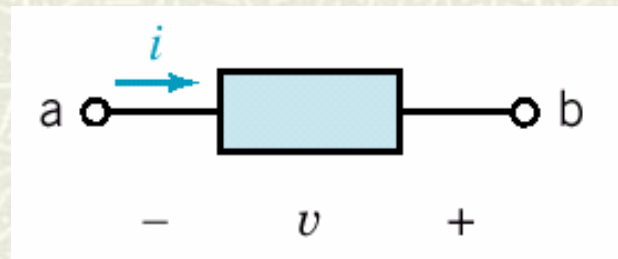
$$w = \int_{-\infty}^t v i d\tau > 0 \quad \text{for at least one } t.$$



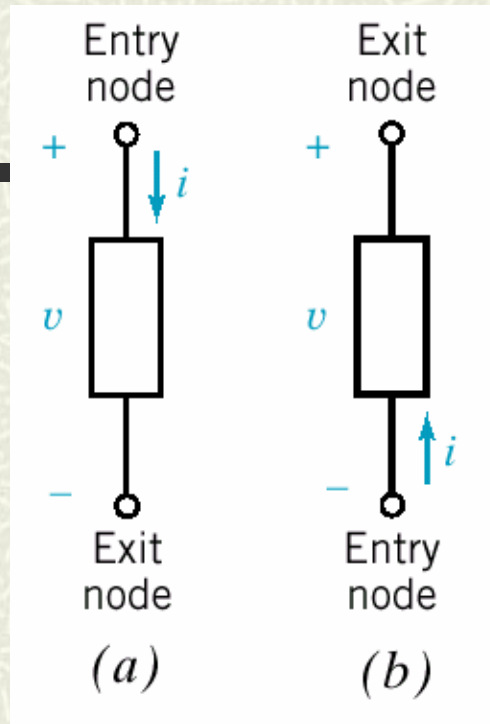


- (a) The entry node of the current i is the positive node of the voltage v ,
- (b) the entry node of the current i is the negative node of the voltage v . The current flows from the entry node to the exit node.


Resistors

Resistors impedes the flow of current.

Unit: Ohm.

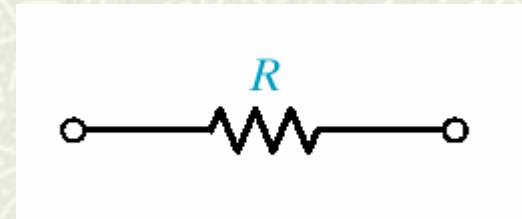

Ohm's law: $v= Ri$

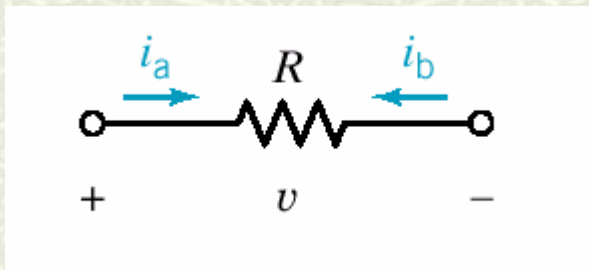

$$v = Ri_a$$

$$v = -Ri_b$$

Power delivered to a resistor:


$$p = vi = v(v/R) = v^2/R$$

$$p = vi = (iR)i = i^2R$$


Independent Sources

- # *Sources*: voltage or current generator capable of supplying energy to a circuit.
 - # *Independent sources*: sources not dependent on other circuit variables.
-

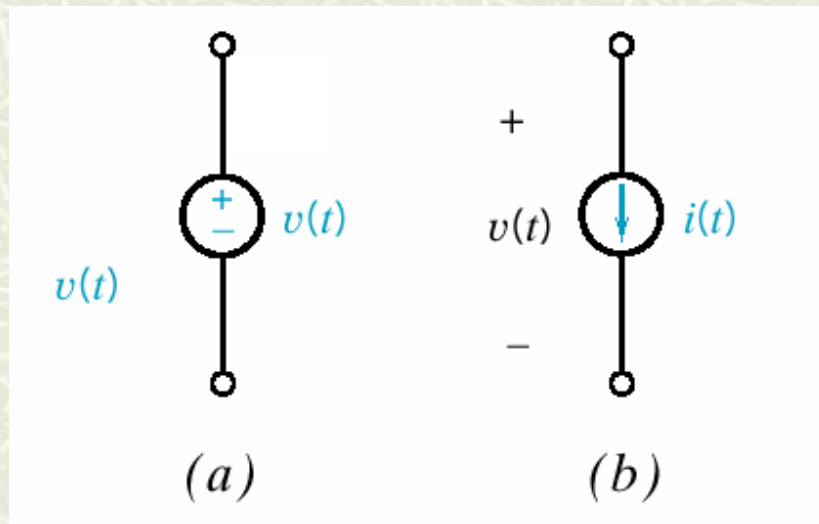-
- (a) Ideal voltage source, denoted by $v(t)$;
(b) Ideal current source, denoted by $i(t)$.






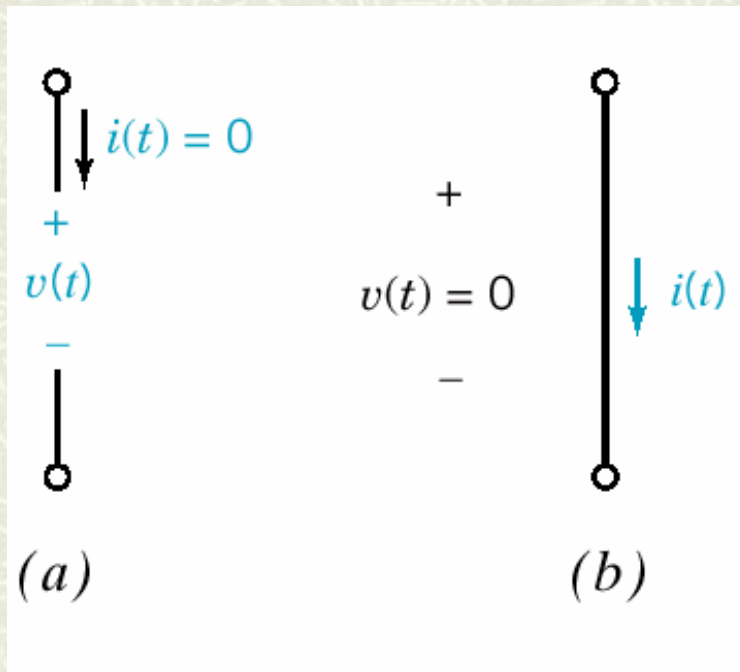
- (a) Open circuit: an ideal current source having $i(t)=0$;
(b) Short circuit: an ideal voltage source having $v(t)=0$.



Dependent Sources


They depend on another circuit variables.

Table 2.8-1 Dependent Sources

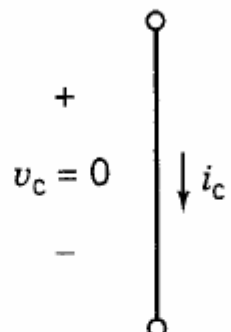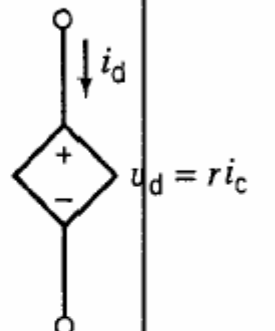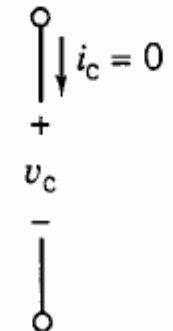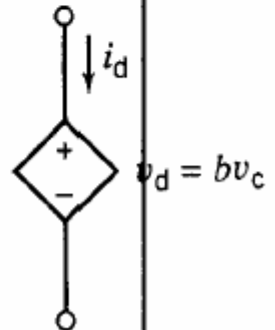Description	Symbol	
<p>Current-Controlled Voltage Source (CCVS)</p> <p>$v_c = 0$</p> <p>r is the gain of the CCVS.</p> <p>r has units of volt/ampere.</p>		
<p>Voltage-Controlled Voltage Source (VCVS)</p> <p>$i_c = 0$</p> <p>b is the gain of the VCVS.</p> <p>b has units of volts/volt.</p>		


**Voltage-Controlled Current Source
(VCCS)**

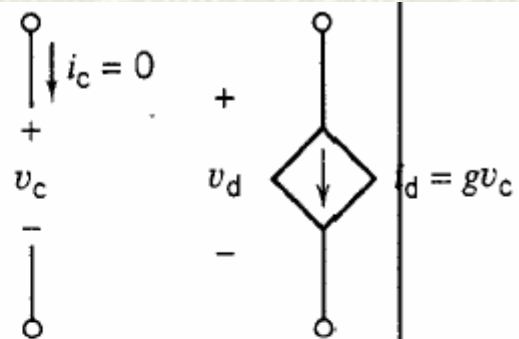g is the gain of the VCCS.
 g has units of amperes/volt.




**Current-Controlled Current Source
(CCCS)**

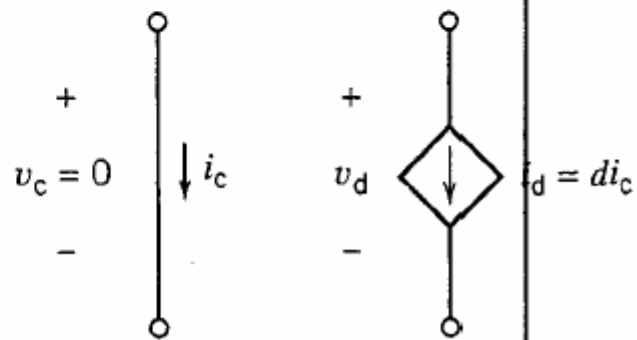d is the gain of the CCCS.
 d has units of amperes/ampere.



Voltmeters

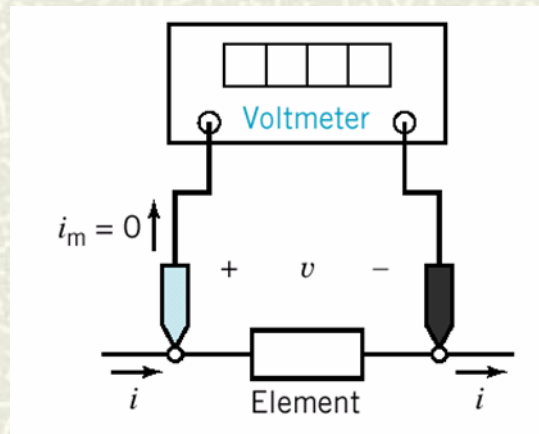
- # An ideal voltmeter measures the voltage *across* its terminals.



It has the terminal current $i_m = 0$.

Ammeters

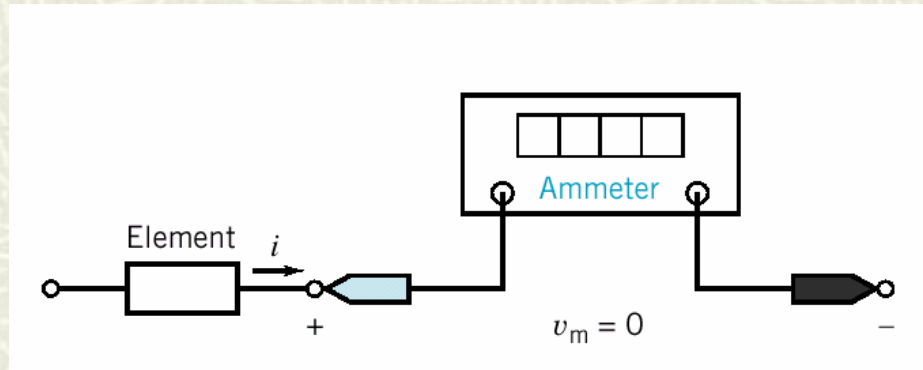
- An ideal ammeter measures the current *flowing through* its terminals.



It has zero voltage across the terminals:

$$v_m = 0.$$


Voltmeters and Ammeters

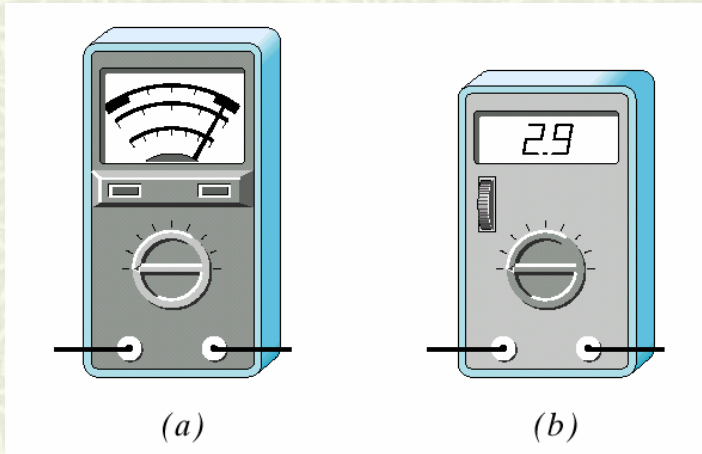

Analog and digital meters.

Probes are color coded: **red** terminal is the positive terminal, black terminal is the negative terminal.


Example:

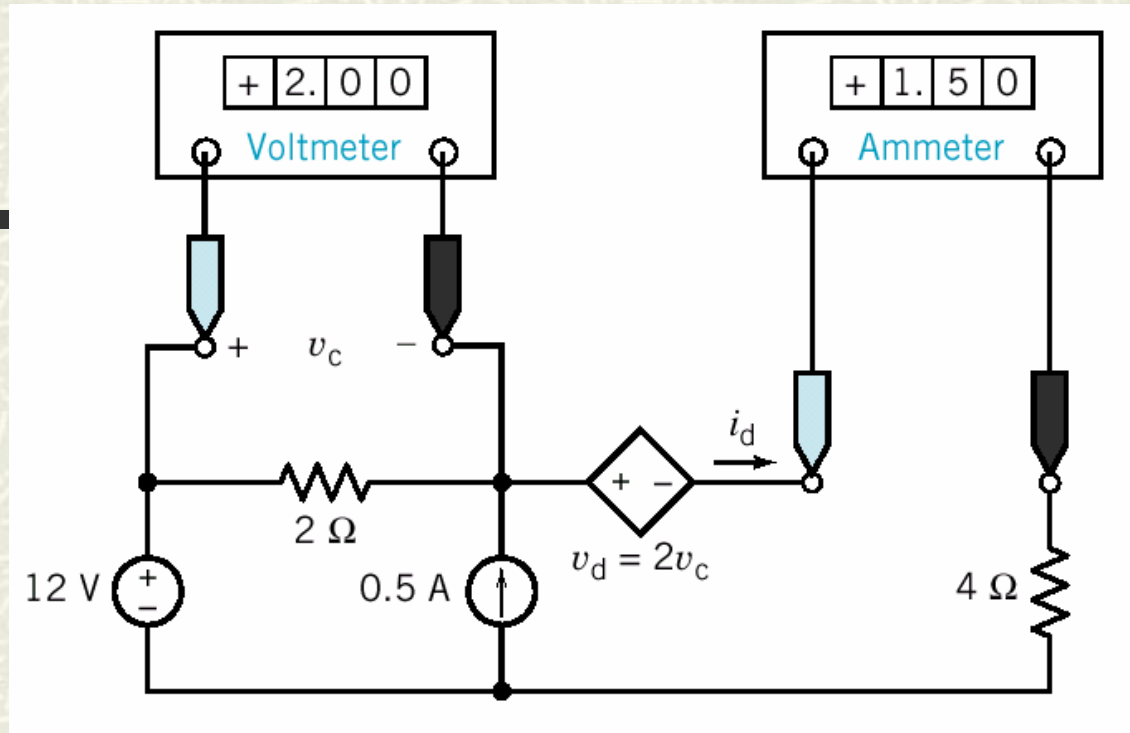

A circuit containing a VCVS. The meters indicate that the voltage of the controlling element is $v_c = 2.0$ volts and that the current of the controlled element is $i_d = 1.5$ amperes. Determine the power absorbed by the VCVS.

Switches



Single-Pole Single-Throw switch:

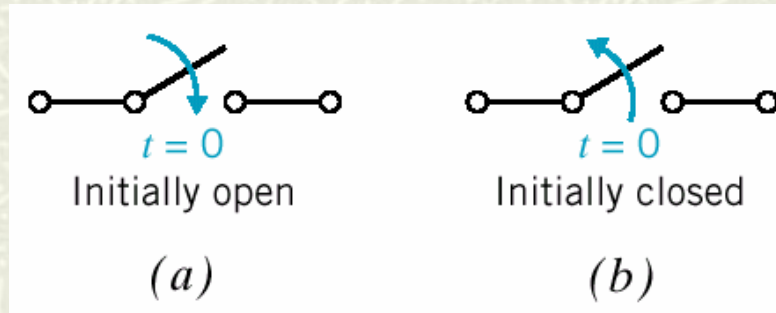


Two distinct states: *open* and *closed*.

Kirchhoff's Law

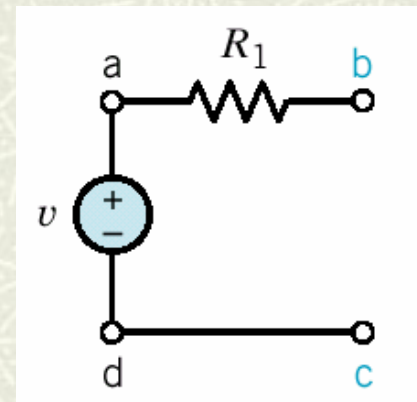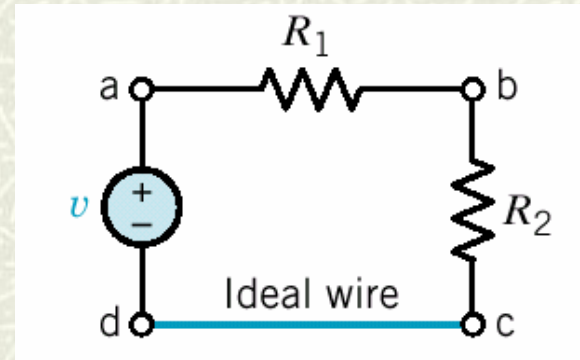- # We consider circuits made up of resistors.
- # We assume *ideal wires*, whose model has zero resistance.
- # We call it an *open circuit* at terminal b-c




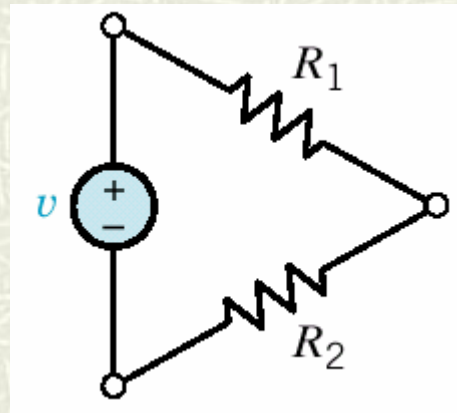Node: A junction in which two or more elements have a common connections, or, a junction of conductors composed of idea wires.



How many nodes in the above figure?

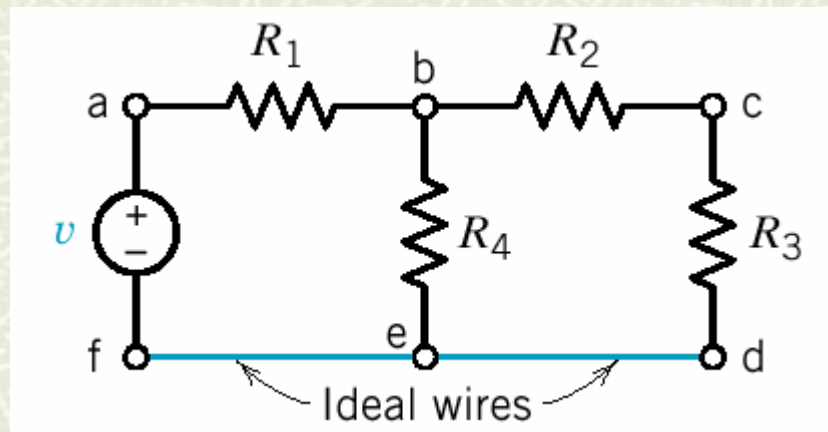Closed path (loop): A traversal through a series of nodes ending at the starting node without encountering a node more than once.




How many loops in the above figure?

Kirchhoff's Current Law

The algebraic sum of the currents into a node at any instant is zero.

i.e. the sum of currents entering the node is equal to the sum of currents leaving the node.

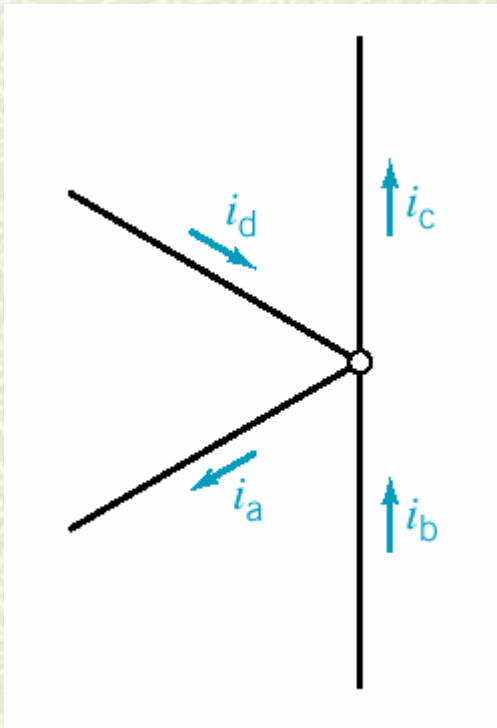Reason: Charge cannot accumulate at a node, as node is a perfect conductor.



$$i_b + i_d = i_a + i_c$$

If assuming entering is positive,

$$-i_a + i_b - i_c + i_d = 0$$


Kirchhoff's Voltage Law

The algebraic sum of the voltages around any closed path in a circuit is zero for all time.

i.e. the voltage rise is equal to the voltage drop in the tracing direction around a closed path.

Reason: Recall that the voltage is work per unit charge. A circuit loop is a conservative system, and the energy required to move a charge around a closed path is zero.

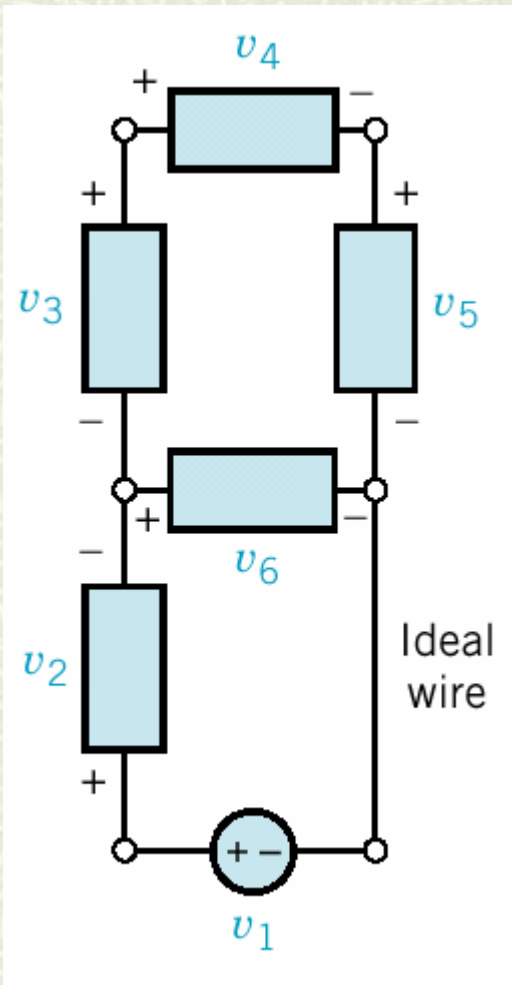-
- # Assign an algebraic sign (reference direction) to each voltage in the loop
 - # A common convention is to use the voltage sign on the first terminal of an element encountered as we traverse a path.
-



$$-v_6 - v_3 + v_4 + v_5 = 0$$